


3 Logic Circuit Analysis and Design: Circuit Minimization.

Analyzing Logic Circuits

 1. From the given logic circuit, write the equation of the circuit;
2. Write the truth table from the equation above;
3. Summary of the operation of the circuit:
 - What conditions that provide the output of '1'
 - What conditions that provide the output of '0'

Note:

If the given circuit is connected to another circuit, we need to know what would happen to that circuit, too.



It can be expressed as: $Y = \bar{A} \bar{B} + \bar{A} B + A B$

A	B	$\bar{A} \bar{B}$	$\bar{A} B$	$A B$	Y
0	0	1	0	0	1
0	1	0	1	0	1
1	0	0	0	0	0
1	1	0	0	1	1

Designing Logic Circuits

From the desired output, write the corresponding **Truth Table**;

- Assign the number of Inputs and Outputs;
- Find the relationship between Inputs and Outputs for all cases;
- Write the **Truth Table**.

Write a **Boolean Equation** from that **Truth Table**;

- In the configuration of either **Sum of Product** or **Product of Sum**.

Designing Logic Circuits

- The **Boolean Equation** comes from the **Truth Table** in the configuration of SOP (or POS),
is **NOT** the shortest equation.
- Sometimes the **Boolean Equation** could be able to be combined several terms in its equation.
- The better equation need to be **shorter**,
or has **less terms and less number of variables**;
- Consequently, the corresponding circuit would be more economical.

Designing Logic Circuits

If we want to reduce the number of gates in the circuit, we need to minimize the output **Equation** by

- To have the least number of terms, or
- To have the least number of variables in the terms, or
- To arrange the term(s) in equation to the appropriate format/gate, repeatedly.

So how could we obtain the **SHORTER** equation?

Designing Logic Circuits

We can minimize a logical Equation by 3 methods:

- Boolean Algebra Method.
- Karnaugh Map Method
- Quine-McCluskey Method

Boolean Algebra

- Use **Algebraical Rules** to reduce the terms in the logical equations;
- The principle was proposed by George **Boole**;
- This method is so-called as **Boolean Algebra**;
 - ➔ The theory of logical relationships;
 - ➔ Using basic operators: NOT, AND (\cdot) and OR ($+$)
 - ➔ The principle has logical **relationships, as follows.**

Boolean Algebra

The Boolean algebra consists of basic **11** relationships:

$$\overline{\overline{A}} = A$$

$$A \cdot A = A$$

$$A \cdot 0 = 0$$

$$A + 0 = A$$

$$A + \overline{A} = 1$$

$$A \cdot B + A \cdot C = A \cdot (B + C)$$

$$A + A = A$$

$$A \cdot 1 = A$$

$$A + 1 = 1$$

$$A \cdot \overline{A} = 0$$

$$A + \overline{A} \cdot B = A + B$$

Boolean Algebra


1. Inverse

Give the output with the opposite logic to the input:

If $A = 0$, then $\bar{A} = 1$ and $\overline{\bar{A}} = 0$

And $A = 1$, then $\bar{A} = 0$ and $\overline{\bar{A}} = 1$

Then $\overline{\bar{A}} = A$

 


Boolean Algebra

2. AND with 0:

$$A \cdot 0 = 0$$

Put Zero to the input of AND gate, make the output to be Zero.

 - Force the output of the AND gate to be Zero.




Boolean Algebra

3. OR with 0: $A + 0 = A$

If $A = 1$, then the output will be 1.

And if $A = 0$, then the output will be 0.

 ➤ Use to drive the next circuit by the OR gate.




Boolean Algebra

4. AND with 1: $A \cdot 1 = A$

If $A = 1$, then the output will be 1.

And if $A = 0$, then the output will be 0.

 ➤ Use to drive the next circuit by the AND gate.




Boolean Algebra

 5. OR with 1: $A + 1 = 1$

Put One to the input of OR gate, make the output to One, too.

➤ Force the output of the OR gate to One/High state.




Boolean Algebra

 6. OR with itself: $A + A = A$

Tie the signal at the input of the OR gate, the output will produce that signal.

- Reproduce the same signal at the output by the OR gate.




Boolean Algebra

 7. AND with itself: $A \cdot A = A$

Tie the signal at the input of the AND gate, the output will produce that signal.

- Reproduce the same signal at the output by the AND gate.




Boolean Algebra

8. OR of the Complement Pair: $A + \overline{A} = 1$

If $A = 1$, so $\overline{A} = 0$ then the output will be 1.

And if $A = 0$, so $\overline{A} = 1$ then the output will be 1.

 ➤ OR of the Complement Pair always produces 1




Boolean Algebra

9 AND of the Complement Pair: $A \cdot \bar{A} = 0$

If $A = 1$, so $\bar{A} = 0$ then the output will be 1.

And if $A = 0$, so $\bar{A} = 1$ then the output will be 1.

 ➤ AND of the Complement Pair always produces 0



Boolean Algebra

10. Association: $A \cdot B + A \cdot C = A \cdot (B + C)$

Proved by the truth table below:

A	B	C	AB	AC	$AB+AC$	$B+C$	$A \cdot (B+C)$
0	0	0	0	0	0	0	0
0	0	1	0	0	0	1	0
0	1	0	0	0	0	1	0
0	1	1	0	0	0	1	0
1	0	0	0	0	0	0	0
1	0	1	0	1	1	1	1
1	1	0	1	0	1	1	1
1	1	1	1	1	1	1	1

Boolean Algebra

11. $A + \overline{A} \cdot B = A + B$

Proved by the truth table below:

A	B	\overline{A}	$\overline{A} \cdot B$	$A + \overline{A} \cdot B$	$A + B$
0	0	1	0	0	0
0	1	1	1	1	1
1	0	0	0	1	1
1	1	0	0	1	1

De' Morgan Theory

De Morgan's Theory

- Used to convert the logic terms between (N)AND and (N)OR;

$$\overline{A \cdot B} = \overline{A} + \overline{B}$$

NAND \leftrightarrow OR


$$\overline{A + B} = \overline{A} \cdot \overline{B}$$

NOR \leftrightarrow AND

De' Morgan Theory

$$\overline{A \cdot B} = \overline{A} + \overline{B}$$

A	B	$A \cdot B$	$\overline{A \cdot B}$	\overline{A}	\overline{B}	$\overline{A} + \overline{B}$
0	0	0	1	1	1	1
0	1	0	1	1	0	1
1	0	0	1	0	1	1
1	1	1	0	0	0	0

 


NAND of 2 inputs = **OR** with **NOT** inputs

De' Morgan Theory

$$\overline{A + B} = \bar{A} \cdot \bar{B}$$

A	B	$A \cdot B$	$\overline{A + B}$	\bar{A}	\bar{B}	$\bar{A} \cdot \bar{B}$
0	0	0	1	1	1	1
0	1	1	0	1	0	0
1	0	1	0	0	1	0
1	1	1	0	0	0	0

 

NOR of 2 inputs = **AND** with **NOT** inputs


Minimization by Boolean Algebra

Minimize the obtained equation by the 11 relationships in the Boolean Algebra:


- To get less terms; [or Number of gates]
 - To get less operators/variables; [or Number of gates]
 - To get the desired gates. [use ONLY NANDs/NORs]
- (Using De' Morgan) (Used in IC Design Fabrication)

Minimization by Boolean Algebra

Example: Minimize the circuit below

 



$$Y = \bar{A}\bar{B} + \bar{A}B + AB$$

 

$$Y = \bar{A} + B$$


Minimization by Boolean Algebra

Example: Minimize the circuit below

  

Minimization by Boolean Algebra

Example: Minimize the logic circuit

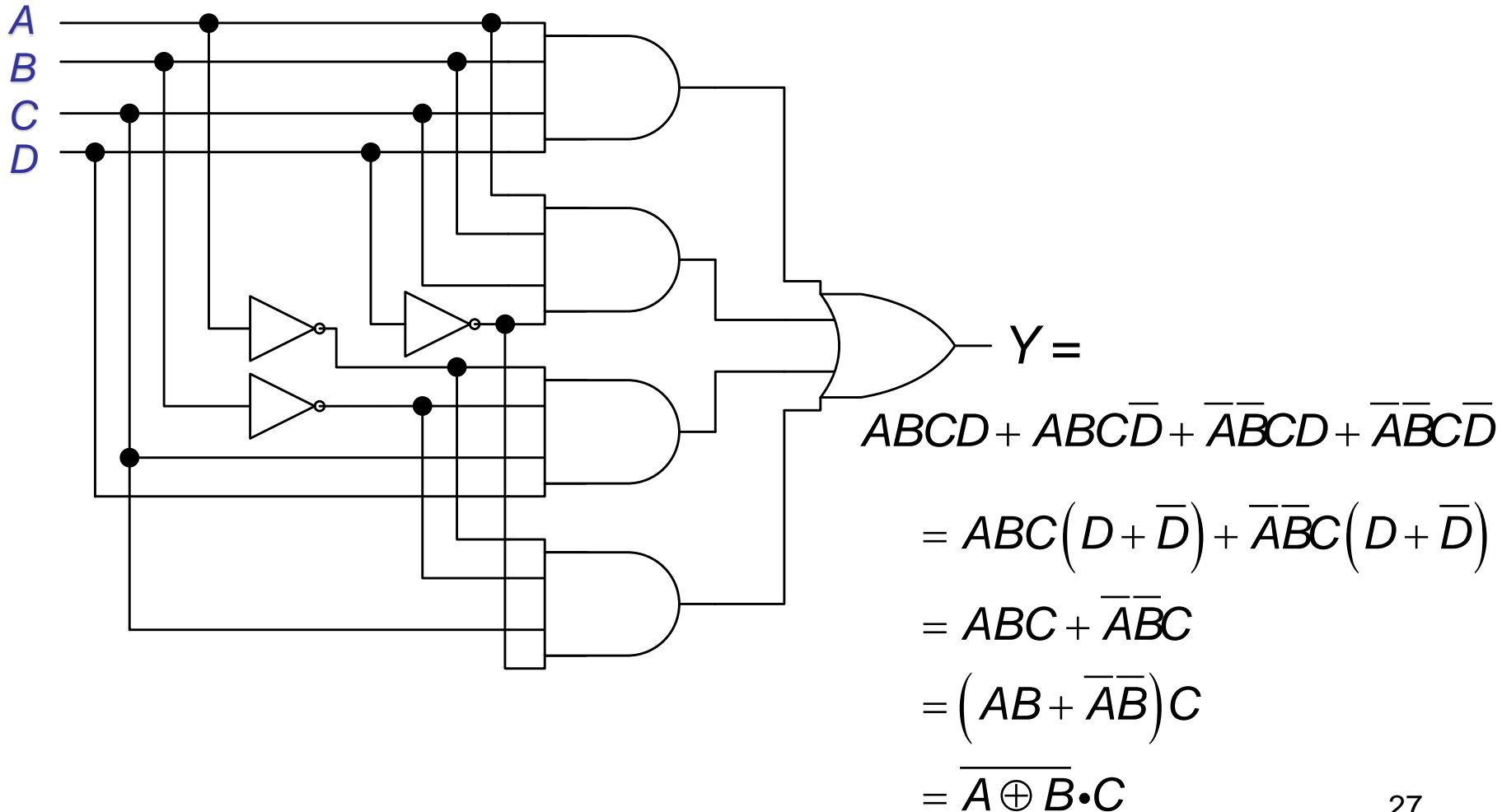

Produce the Logic Equation from Truth Table

Example: Find the Boolean Eq. from the truth table.

Input			Output
A	B	C	Y
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	1

Solution: Found that the outputs of '1' occur at ABC of 011, 110 and 111.

$$Y = 011 + 110 + 111$$

$$Y = \text{min}3 + \text{min}6 + \text{min}7$$

$$Y = \Sigma \text{min}(3, 6, 7) = F(A, B, C)$$

$\bar{A}BC$ Which is another way to write the SOP output by minterms.

And produces the output equation:

$AB\bar{C}$

ABC

$$Y = \bar{A}BC + AB\bar{C} + ABC$$

Example: Design the circuit from the logic equation:


$$Y = \bar{A}BC + A\bar{B}\bar{C} + ABC$$

$$= \bar{A}BC + AB(\bar{C} + C)$$

$$= \bar{A}BC + AB$$

$$= B(\bar{A}C + A)$$

$$= B(C + A)$$

 

Example: Design the circuit from the truth table:

Input			Output
A	B	C	Y
0	0	0	1
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	1
1	0	1	0
1	1	0	1
1	1	1	1

$$\overline{A}\overline{B}\overline{C}$$

$$\overline{A}\overline{B}C$$

$$\overline{A}BC$$


$$A\overline{B}\overline{C}$$

$$A\overline{B}C$$

$$ABC$$

 Example: Design the circuit from the logic equation:

$$\begin{aligned} Y &= \bar{A} \bar{B} \bar{C} + A \bar{B} \bar{C} + AB \bar{C} + \bar{A} \bar{B} C + \bar{A} B C + AB C \\ &= \bar{B} \bar{C} (A + \bar{A}) + AB (C + \bar{C}) + \bar{A} C (B + \bar{B}) \\ &= \bar{B} \bar{C} + AB + \bar{A} C \end{aligned}$$




XOR & XNOR Gates using Boolean Algebra.


$$\begin{aligned}Y_1 &= A \oplus B \\&= A \cdot \bar{B} + \bar{A} \cdot B\end{aligned}$$

$$\begin{aligned}Y_2 &= \overline{A \oplus B} \\&= \overline{A \cdot \bar{B} + \bar{A} \cdot B} \\&= \overline{(A \cdot \bar{B}) \cdot (\bar{A} \cdot B)} \\&= (\bar{A} + B) \cdot (A + \bar{B}) \\&= (\bar{A} + B) \cdot A + (\bar{A} + B) \cdot \bar{B} \\&= \bar{A}A + AB + \bar{A}\bar{B} + B\bar{B} \\&= \bar{A}\bar{B} + AB\end{aligned}$$

XOR & XNOR Gates using SOP Form.

 

$$Y = A \oplus B$$

 

$$Y = \overline{A \oplus B}$$

Input		Output
A	B	Y
0	0	0
0	1	1
1	0	1
1	1	0


$$\overline{A} \cdot B$$

$$A \cdot \overline{B}$$


Input		Output
A	B	Y
0	0	1
0	1	0
1	0	0
1	1	1

$$\overline{A} \cdot \overline{B}$$

$$A \cdot B$$

 


$$Y = \overline{A}B + A\overline{B}$$

 

$$Y = \overline{A}\overline{B} + AB$$

Logical Circuit Design: Half-Adder [1]

 

Input		Output	
A	B	C _o	Sum
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	0

$$Sum = A \oplus B$$

$$C_o = A \cdot B$$


$$= \overline{\overline{A \oplus B}}$$

$$= \overline{\overline{A} \overline{B} + AB}$$


$$= \overline{\overline{A} \overline{B} + AB}$$

$$= \overline{\overline{A} + \overline{B} + AB}$$

Logical Circuit Design: Half-Adder [2]

 


6 Gates

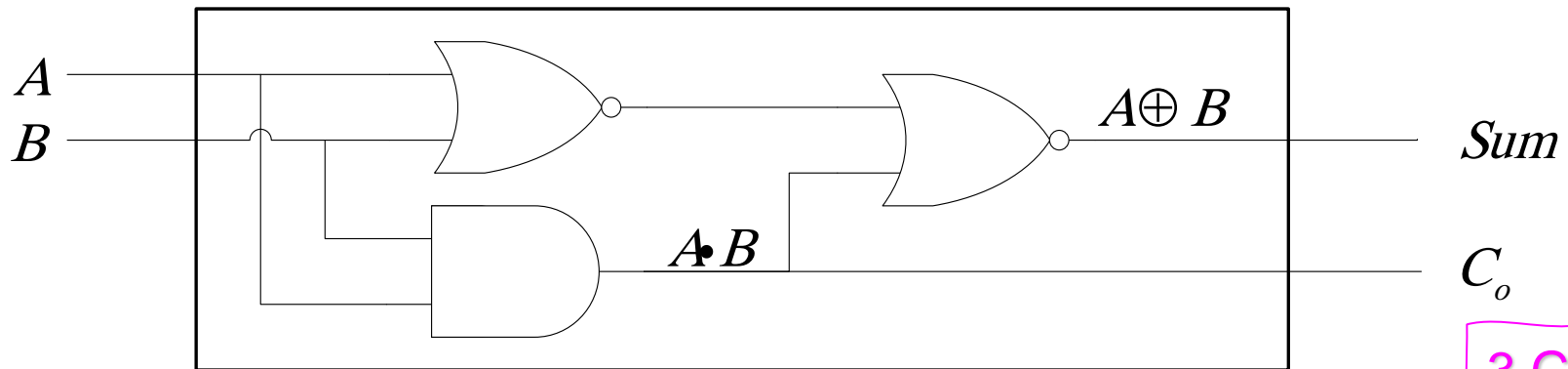

3 Gates

Logical Circuit Design: Full Adder [1]

Input			Output	
C_{in}	A	B	C_o	Sum
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

 


$$\begin{array}{r} C_{in} \\ A \\ + B \\ \hline Co \quad Sum \end{array}$$

Logical Circuit Design: Full Adder [2]

$$Sum = \overline{A}\overline{B}C_{in} + \overline{A}B\overline{C}_{in} + A\overline{B}\overline{C}_{in} + ABC_{in}$$

$$= (\overline{A}\overline{B} + \overline{A}B) \overline{C}_{in} + (\overline{A}\overline{B} + AB) C_{in}$$

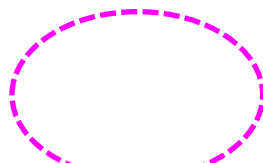
$$= (A \oplus B) \overline{C}_{in} + (\overline{A \oplus B}) C_{in}$$

$$= (A \oplus B) \oplus C_{in}$$

$$C_o = \overline{A}BC_{in} + A\overline{B}C_{in} + AB\overline{C}_{in} + ABC_{in}$$


$$= C_{in}(\overline{A}B + A\overline{B}) + AB(\overline{C}_{in} + C_{in})$$

$$= C_{in}(A \oplus B) + AB$$


Logical Circuit Design: Full Adder [3]

$$Sum = (A \oplus B) \oplus C_{in}$$

$$C_o = C_{in}(A \oplus B) + AB$$

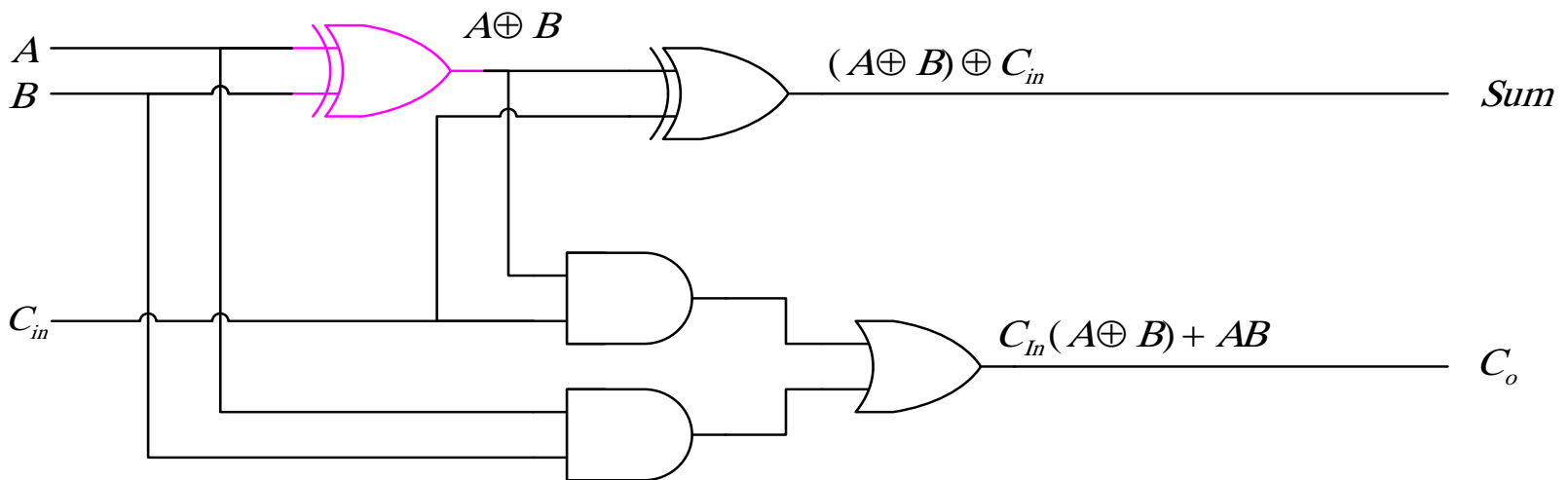


Logical Circuit Design: Full Adder [4]



 


$$Sum = (A \oplus B) \oplus C_{in}$$

$$C_o = C_{in}(A \oplus B) + AB$$

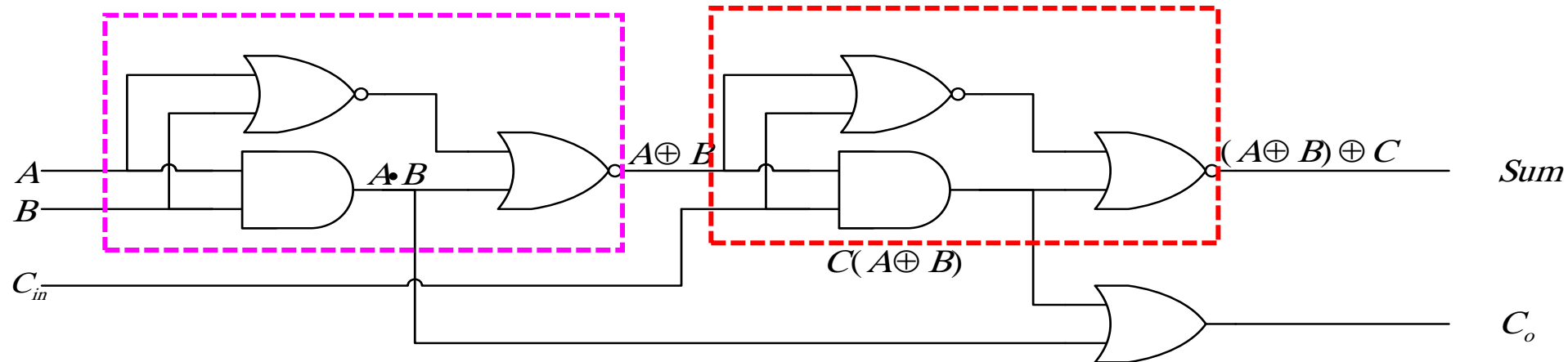

Logical Circuit Design: Full Adder [5]

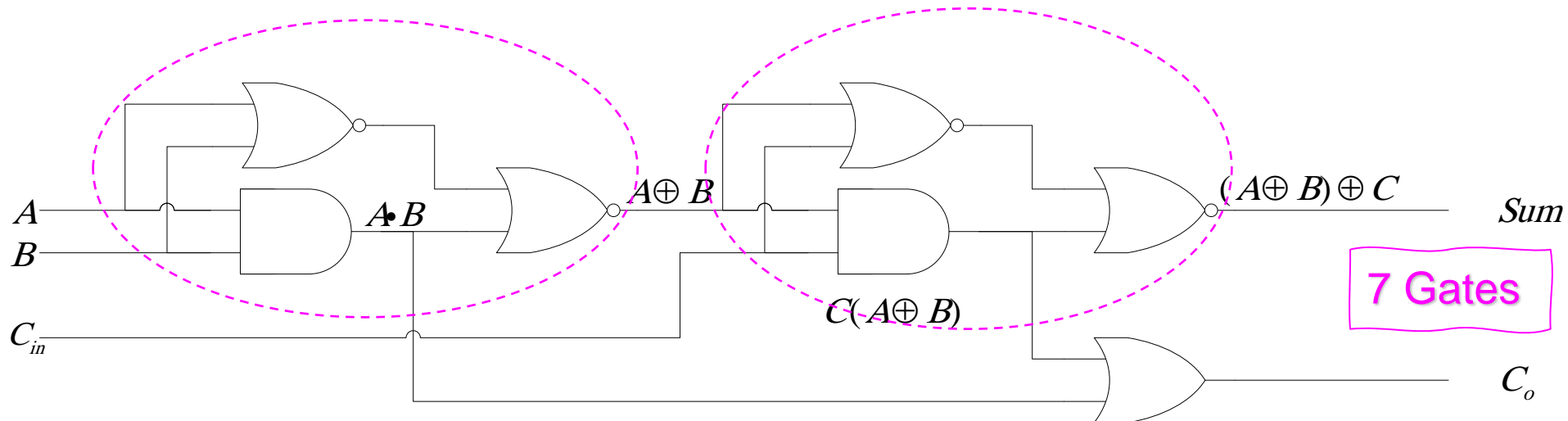  

Boolean Algebra Usage: Summary

- The Boolean Algebra can be used to reduce the terms in the output equation,
- But we have to **recall** all rules in the theory;
- This requires some **practice and experience** to manage the terms in the equation;
- So, the method is suitable for the system with **several** inputs.
- For the system with **more** inputs, we would rather use:
 - Karnaugh Map
 - Quine-Mc Cluskey Method.

Karnaugh Map

- Karnaugh's Map is a Table of $2^m \times 2^n$,
- where $m + n =$ total number of the variables.
- The column and row are in the sequence of the grey codes: 000, 001, 011, 010,...
- First, we put the '1' marks on the diagram corresponds to the individual minterms, and the '0' marks for the rest.
- Typically, total number of variables is not more than 4,
- Otherwise, the diagram would get too big to handle, more complicated to consider.

Karnaugh Map

K-Map Plot:

$$Y = F(B, A)$$


		A	
		\bar{A}	A
B	\bar{B}	$\bar{B}\bar{A}$	$\bar{B}A$
	B	$B\bar{A}$	BA

$$Y = F(C, B, A)$$

		BA			
		$\bar{B}\bar{A}$	$\bar{B}A$	BA	$B\bar{A}$
C	\bar{C}	$\bar{C}\bar{B}\bar{A}$	$\bar{C}\bar{B}A$	$\bar{C}BA$	$\bar{C}B\bar{A}$
	C	$C\bar{B}\bar{A}$	$C\bar{B}A$	CBA	$CB\bar{A}$

$$Y = F(D, C, B, A)$$

		BA			
		$\bar{B}\bar{A}$	$\bar{B}A$	BA	$B\bar{A}$
DC	$\bar{D}\bar{C}$	$\bar{D}\bar{C}\bar{B}\bar{A}$	$\bar{D}\bar{C}\bar{B}A$	$\bar{D}\bar{C}BA$	$\bar{D}\bar{C}B\bar{A}$
	$\bar{D}C$	$\bar{D}C\bar{B}\bar{A}$	$\bar{D}C\bar{B}A$	$\bar{D}CBA$	$\bar{D}CB\bar{A}$
	DC	$DC\bar{B}\bar{A}$	$DC\bar{B}A$	$DCBA$	$DCB\bar{A}$
	$D\bar{C}$	$D\bar{C}\bar{B}\bar{A}$	$D\bar{C}\bar{B}A$	$D\bar{C}BA$	$D\bar{C}B\bar{A}$

 

Karnaugh Map

K-Map Plot:

$Y = F(B, A)$

		A	
		\bar{A}	A
B	\bar{B}	$\bar{A} \bar{B}$ 00	$\bar{A} B$
	B	$A \bar{B}$	$A B$

$Y = F(C, D, A, B)$

		AB			
		00	01	11	10
CD	00				
	01				
	11				
	10				

$Y = F(C, A, B)$

		AB			
		00		11	
C	0				
	1				

$Y = F(A, B, C, D, E)$

		CDE			
		000	001	011	01
A	B				
	00				
	01				

Karnaugh Map: How to use it

- Fill the outputs (0/1) into the condition corresponding to the individual minterms in the Karnaugh's diagram;
- Marks (encircle) all the outputs of '1';
- Try to make a group the output of '1' with the neighboring output(s) of '1' to make a bigger group of 2, 4, 8, ..., 2^n by drawing a bigger circle around either in line or in square.
- In the individual group, take away the variable that has changed its logic, namely, we can reduce that variable from the minterms;
- Finally, collect/sum all the outcome products as the output equation.

Karnaugh Map : Example 1

Input			Output
<i>A</i>	<i>B</i>	<i>C</i>	<i>Y</i>
0	0	0	1
0	0	1	1
0	1	0	1
0	1	1	1
1	0	0	0
1	0	1	0
1	1	0	0
1	1	1	1

$$Y = F(A, B, C) = \sum \text{Min}(0, 1, 2, 3, 7) \\ = \sum m(0, 1, 2, 3, 7)$$

		AB			
		00	01	11	10
C	0	1	1	0	0
	1	1	1	1	0

A \ BC				
	00	01	11	10
0				
1				

Karnaugh Map : Example 1

Input			Output
<i>A</i>	<i>B</i>	<i>C</i>	<i>Y</i>
0	0	0	1
0	0	1	1
0	1	0	1
0	1	1	1
1	0	0	0
1	0	1	0
1	1	0	0
1	1	1	1

		AB			
		00	01	11	10
C	0	1	1	0	0
	1	1	1	1	0

$$Y = \overline{A} + BC$$

Karnaugh Map : Example 2

Input			Output
A	B	C	Y
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1

$$Y = F(A, B, C) = \sum \text{Min}(1, 5, 6, 7)$$

		AB			
C		00	01	11	10
	0	0	0	1	0
1	1	1	0	1	1

$$Y = AB + \bar{B}C$$

A \ BC	00	01	11	10
0				
1				

Karnaugh Map : Example 3

Input				Output
A	B	C	D	Y
0	0	0	0	1
0	0	0	1	0
0	0	1	0	1
0	0	1	1	0
0	1	0	0	0
0	1	0	1	1
0	1	1	0	0
0	1	1	1	0
1	0	0	0	1
1	0	0	1	0
1	0	1	0	1
1	0	1	1	0
1	1	0	0	1
1	1	0	1	1
1	1	1	0	1
1	1	1	1	1

$$Y = F(A, B, C, D)$$

$$= \sum \text{Min}(0, 2, 5, 8, 10, 12, 13, 14, 15)$$

		AB			
		00	01	11	10
CD	00	1	0	1	1
	01	0	1	1	0
	11	0	0	1	0
	10	1	0	1	1

$$Y = AB + \bar{B}\bar{D} + \bar{B}\bar{C}D$$

Karnaugh Map : Example 4

Simplify (minimize) this Boolean equation

$Y = F(A, B, C, D) = \sum m(2, 3, 6, 10, 11)$ using the Karnaugh Map.

Solution

The first step is to change the Boolean equation to the Sum of Product form:

$$Y = \overline{A}\overline{B}\overline{C}\overline{D} + \overline{A}\overline{B}CD + \overline{A}B\overline{C}\overline{D} + \overline{A}BCD + A\overline{B}C\overline{D}$$

Then draw the Karnaugh Map as follows:

Karnaugh Map : Example 4

CD \ AB	00	01	11	10
00	0	0	1	1
01	0	0	0	1
11	0	0	0	0
10	0	0	1	1

Then gets the Answer: $Y = \bar{B}C + \bar{A}C\bar{D}$

Karnaugh Map : Example 5

Determine the product terms for each of the Karnaugh maps in Figure 4–32 and write the resulting minimum SOP expression.

 


FIGURE 4-32

Solution The resulting minimum product term for each group is shown in Figure 4–32. The minimum SOP expressions for each of the Karnaugh maps in the figure are

$$\begin{aligned}
 \text{(a)} \quad & AB + BC + \overline{A}\overline{B}\overline{C} & \text{(b)} \quad & \overline{B} + \overline{A}\overline{C} + AC \\
 \text{(c)} \quad & \overline{A}\overline{B} + \overline{A}\overline{C} + \overline{A}BD & \text{(d)} \quad & \overline{D} + \overline{A}\overline{B}\overline{C} + \overline{B}\overline{C}
 \end{aligned}$$

Karnaugh Map : Don't Care Case

Don 't Care

- The case that can be ignored its logic value;
- Expressed by the symbol d , (x , $*$, ...);
- Therefore, d could be any logic either 0 or 1;
- Help to simplify the output equation since it can be any logic:

Typically, Set $d = 1$ for SOP form;

Set $d = 0$ for POS form.

Minimize the case with Don't Care:

Set logic of the Don't Care that helps for Output Minimization;

- All '1' state need to be used;
- But Just use ONLY the Don't Cares as necessary.

Karnaugh Map: Don't Care Case

Use the Karnaugh Map to design circuits for the truth table below.

Input

N

0

1

2

3

4

5

6

7

8

9

10

11

12

13

14

15

Input				Output
A	B	C	D	Y
0	0	0	0	1
0	0	0	1	0
0	0	1	0	1
0	0	1	1	0
0	1	0	0	0
0	1	0	1	1
0	1	1	0	0
0	1	1	1	1
1	0	0	0	1
1	0	0	1	0
1	0	1	0	d
1	0	1	1	0
1	1	0	0	d
1	1	0	1	d
1	1	1	0	d
1	1	1	1	1

$$Y = F(A, B, C, D)$$


$$= \sum m($$

$$+ \sum d($$

Karnaugh Map: Don't Care Case

$$Y = F(A, B, C, D) = \sum m(0, 2, 5, 7, 8, 15) + \sum d(10, 12, 13, 14)$$

AB \ CD	00	01	11	10
00	1	0	0	1
01	0	1	1	0
11	d	d	1	d
10	1	0	0	d

 

$$Y = BD + \overline{B}\overline{D}$$