

9 Combinational Circuit Design Using MSI (Medium Scale IC)

Introduction

Combinational Circuit Design Using MSI (Medium Scale IC)

e.g.


- Multiplex (MUX),
 - Decoder (DX),
 - Read only Memory (ROM)
 - Programmable Logic Devices (PLD)
- Next Week

MULTIPLEXER


- A multiplexer (MUX) is a device that allows digital information from several sources to be routed onto a single line for transmission over that line to a common destination;
- The basic multiplexer has many data-input lines and a single output line.
- It also has data-selection inputs, which indicates the input channel for data transmission to the output.

MULTIPLEXER

 Circuit symbols of n-to-1 Data Selector/Multiplexer (n:1 MUX)




 Circuit symbols of 4-to-1 Data Selector/Multiplexer (4:1 MUX)



MULTIPLEXER


Data Selection of 4-to-1 Multiplexer

 

DATA-SELECT INPUTS		INPUT SELECTED
S_1	S_0	
0	0	D_0
0	1	D_1
1	0	D_2
1	1	D_3

MULTIPLEXER

 Schematic circuit diagram of the Multiplexer with 4 Inputs



Combinational Circuit Design Using MULTIPLEXER

Combinational Circuit Design Using MULTIPLEXER

- Reduce the complication of the variables in the truth table.
- Reduce the number of logical gates by using MUX IC instead


As in the following example

Combinational Circuit Design Using MULTIPLEXER:

Example of 3 Variables

Design a logical logic circuit that provides the outputs as following truth table

ค่าจำนวนฐานสิบ	A	B	C	Output (Y)
0	0	0	0	1
1	0	0	1	0
2	0	1	0	1
3	0	1	1	1
4	1	0	0	0
5	1	0	1	1
6	1	1	0	1
7	1	1	1	0

 


Let's see a MUX IC: MAX4691-MAX4694

Combinational Circuit Design Using MULTIPLEXER:

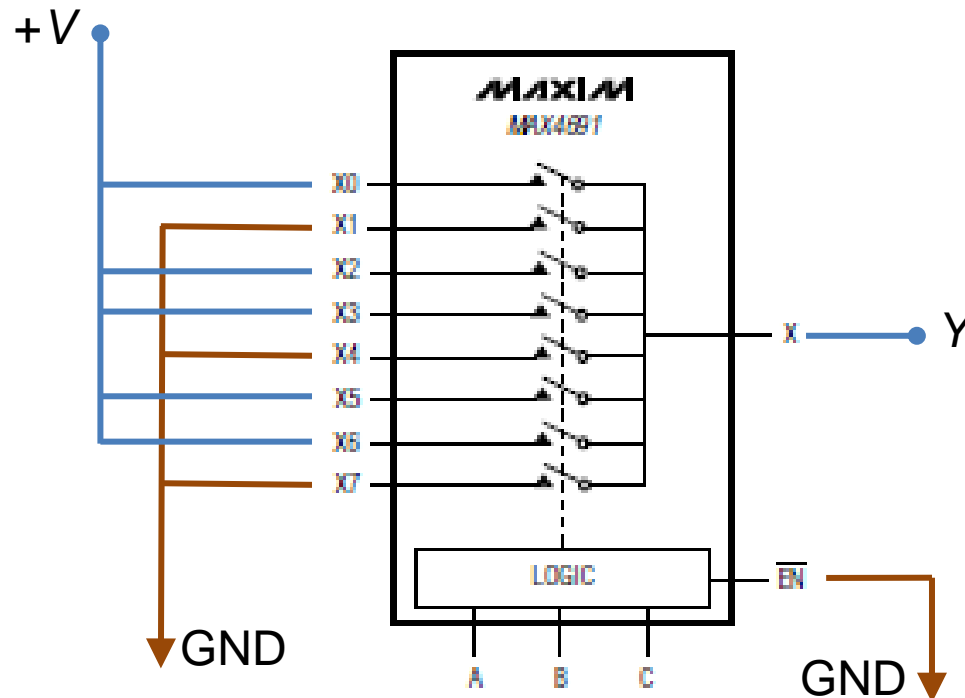Example of 3 Variables

- Since it is a circuit that has 8 input signals, 8:1 MUX is employed.
- The output signals of 1 occurs at the input signal = 0, 2, 3, 5 and 6;
- The output signals of 0 occurs at the input signal = 1, 4 and 7.
- So, use MULTIPLEXER to replace this mixed logic circuit as follows



Combinational Circuit Design Using MULTIPLEXER:

Example of 3 Variables

- In design using MUX
- We can create a larger MUX from a smaller MUX connected in parallel.
- We can replace a larger MUX and replace it with a smaller MUX in conjunction with VEM principles.
- From the previous example, If we set C to be the Entered Variable, we get:

$$Y = \sum m(0, 2, 3, 5, 6) = \overline{A}\overline{B}\overline{C} + \overline{A}B(\overline{C} + C) + A\overline{B}C + ABC = f(A, B)$$

A \ B	0	1
0	<u>C</u>	1
1	C	<u>C</u>

Combinational Circuit Design Using MULTIPLEXER:

Example of 3 Variables

For the requirement of the output:


$$Y = \sum m(0, 2, 3, 5, 6) = \overline{A}\overline{B}\overline{C} + \overline{A}B(\overline{C} + C) + A\overline{B}\overline{C} + ABC\overline{C} = f(A, B)$$

We can write the VEM as following table:

B \ A	0	1
	\overline{C}	C
0	\overline{C}	C
1	$\overline{C} + C$	\overline{C}

➔

B \ A	0	1
	\overline{C}	C
0	\overline{C}	C
1	1	\overline{C}

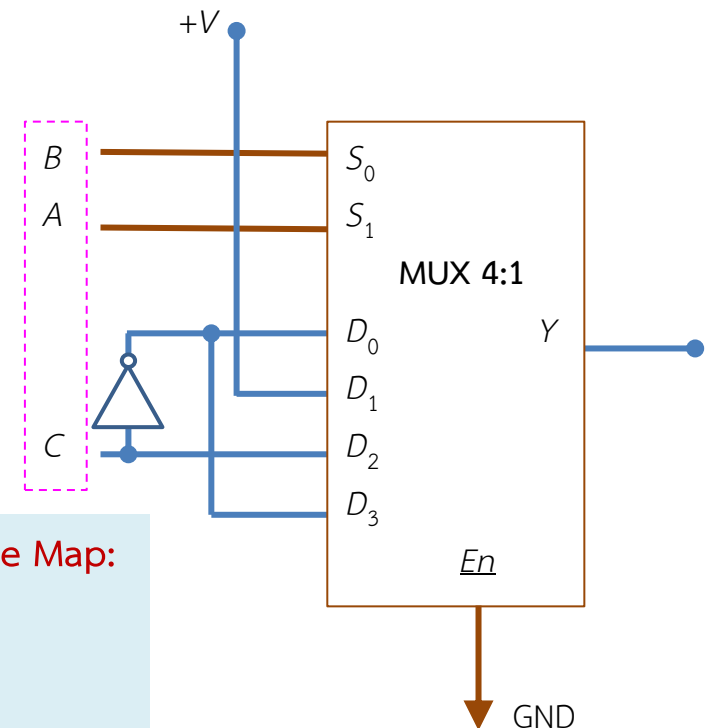

- As the principle of VEM of N variables, and n entered in the Map:
- The Size of MULTIPLEXER used in the system will be:

MULTIPLEXER of $2^{N-n} : 1$

- Typically, the largest MUX is 16:1 or $2^4:1$.
- For the system with the N variable, the no. of variables has to put in the map would be $n = N - 4$.

Combinational Circuit Design Using MULTIPLEXER:

Example of 4 Variables

To design a mixed logic circuit whose outputs signal is

$$Y = \overline{A}\overline{B}\overline{C}\overline{D} + \overline{A}\overline{B}C\overline{D} + \overline{A}B\overline{C}\overline{D} + \overline{A}B\overline{C}D + \overline{A}BCD$$

If we use 8:1 MULTIPLEXER, it can handle only 3 variables.

So, we need to put one variable in to map by marking D :

$$Y = \overline{A}\overline{B}C(\overline{D} + D) + \overline{A}\overline{B}\overline{C}(D) + \overline{A}B\overline{C}(\overline{D}) + \overline{A}B\overline{C}(\overline{D}) = f(A, B, C)$$

AB \ C		AB			
		00	01	11	10
C	0	0	\overline{D}	D	1
	1	0	0	0	\overline{D}

Combinational Circuit Design Using MULTIPLEXER:

Example of 4 Variables

For outputs signal

$$Y = \overline{A}\overline{B}\overline{C}(\overline{D} + D) + \overline{A}\overline{B}CD + \overline{A}B\overline{C}\overline{D} + \overline{A}B\overline{C}D = f(A, B, C)$$

Then we can write the VEM as:

AB \ C		AB			
		00	01	11	10
C	0	0	\overline{D}	D	1
	1	0	0	0	\overline{D}

And can get the circuit




0:

1:

D:

\overline{D} :

 

Combinational Circuit Design Using MULTIPLEXER:

Example of 5 Variables

To design a mixed logic circuit whose output signal is

$$Y = \overline{A}\overline{B}\overline{C}\overline{D}\overline{E} + \overline{A}\overline{B}\overline{C}\overline{D}E + \overline{A}\overline{B}\overline{C}D\overline{E} + \overline{A}\overline{B}\overline{C}DE + \overline{A}\overline{B}C\overline{D}\overline{E} + \overline{A}\overline{B}C\overline{D}E + \overline{A}\overline{B}CD\overline{E} + \overline{A}\overline{B}CDE$$

If we use 8:1 MULTIPLEXER, it can handle only 3 variables.

So, we need to put TWO variables in to map by marking DE:

$$Y = \overline{A}\overline{B}(\overline{D}E + \overline{D}\overline{E}) + \overline{A}\overline{B}C(\overline{D}E) + \overline{A}\overline{B}C(DE) + \overline{A}\overline{B}C(\overline{D}\overline{E} + D\overline{E}) + \overline{A}\overline{B}C(DE)$$

AB		00	01	11	10
C	0	DE	$\overline{D}\overline{E} + D\overline{E}$	$\overline{D}\overline{E}$	0
	1	0	0	DE	$\overline{D}\overline{E} + D\overline{E}$

AB		00	01	11	10
C	0	DE	\overline{E}	$\overline{D}\overline{E}$	0
	1	0	0	DE	\overline{D}


Combinational Circuit Design Using MULTIPLEXER: Example of 5 Variables

Then we can write the VEM as:

AB					
		00	01	11	10
C	0	DE	$\overline{DE+DE}$	$\overline{D} \overline{E}$	0
	1	0	0	D E	$\overline{DE+DE}$



AB					
		00	01	11	10
C	0	DE	\overline{E}	$\overline{\overline{DE}}$	0
	1	0	0	DE	\overline{D}

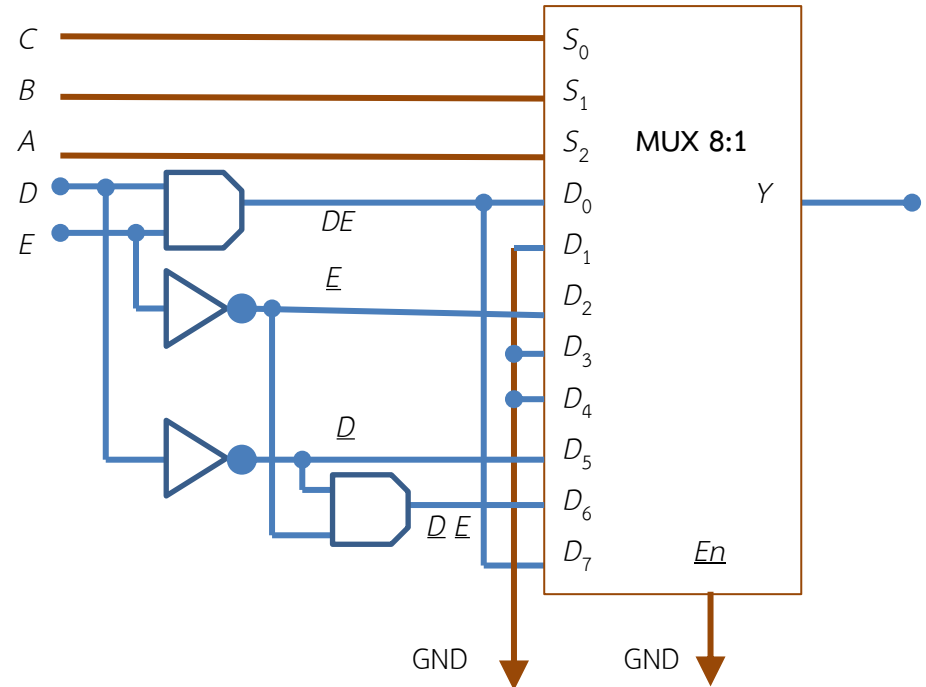

And can get the circuit



The greater number of variables entered in the map,
The more complication in design of the control circuit.


The Expansion the SIZE of MULTIPLEXER: 16n to 1 MULTIPLEXER.

- For more input channels,
- we want to expand the MULTIPLEXER to be a larger size.
- We can do this by gather a number of MULTIPLEXERs together.
- For example, if a system of 64 channels required,
- we have to use four MUX 16: 1 for 64 channel inputs,
- and one MUX 4: 1 to gather them together for ONE output.
- As follows

The Expansion the SIZE of MULTIPLEXER: 16n to 1 MULTIPLEXER.


Example of a 64 channels switching system

35 = 10 0011₂
12 = 00 1100₂

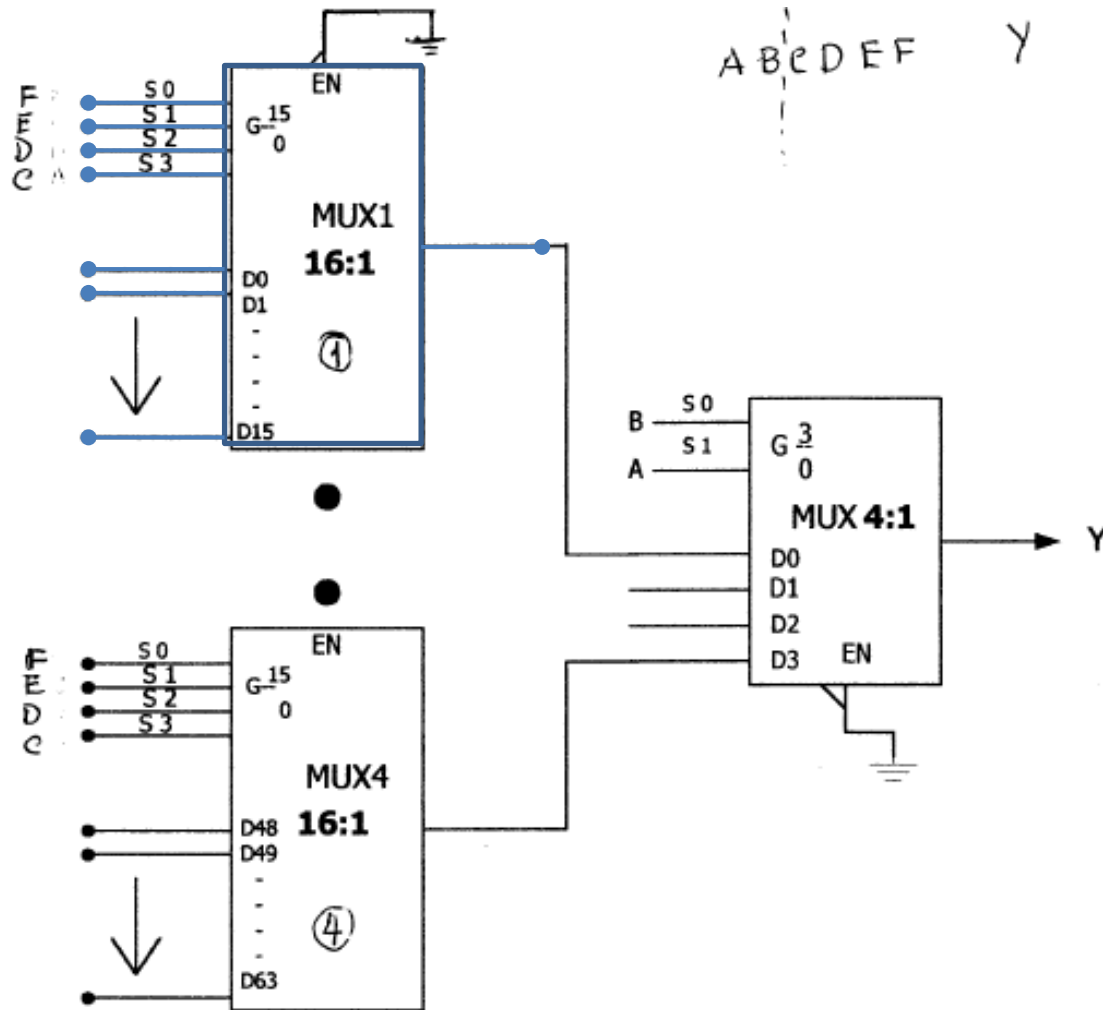

Decoders

 
- The decoder is the circuit that gives the output n to be H .
- Where n is a number corresponding to the input code.
- For example, input = 1101 will allow H to come out from output 13.
- Called DX $n:2^n$
- The largest size in the IC format is DX 4:16 (24-pin IC).
- Applications:
- 24 Device (ON/OFF) selection.




Decoder Expansion

- Decoder Expansion can be done by using n 4:16 decoders, which provides $16n$ outputs.
- However, these individual decoders are required to be selected by another $m:n$ decoder, where $2m \geq n$.
- For example: A 6:64 decoder
- is made by using FOUR DX 4:16 decoders (4-bit code);
- In conjunction with A DX 2:4 Decoder (2-bit code) to select one from four to be activated.
- Example: To decode 25 = 01 1001
 6bit code = AB CDEF
 Connect to IC139 IC154

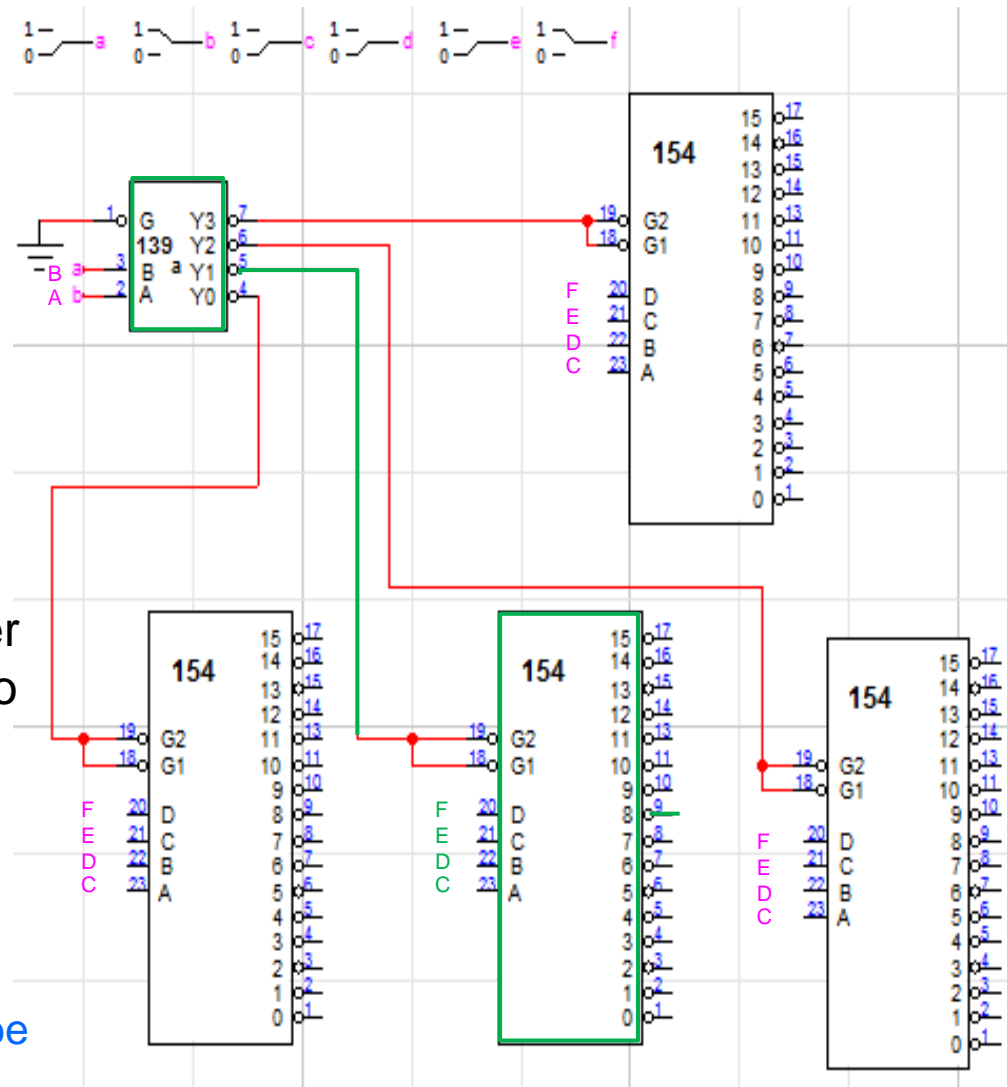Then the output 9 of the second IC154 will be activated to L.



Read Only Memory: ROM

 


ROM $m:n$

- ROM $m:n$
- The m -line input will point the address $0-2^m - 1$;
- The individual address has a n -bit data.
- Which is permanent programmed values.
- The easy structure of ROM is in the next page.

The Structure of ROM Size $2^3 \times 4$

- ROM has the structure of the diode array
- Input the address (3bit);
- The activated address will produce 0 at its output (active LOW):
- The data will be read out by:
- With Diode: $D = 0$;
- Without Diode: $D = 1$;
- Initially, the ROM would have ALL diodes;
- The ROM can be programmed by exploding the diode(s) in the array.
- Example: Input = $101_2 = 5$
- Address 5 = 0;
- Data out = 1100_2
- These data be used to
- Turn ON/OFF 4 devices in the same time;
- Drive the 7-Segment LED;
- Etc.

 

ROM Implication

- To design a ROM that provides the following signal outputs:

$$Y_1 = F(A, B, C) = \sum m(1, 3, 4, 6) \quad Y_2 = F(A, B, C) = \sum m(2, 4, 5, 7)$$

$$Y_3 = F(A, B, C) = \sum m(0, 1, 5, 7) \quad Y_4 = F(A, B, C) = \sum m(1, 2, 3, 4)$$

- There are three variable inputs, which produces a code of values 0 - 7
- Use the corresponding value code to generate the outputs $Y_1 - Y_4$.

