 



7 REGISTERS

Registers

- A register is a circuit that receives and maintains the data;
- And/or transfers the data to another circuit.
- May be called a memory circuit;
- Made from a number of D Flip-flops;
- Memory Capacity of n bits requires n Flip-flops.



Set to 1

 

Set to 0

Register Types

Categorized by the method of data import/export:


- Serial Data Transfer: Need a number of clocks to trigger the data transfer.
- Parallel Data Transfer: Need only **one** clock to trigger the transfer.




(a) Serial in/shift right/serial out




(b) Serial in/shift left/serial out

 


(c) Parallel in/serial out

 


(d) Serial in/parallel out

 

(e) Parallel in/parallel out

 

(f) Rotate right

 

(g) Rotate left

Shift Register

Shift Register transfers data (bit by bit) in serial both input and output;

Categorized by orientation of the data transfer:


- Shift-Right Register (SRR)

- data is imported from the left.
- Keep transferring to the right until it reaches the end of the data.


- Shift-Left Register (SLR)

- input data from the right.
- Keep transferring to the left until it reaches the end of the data.


Serial-In/Serial-Out Shift Register

 



Serial-In/Serial-Out Shift Register

 

Serial-In/Serial-Out Shift Register

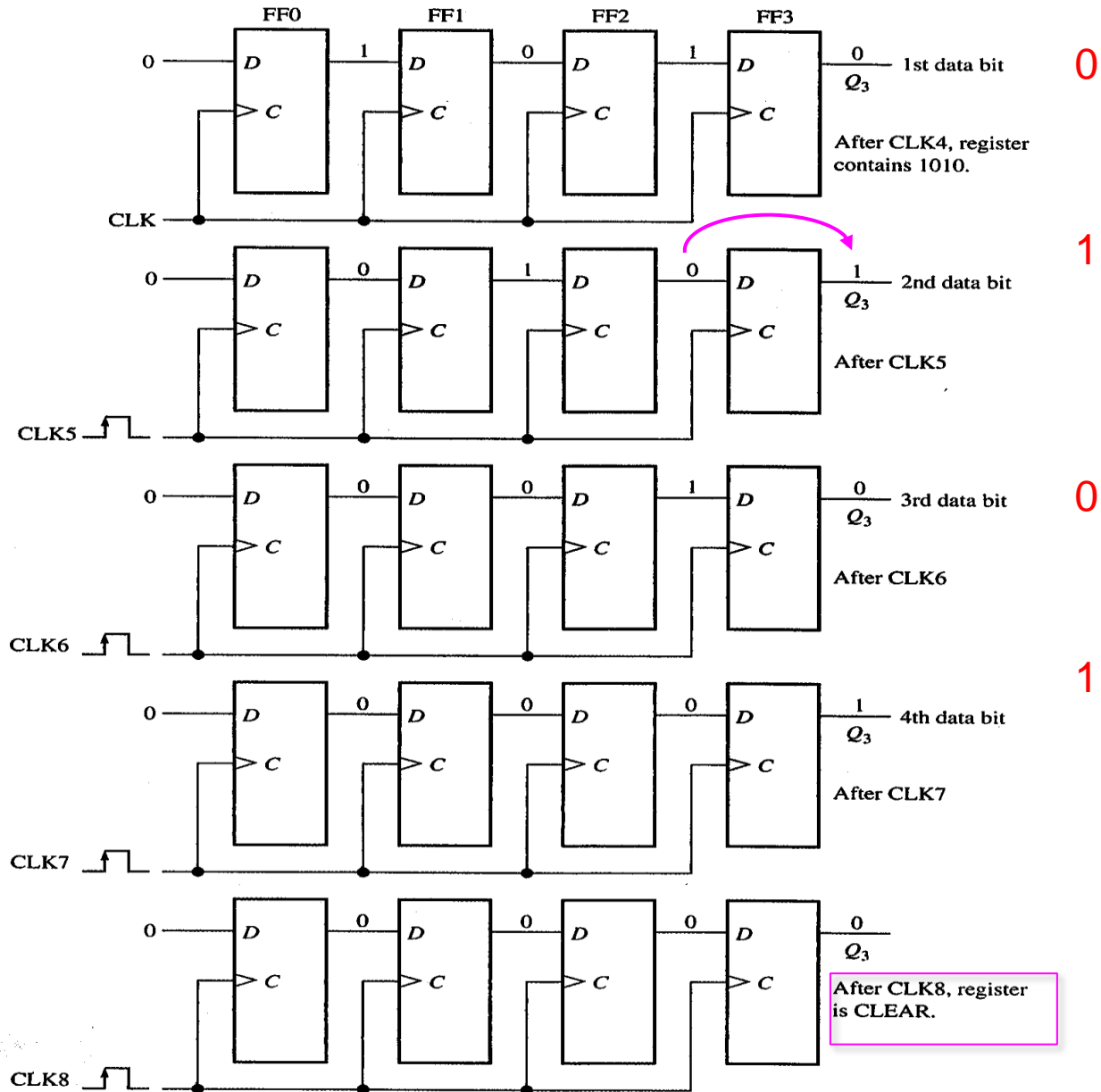


5-Bit Shift Register: Timing Diagram

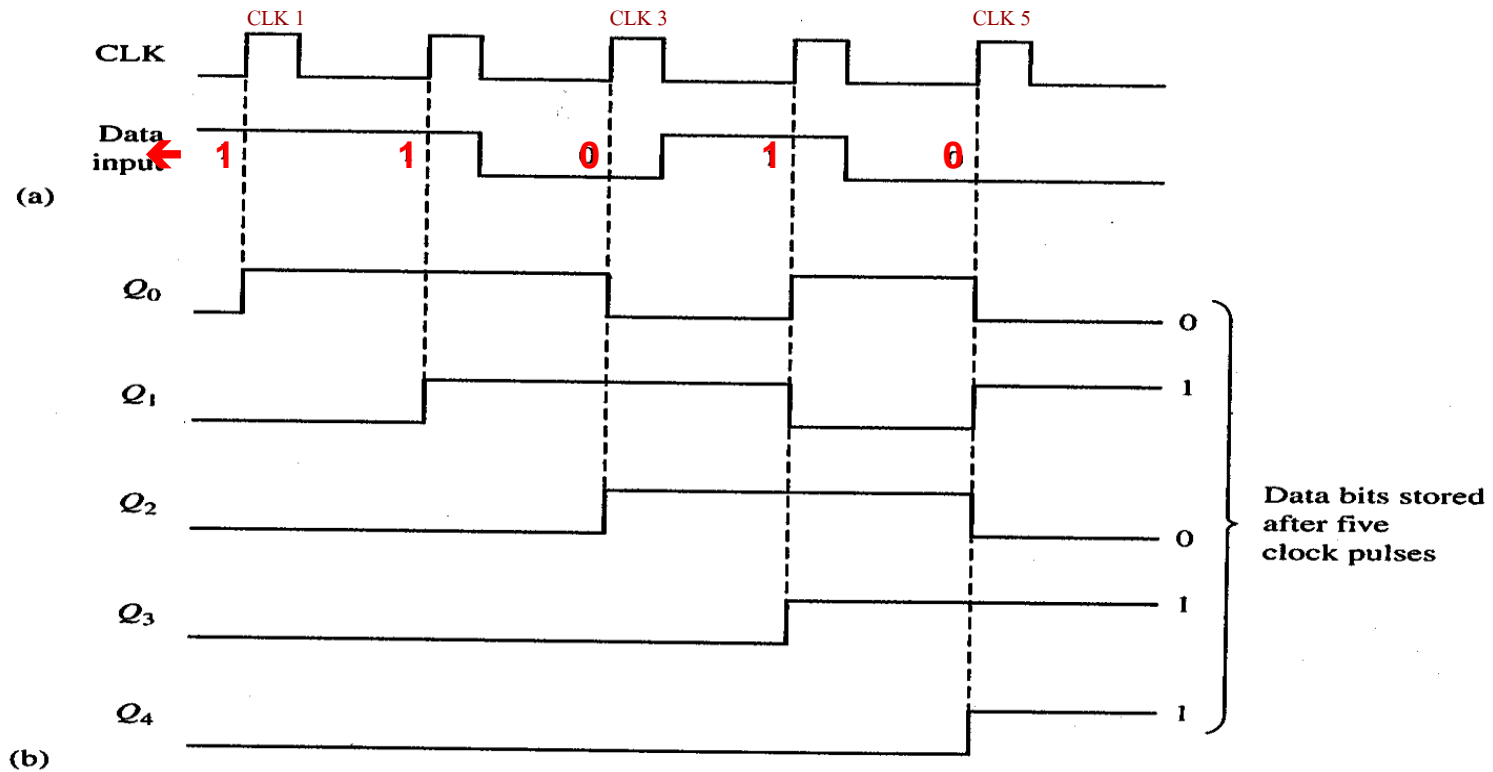 


Serial-In Parallel-Out (SIPO) Register

 - SIPO is a register that imports data in serial (the MSB first) and transfer data out parallelly (from the outputs of all Flip-Flops)
- Import the data of n bits requires n clocks;
- Once the all bits already Imported, the n -bit data will appear immediately at the output of individual Flip-flops.






Block Diagram

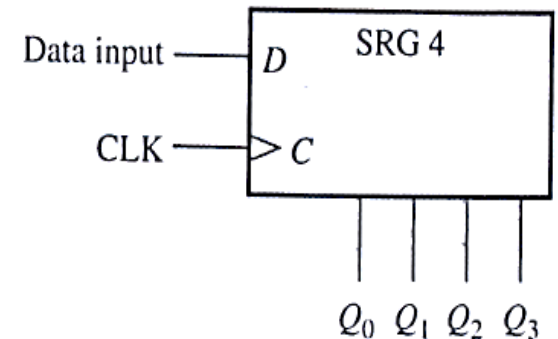


Symbol

   Serial-In Parallel-Out Register: Timing Diagram





Parallel-In Serial-Out (PISO) Shift Register

- PISO is a register with multiple inputs of n Flip-Flops;
- Requires a control signal (SHIFT/LOAD) to indicate loading or shifting the data;
- **For the data loading state:** the n -bit data will be imported to be at the individual outputs of the Flip-Flops **by 1 clocks**;
- **For the data shifting state:** the n -bit data will be shifted to the right of the individual Flip-Flops **by $(n - 1)$ clocks**;

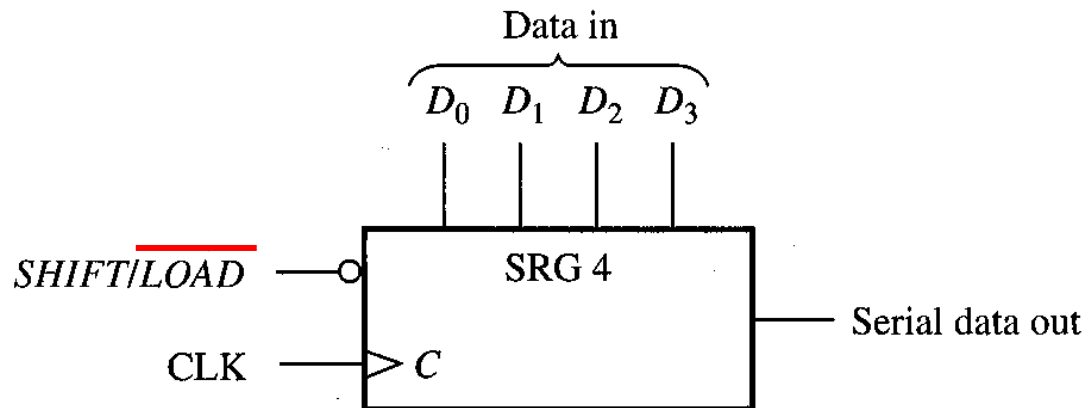


- If SHIFT/LOAD = 0, G_1 to G_3 are active:
 - ➔ the input data will be imported into the parallel register **by 1 clocks**.
- If SHIFT/LOAD = 1, G_4 to G_6 are active:
 - ➔ the data will be shifted bit by bit to the right **by (n) clocks**.

Parallel-In Serial-Out Shift Register

 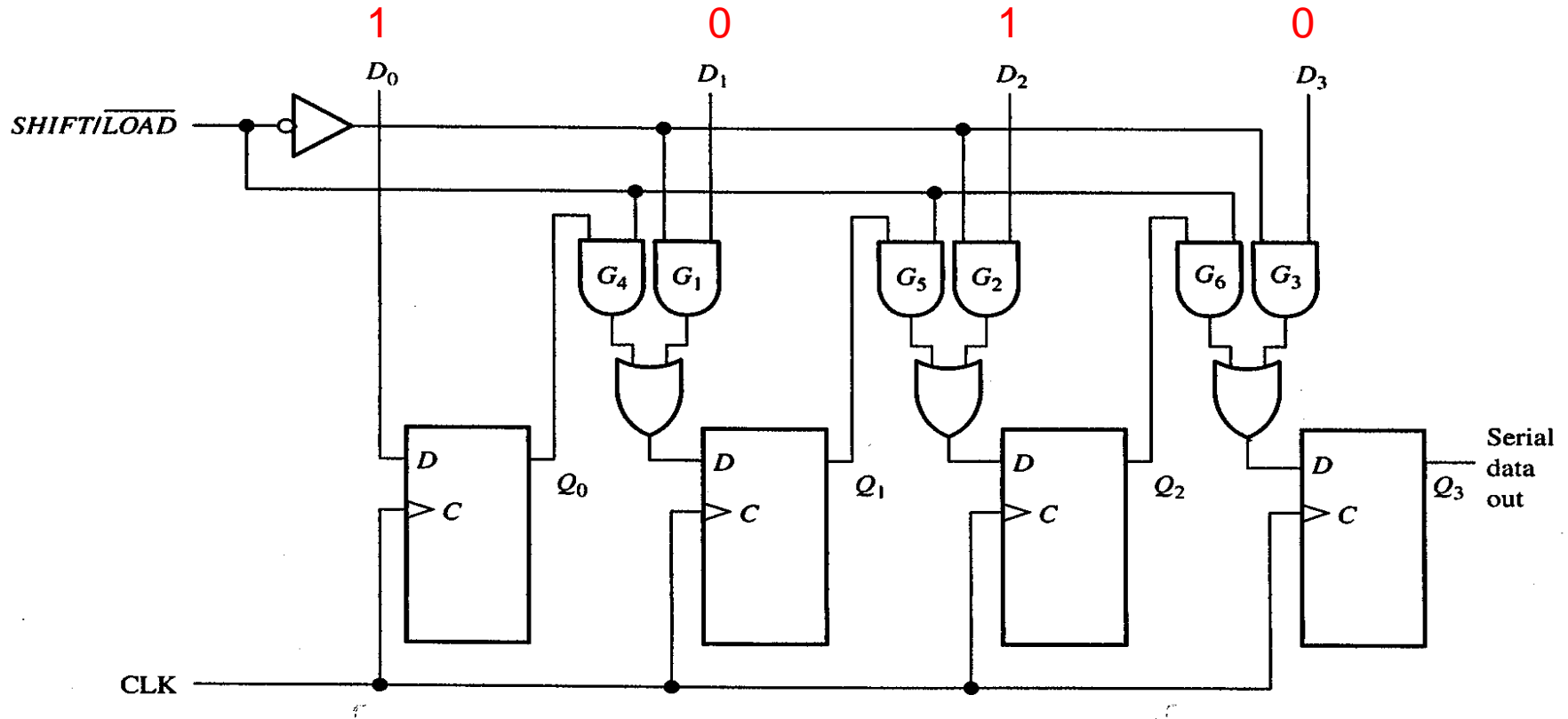


Parallel-In/Parallel-Out (PIPO) Register

 



- The input data will be imported into the parallel register **by 1 clocks**.
- And ready to be exported for another register.

Bidirectional Shift Register

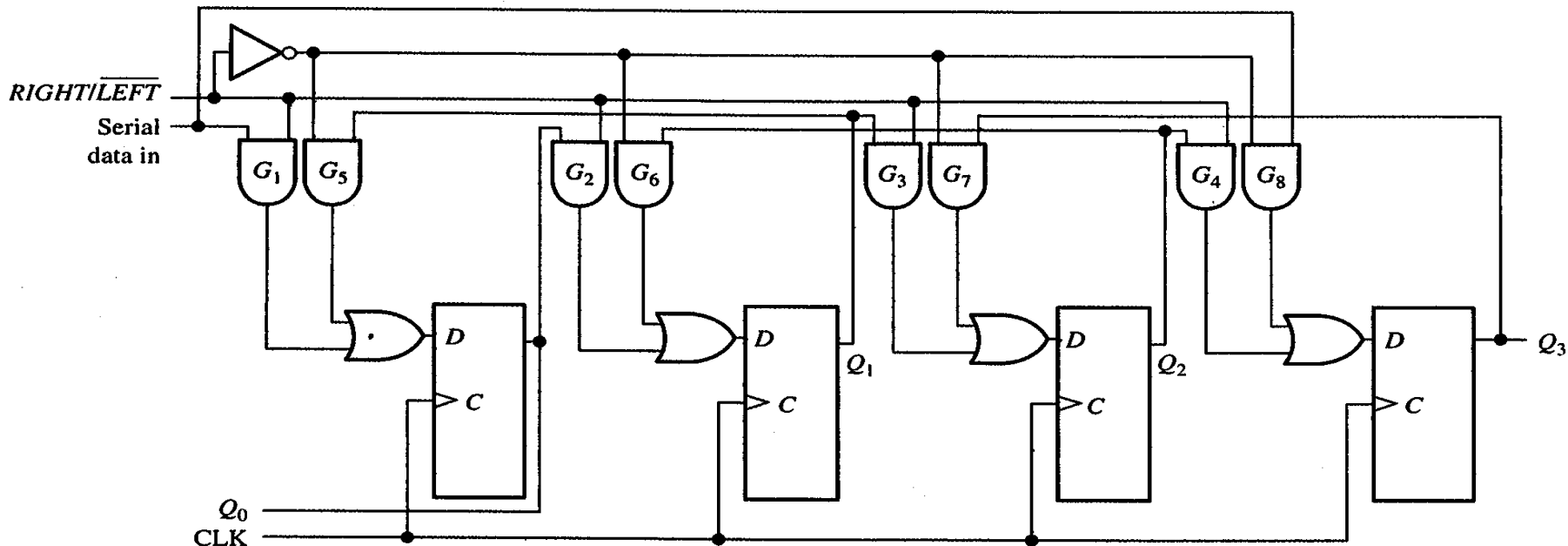- If need to shift the data in the register either to the right or to the left.
- By inserting a gate circuit to controls the direction of shifting;
- to control by the RIGHT/LEFT pin:
 - If the pin is 1, the data shifting is to the right;
 - If the pin is 0, the data shifting is to the right left.




Bidirectional Shift Register

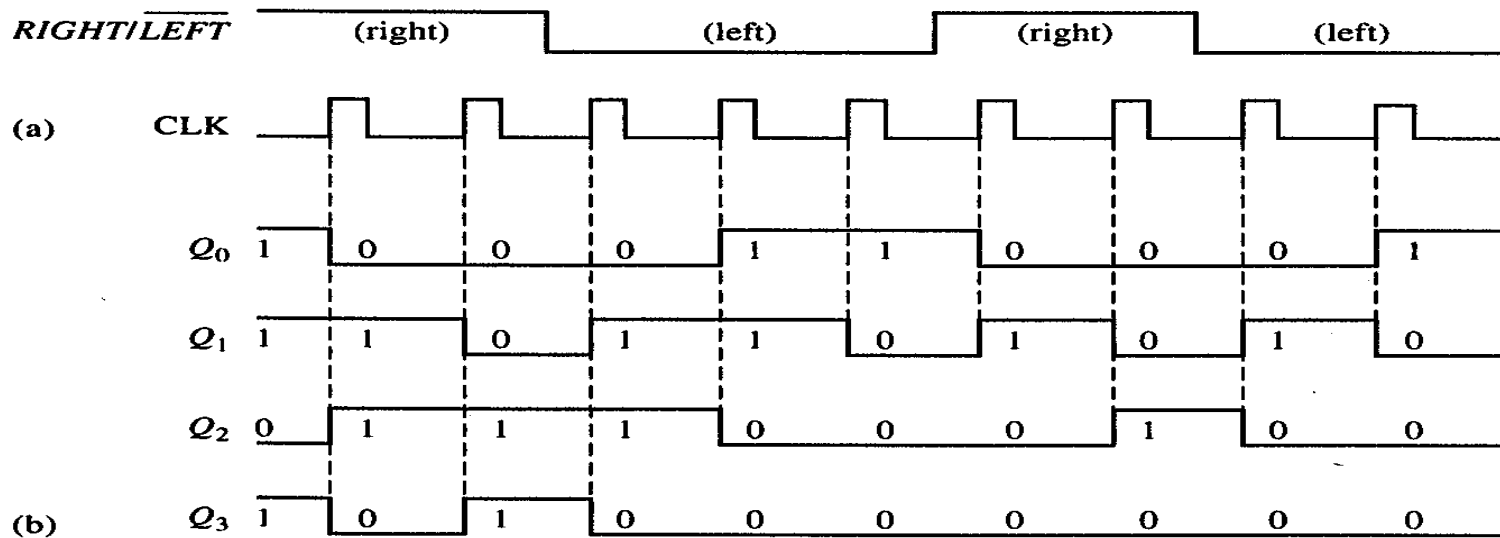 



Parallel-In Serial-Out (PISO) Shift Register

Typically, we use D Flip-Flop to create registers.


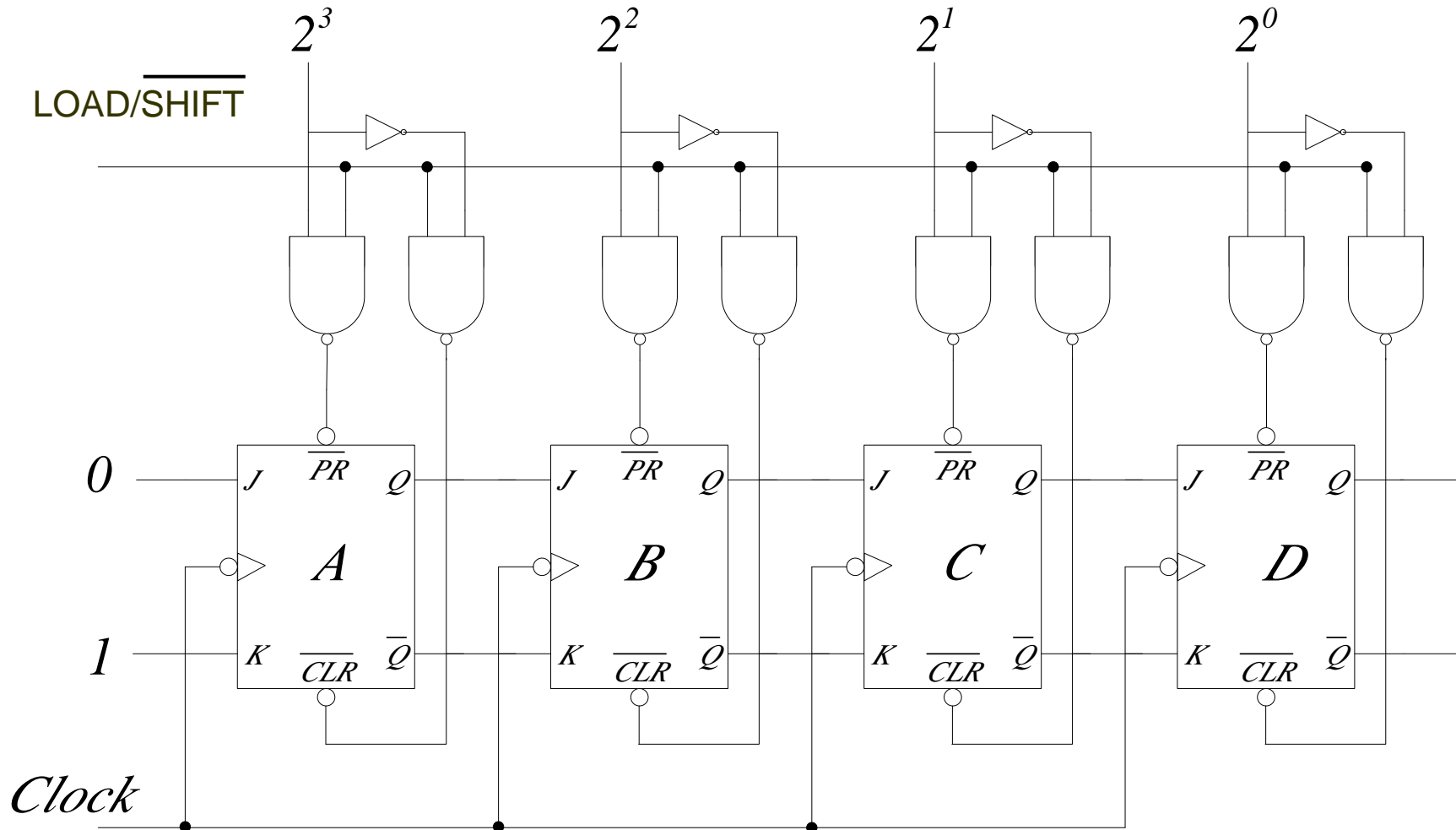
However, we may use JK Flip-Flops with Preset and Clear too.




Parallel-In Serial-Out Shift Register

  

Parallel-In Serial-Out Shift Register

  


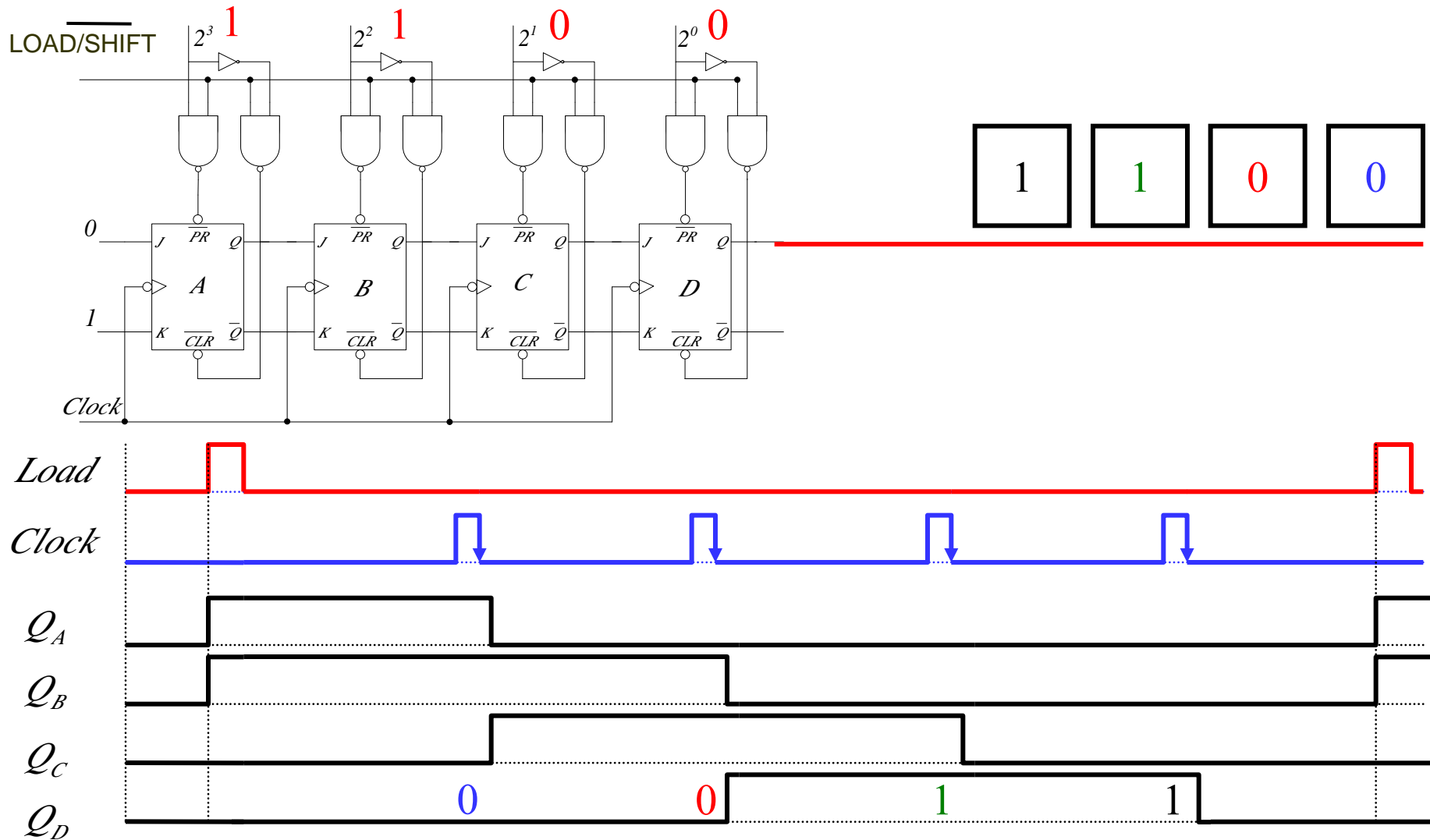Parallel-In Serial-Out (PISO) Shift Register




Shift-in Shift-around Register

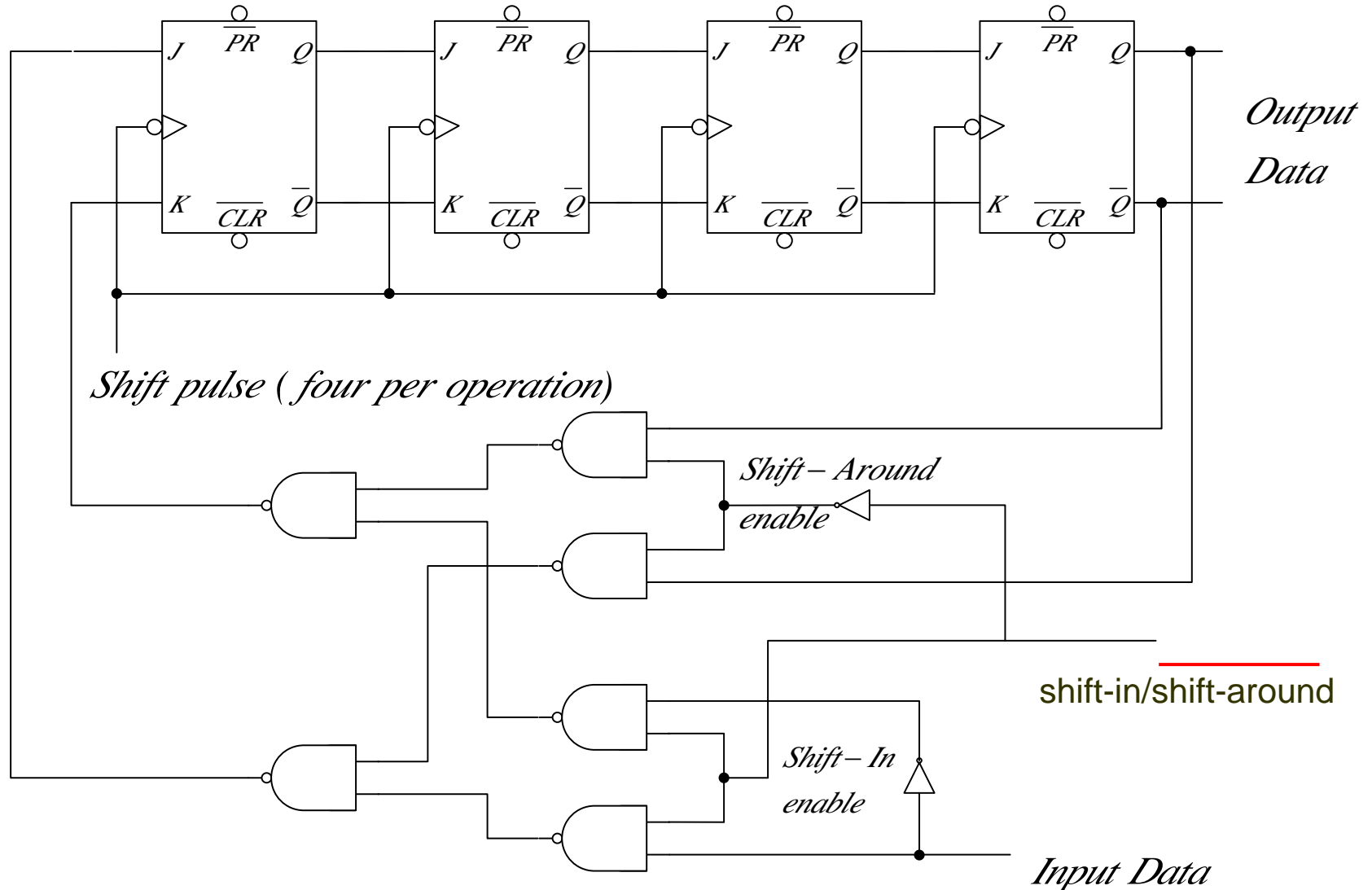
- This register can import the data from outside (shift-in) or from itself (shift-around).
- Need a control signal for gating the data either from outside or from itself.



Shift-in Shift-around Register

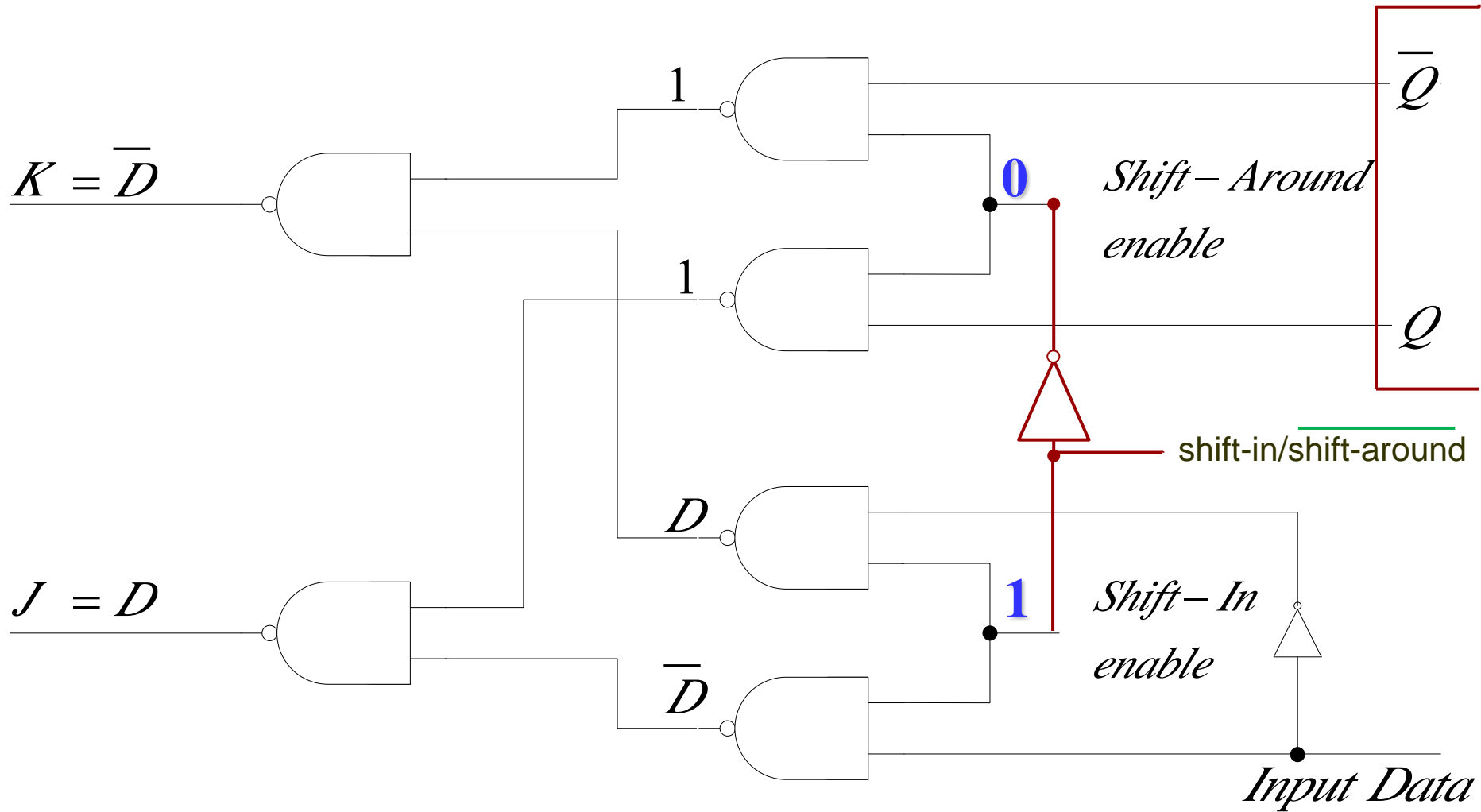

Shift-in Shift-around Register

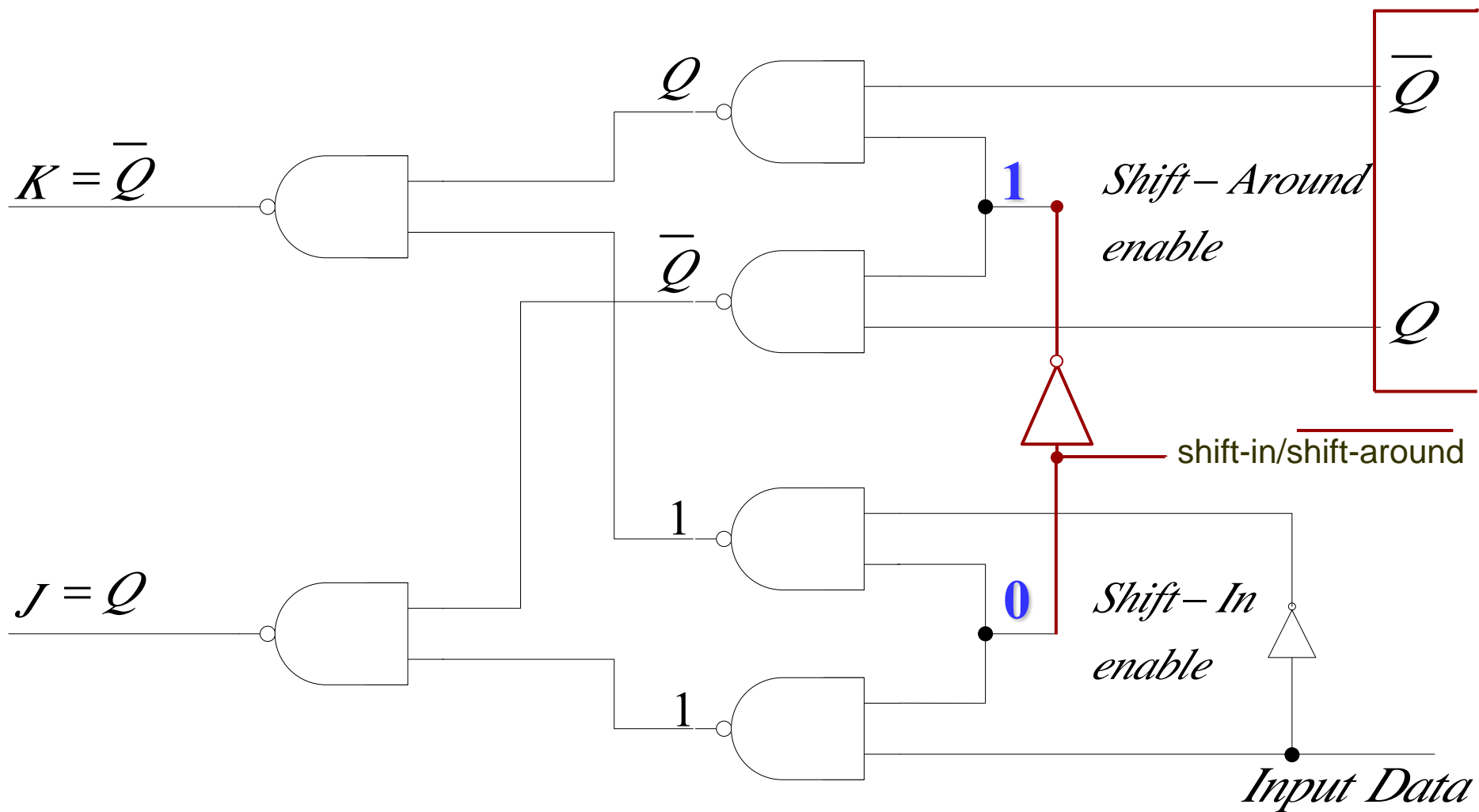


Shift Register Counter

- Shift Register Counter is a Shift-around register with feeding the last output back to the first input.
- This will create a specific sequence of data,
- And be called as a Counter i.e. Shift Register Counter.
- There are 2 types of Shift Register Counter:
 - ❑ Ring Counter: Feed the last output Q to the first input D
 - ❑ Johnson Counter : Feed the last invert output \overline{Q} to the first input D

Ring Counter

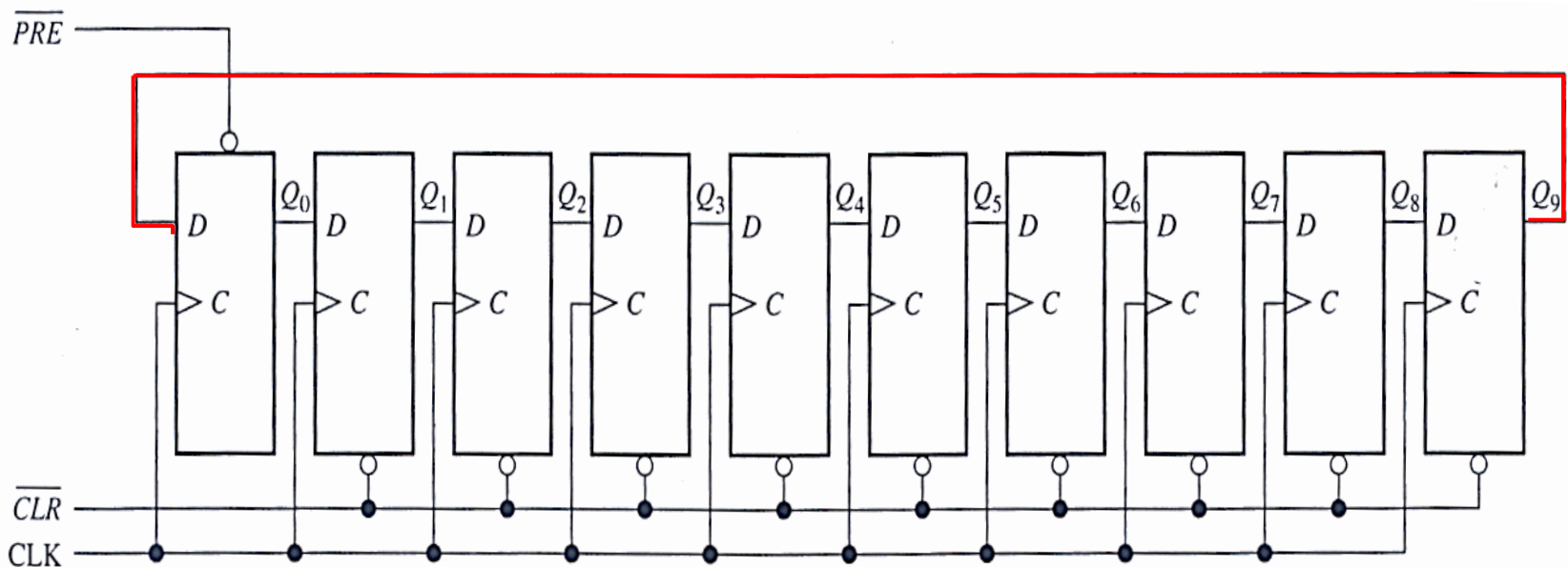- The counter that uses n Flip-Flops to count n states;
- It will repeat the specific number for every n cycles;
- Therefore, do not need gates to help process the output at all;
- For example, for 10-bit Ring Counter, the circuit will repeat its initial number in every 10 clock cycles.




Ring Counter

[illegible]


Ring Counter

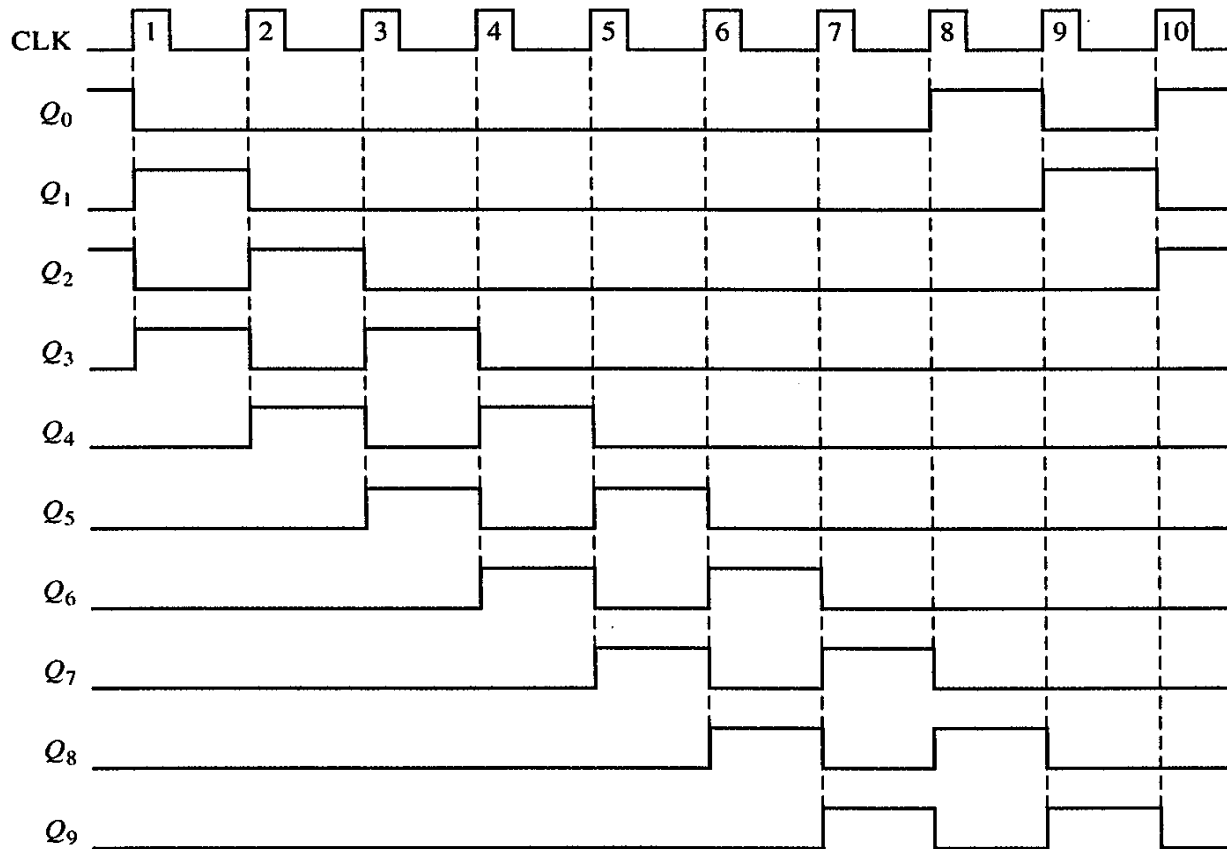10-bit Ring Counter with an initial value of 00000000101




Shift Register: Applications

- Time Delay

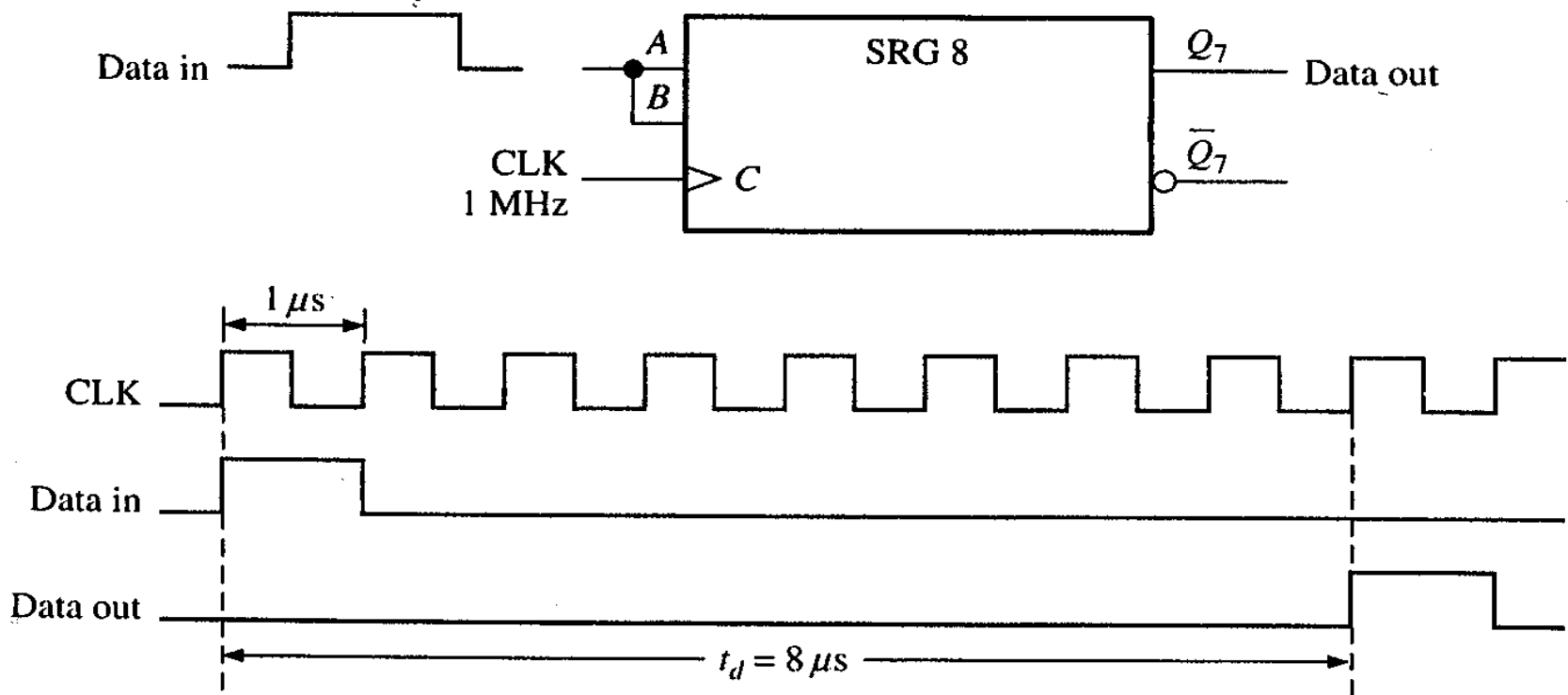

Shift Register: Applications

 
Example: Calculate the time delay when the clock runs at 500 kHz.



* Data shifts from Q_0 toward Q_7 .


The time delay = $1/f = 1/(500 \times 10^3) = 2 \times 10^{-6}$ second = $2 \mu s$.

Shift Register: Applications

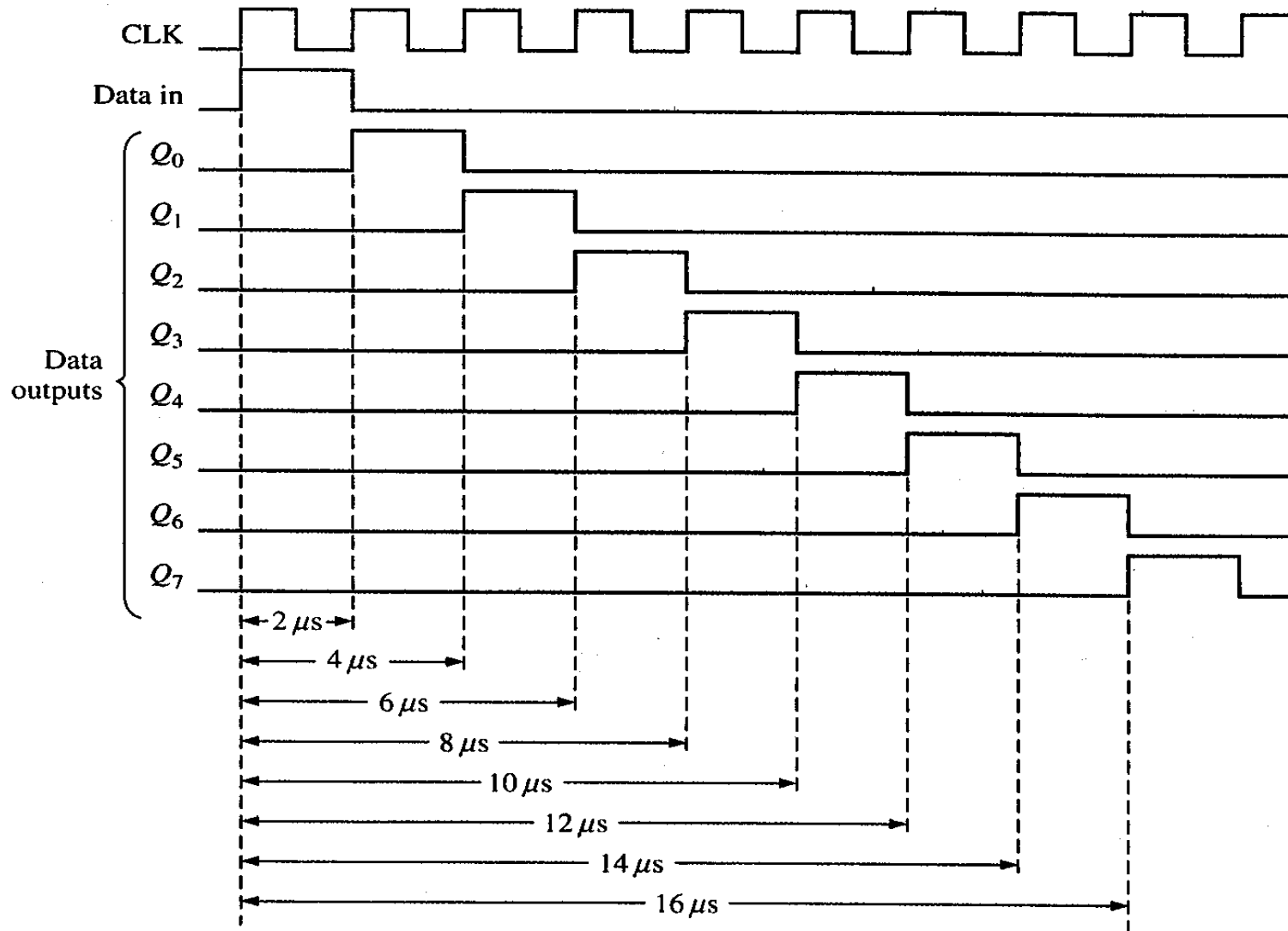

Shift Register: Applications

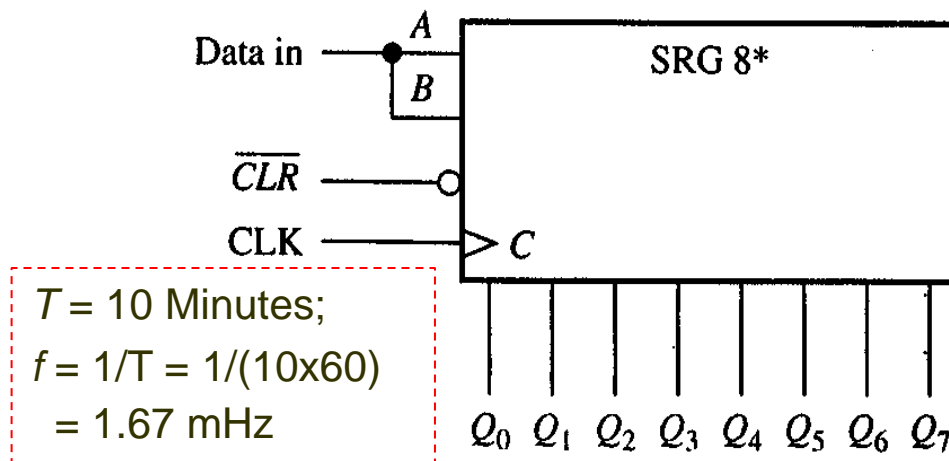
Example: Find the clock that provides 10 minutes duration step for the morning routine below.



- Q_0 : Turn-off the air-conditioner;
- Q_1 : Turn-on heater for the electric shower;
- Q_2 : Alarm to wake up;
- Q_3 : Boil the water pot for tea/coffee;
- Q_7 : Turn off the circuit braker.

Johnson Counter

4-bit Johnson Counter

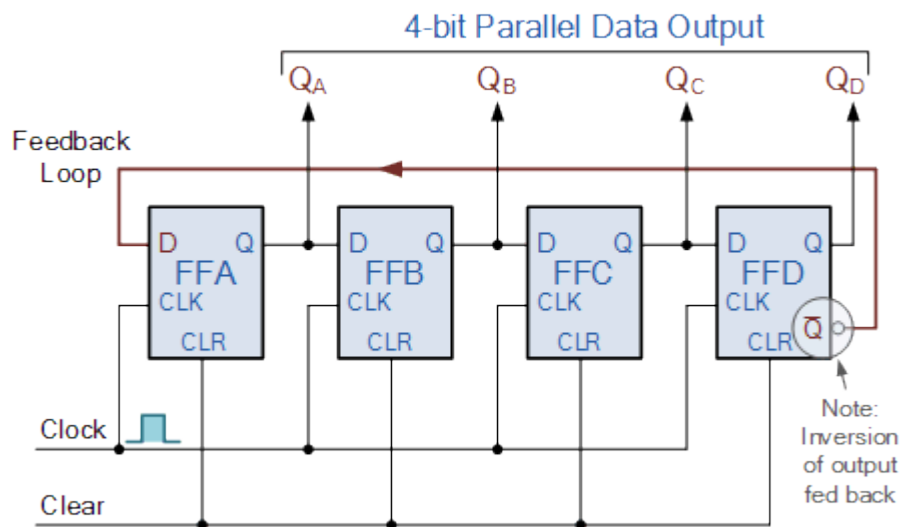

Truth Table

| Clock Pulse No | FFA | FFB | FFC | FFD |
|----------------|-----|-----|-----|-----|
| 0 | 0 | 0 | 0 | 0 |
| 1 | 1 | 0 | 0 | 0 |
| 2 | 1 | 1 | 0 | 0 |
| 3 | 1 | 1 | 1 | 0 |
| 4 | 1 | 1 | 1 | 1 |
| 5 | 0 | 1 | 1 | 1 |
| 6 | 0 | 0 | 1 | 1 |
| 7 | 0 | 0 | 0 | 1 |

- The counter that uses n Flip-Flops to generate $2n$ states;
- It will repeat its initial number for every $2n$ cycles;