

Name:.....Student ID Sent by 7/3/2024

Find the state table, state diagram and timing diagram for the circuit below,
when the input $x = 001011010$ and initial state of 10.

