
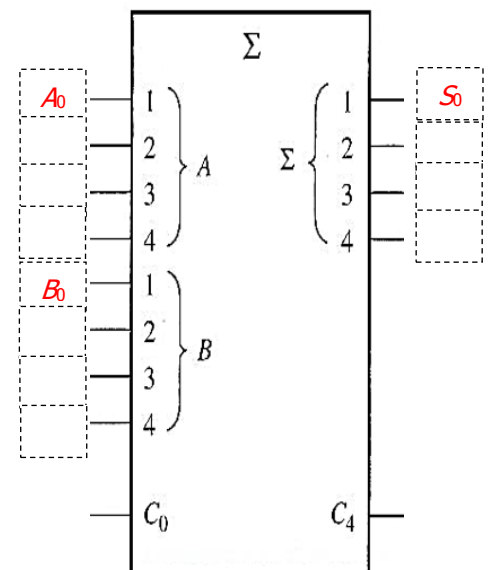


1) Fill the EVEN parity bit in the table below.

Data	Even Parity Bit will be:
00100	
01011	
0110101	
1010101	
11010100	
1010110101	

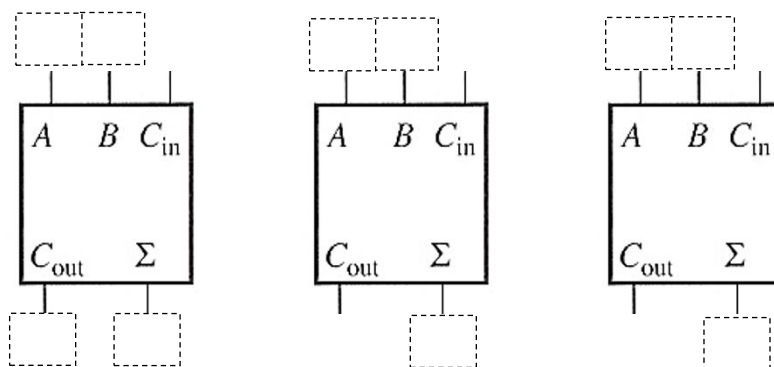2) Design 7-bit Adder Circuit using a 4-bit adder and 3 Full Adders below. Complete the circuit connection (drawing connecting lines) and fill all the signals A_1 - A_6 , B_1 - B_6 and S_1 - S_7 .



$$\begin{array}{r}
 A_6 \ A_5 \ A_4 \ A_3 \ A_2 \ A_1 \ A_0 \\
 B_6 \ B_5 \ B_4 \ B_3 \ B_2 \ B_1 \ B_0 \\
 \hline
 S_7 \ S_6 \ S_5 \ S_4 \ S_3 \ S_2 \ S_1 \ S_0
 \end{array}
 +$$

3) Convert the last 2 digits of your ID to a binary B. Then Design the decoder to indicate this binary B.

4) Plot the pulse diagram for the signal $Y = (AB + C) \cdot B$

