

6 Flip-Flop

Devices Used in Digital Systems

Devices used in digital systems:

❑ Logical Devices:

- Gate circuits
- Combination circuits

❑ Memory Devices:

- Flip-flops
- Sequential Circuits


Flip-Flop

Flip-Flop

- is a device with a pair of inputs, and one output Q with its inverting Q' .
- We can program the output Q to be either 0 or 1;
- By activating the pair of inputs;
- The output Q could be hold its state until the new inputs are activated;

Flip-Flop can be used to make:

 - Registers;
- Counters;
- Sequential Circuits.



Flip-Flop: Types

Flip-Flop may be categorized by following characteristics


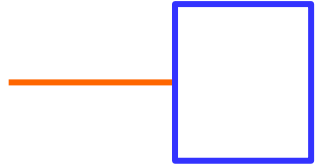

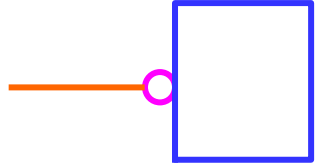

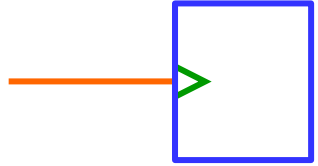
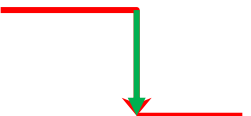
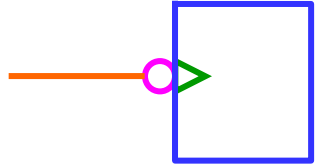
- Controlling signal can be divided into

- Flip-Flop with Clock and
- Flip-Flop without Clock.


- Input activation can be divided into 6 types:

- SR Flip-Flop
- JK Flip-Flop
- D (Data) Flip-Flop
- T (Toggle) Flip-Flop
- Master/Slave Flip-Flop
- Preset and Clear Flip-Flop

Flip-Flop Types: Clock Activation


Types of Clock Activation		Symbols
	Positive Level	
	Negative Level	
	Positive Edge Triggered	
	Negative Edge Triggered	

Set-Reset Flip-Flop

 

SR Flip-Flop

- There are 2 inputs: **Reset (R)** and **Set (S)**.
- **Setting** is to make the output to 1, and
- **Resetting** is to make the output to 0.
- **Setting** can get by activating the inputs: $S = 1$ and $R = 0$.
- **Resetting** can get by activating the inputs: $S = 0$ and $R = 1$.
- When **BOTH** inputs are **not** activated: $S = 0$ and $R = 0$, the output will remain its previous logic, or **NO CHANGE**.
- When **BOTH** inputs are **activated**: $S = 1$ and $R = 1$, the output will be ambiguous, so **UNUSEABLE**.

 


Set-Reset Flip-Flop: Excitation Table

Input		Output		Status
<i>SET</i>	<i>RESET</i>	Q	\overline{Q}	
0	0	Q	\overline{Q}	Unchanged State
0	1	0	1	Reset State
1	0	1	0	Set State
1	1			Unused State



Set-Reset Flip-Flop: Configuration

 It may be constructed from either 2 NAND gates or 2 NOR gates with one's output feeding to the other input;




Let's see what happens when applying all possible inputs:

Crossed NAND Set-Reset Flip-Flop [1]

  


<i>A</i>	<i>B</i>	$\overline{A \cdot B}$
0	0	1
0	1	1
1	0	1
1	1	0

Crossed NAND Set-Reset Flip-Flop [2]

 


No Change

 

No Change

<i>A</i>	<i>B</i>	$\overline{A \cdot B}$
0	0	1
0	1	1
1	0	1
1	1	0

Crossed NAND Set-Reset Flip-Flop [3]

 

A	B	Upper
0	0	1
0	1	1
1	0	0
1	1	Q

Activated by 0

Unused

Set


Reset

Unchanged
(Previous case)


Crossed NAND Set-Reset Flip-Flop [4]

SET	$RESET$	\overline{SET}	\overline{RESET}	Q	\overline{Q}	
1	1	0	0	1	1	Unused State
1	0	0	1	1	0	Set State
0	1	1	0	0	1	Reset State
0	0	1	1	Q	\overline{Q}	Unchanged State


Crossed NAND Set-Reset Flip-Flop [5]

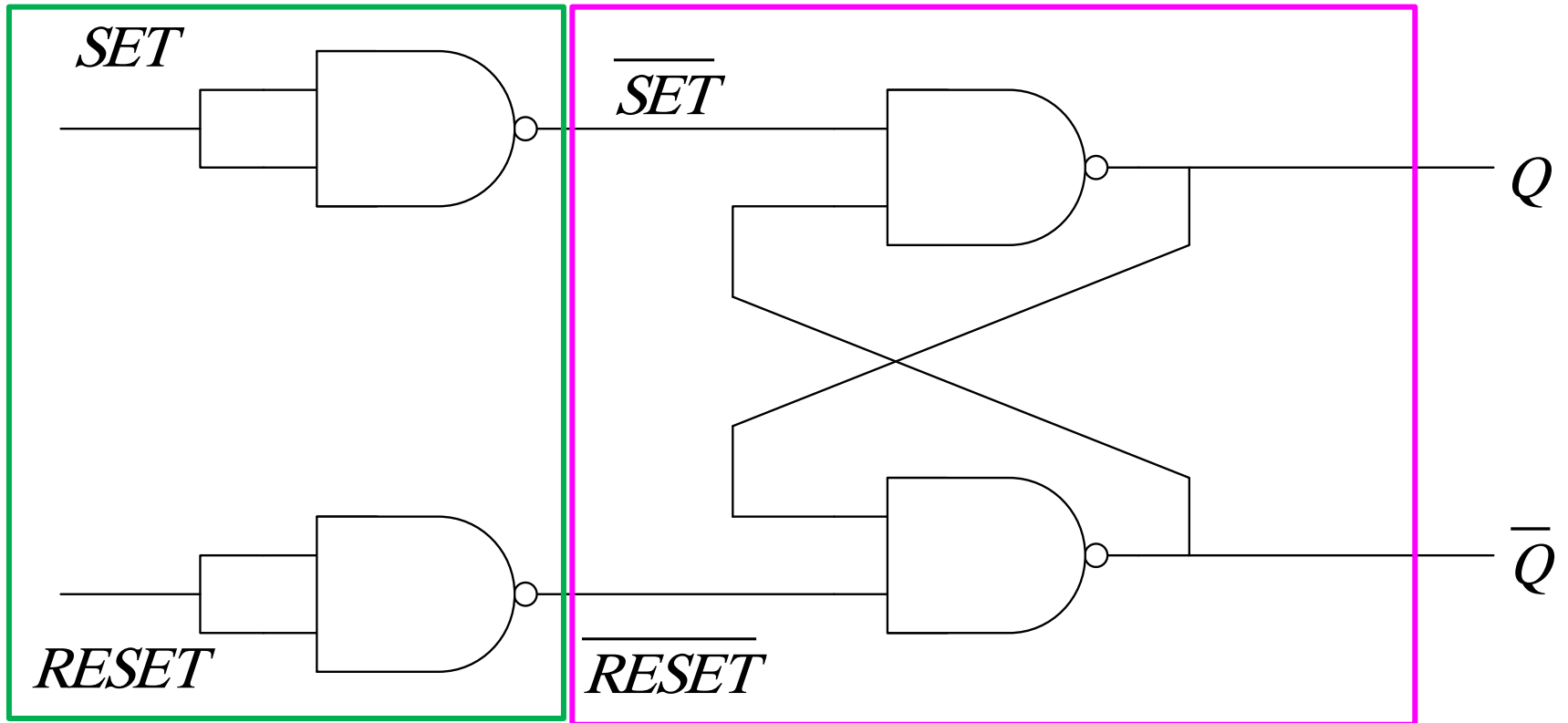



Crossed NAND Set-Reset Flip-Flop [6]

 

Crossed NOR Set-Reset Flip-Flop [1]


 


Crossed NOR Set-Reset Flip-Flop [2]

  


A	B	$\overline{A+B}$
0	0	1
0	1	0
1	0	0
1	1	0

Crossed NOR Set-Reset Flip-Flop [3]

  


A	B	$\overline{A+B}$
0	0	1
0	1	0
1	0	0
1	1	0

Crossed NOR Set-Reset Flip-Flop [4]

 


A	B	Upper
0	0	Q
0	1	1
1	0	0
1	1	0

 


Crossed NOR Set-Reset Flip-Flop [5]

Set	Reset	Q	\overline{Q}	State
1	1	0	0	Unused
1	0	1	0	Set
0	1	0	1	Reset
0	0	Q	\overline{Q}	Unchanged


Crossed NOR Set-Reset Flip-Flop [6]

 

Waveform Crossed SR Flip-Flop

 


Gated Set-Reset Flip-Flop

 


- Sometimes called Clocked SR Flip-Flop.
- With a clock used to activate the Flip-Flop operation.
- When no clock,
 - The flip floppy will not work,
 - The output value will maintain the previous logic state.
- Presenting with a clock,
 - It would operate as the normal SR Flip-Flop;
 - Depends on the activation at S and R.


Gated Set-Reset Flip-Flop

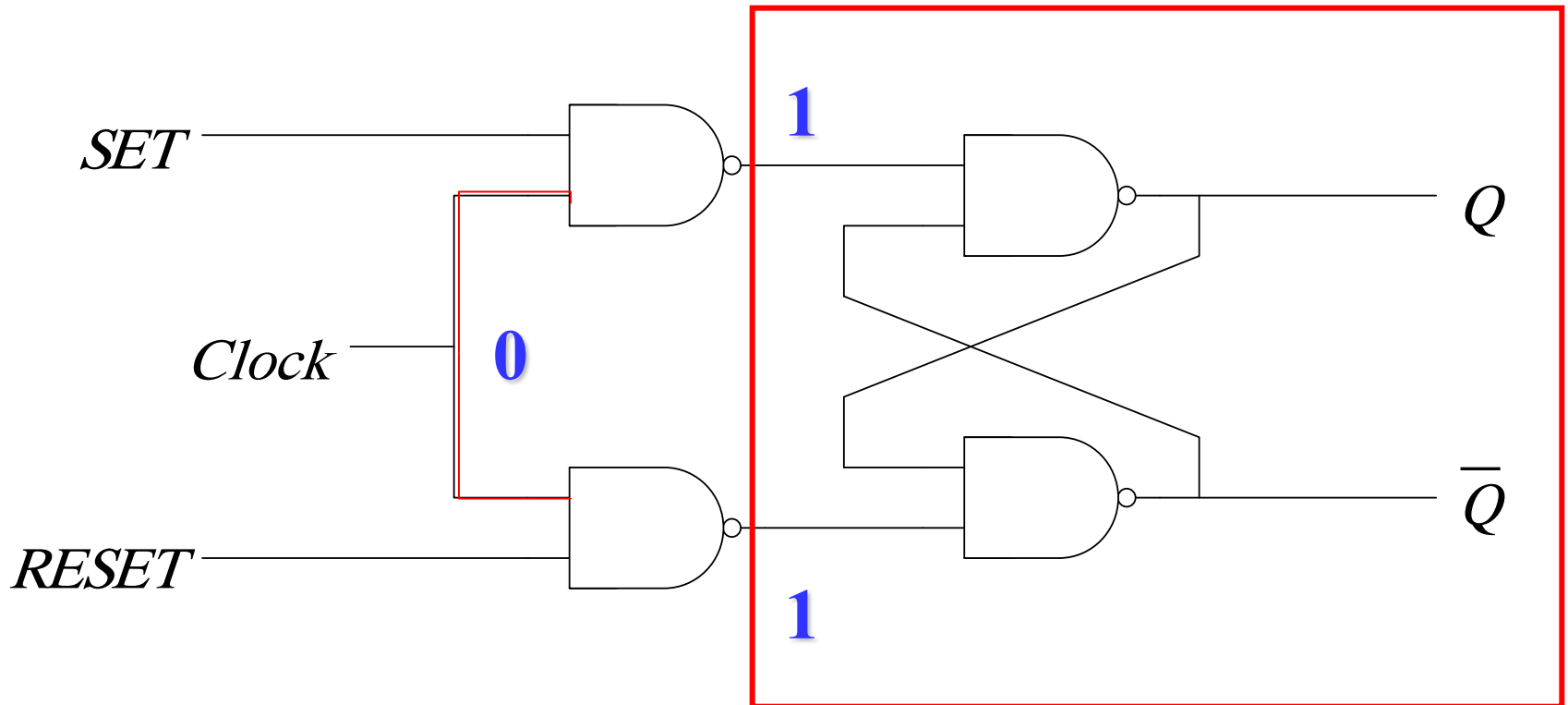



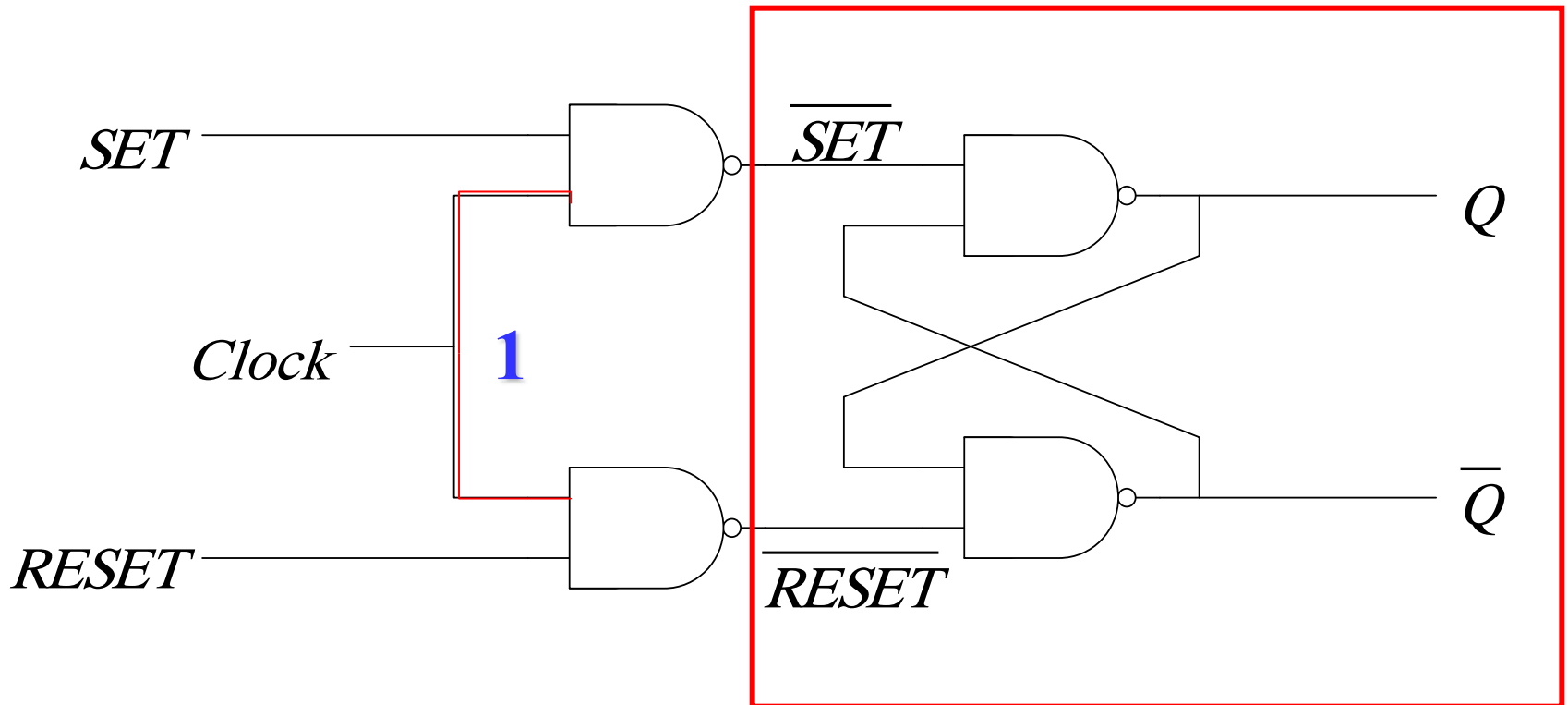

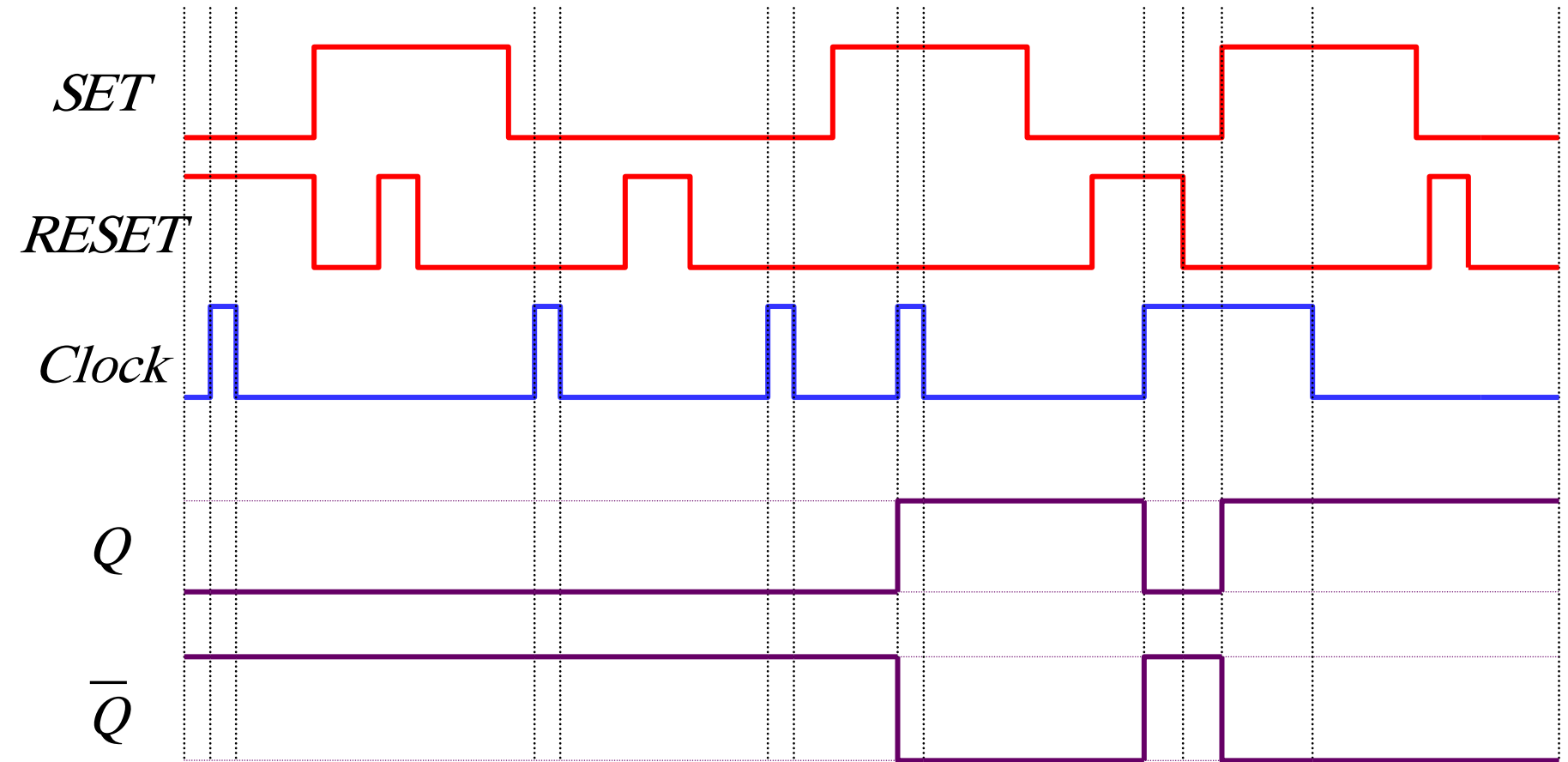


Gated Set-Reset Flip-Flop



Gated Set-Reset Flip-Flop



Gated Set-Reset Flip-Flop




<i>Clock</i>	<i>SET</i>	<i>RESET</i>	Q	\bar{Q}	Status
	0	0	Q	\bar{Q}	Unchanged
	0	1	Q	\bar{Q}	
	1	0	Q	\bar{Q}	
	1	1	Q	\bar{Q}	
	0	0	Q	\bar{Q}	
	0	1	0	1	Reset
	1	0	1	0	Set
	1	1	1	1	Unused

JK Flip-Flop



- JK Flip-Flop is the flip flop modified from the SR Flip-Flop.
- Modify the case for both inputs activated or **the unused case** in the SR Flip-Flop.
- The JK Flip-Flop circuit has 2 inputs: J and K .
- By comparing the input signals J as S , and K as R .
- In the case of the modified state with the inputs of $J = 1$ and $K = 1$.
- Call the state as the **Toggle or Complement** state.
- The operation will give the **complemented** output i.e.
- If the present $Q = 0$, it will change to the new state of $Q = 1$;
- if the present $Q = 1$, it will change to the new state of $Q = 0$.

JK Flip-Flop


- In practice, The JK Flip-Flop will have 2 additional control inputs:
 - Preset (PR) and
 - Clear (CLR)
- Which can control the operation of the Flip-Flop
 - independent to the activation at the input J , K and Clock;
 - Both controlling pins are 'active low'.
- The operation table is presented below:

<u>Preset</u>	<u>Clear</u>	J	K	Clk	Q	\bar{Q}	State
0	1	X	X	X	1	0	Set
1	0	X	X	X	0	1	Reset
0	0	X	X	X	1	1	Unused State
1	1	0	1		0	1	
1	1	1	0		1	0	
1	1	0	0	X	Q	\bar{Q}	Unchanged
1	1	1	1		Complemented		Toggle


JK Flip-Flop

  

JK Flip-Flop


 


D (Data) Flip-Flop

 


- is a flip-flop with only **one** input D ;
- Work with **the controlling signal** – the Clock signal.
- When the circuit is triggered by a clock, the input D would be passed to output:
- when $D = 0$ gives $Q = 0$;
- And if $D = 1$, then $Q = 1$.
- Therefore, D Flip-Flops is used to memorize the input values..
- This principle applies to memorize the desired information.


D (Data) Flip-Flop

  

D Flip-Flop using **ONLY** NOR Gates

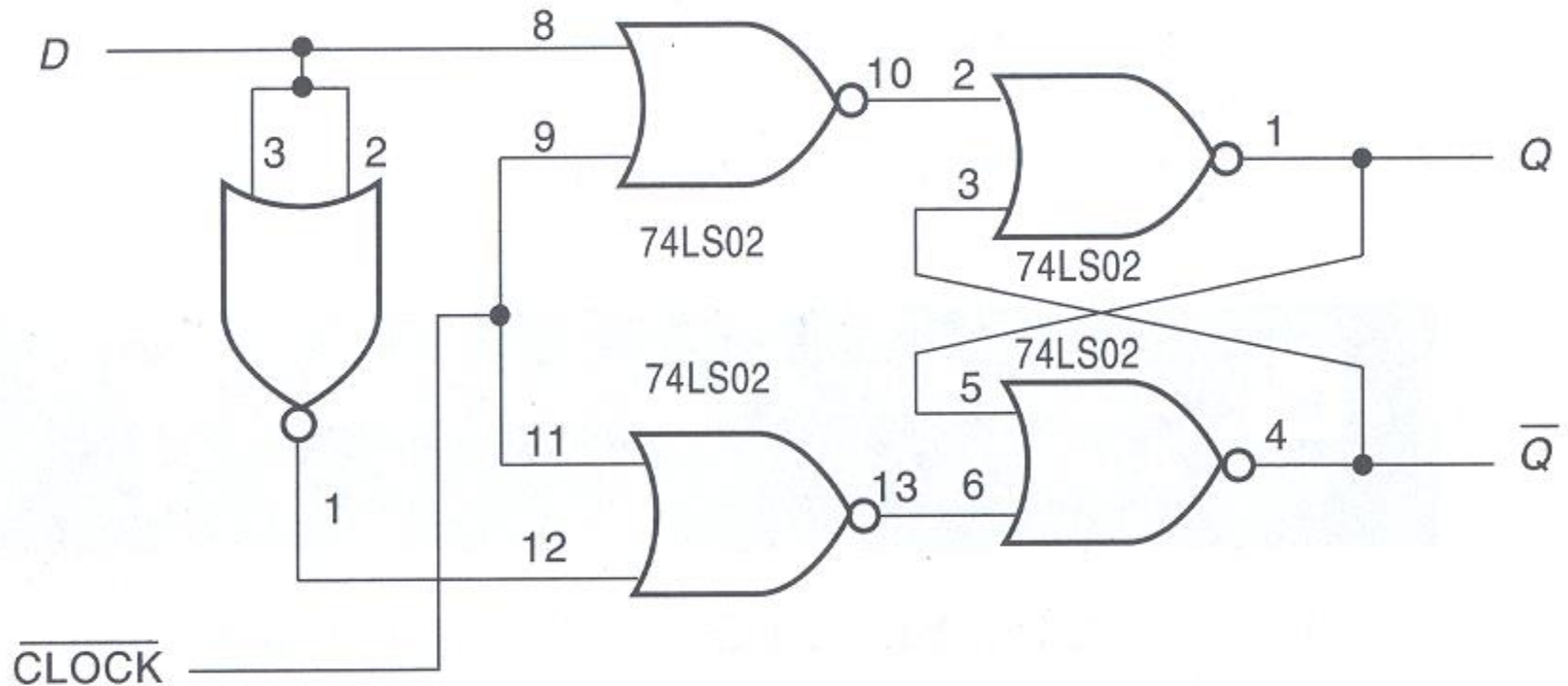

D Flip-Flop with **CLOCK** Activation

 


<i>D</i>	Clock	<i>Q</i>	\overline{Q}	Status
0	0	<i>Q</i>	\overline{Q}	Unchanged
1	0	<i>Q</i>	\overline{Q}	
0	1	0	1	Data Flip-flop
1	1	1	0	


D Flip-Flop from JK Flip-Flop

- D Flip-Flops can be configured from JK Flip-Flops;
- By use the J input as the D input;
- And putting an inverter between the J and K ;
- So, the J and K inputs will always be opposite logic.
- If $D = J = 1$ and ($K = 0$), the output will be 1;
- If $D = J = 0$ and ($K = 1$), the output will be 0;

D Flip-Flop from JK Flip-Flop

 


J	K	Q	\bar{Q}
0	0	Q	\bar{Q}
0	1	0	1
1	0	1	0
1	1	Toggle	

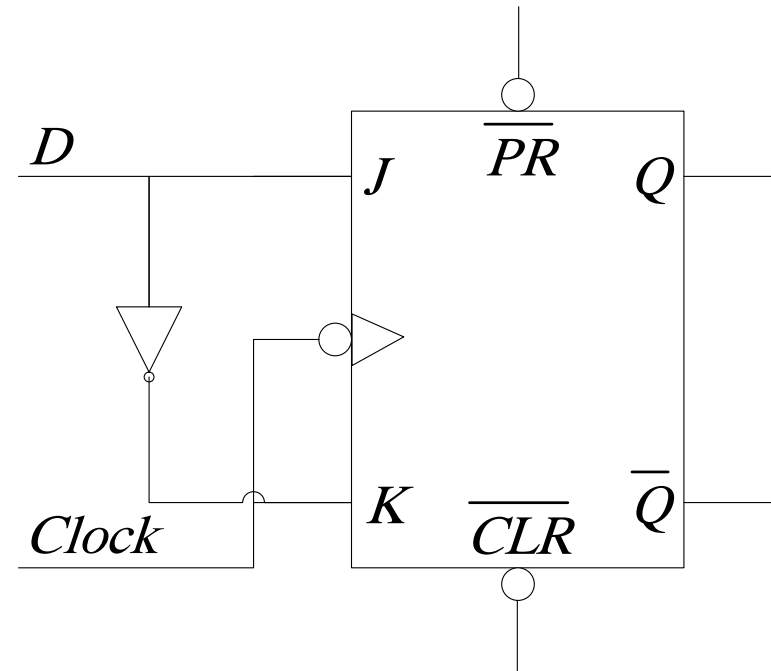


T (Toggle) Flip-Flop

- ❑ T Flip-Flop is another type of flip flop used in counting circuits.
- ❑ T Flip-Flop can be made from JK flip flop by
 - Applying 1 to both J and K .
 - And active the toggle by triggering from a clock;
 - The output will be inverted or opposite to the present logic.

T (Toggle) Flip-Flop

 


J	K	Q	\bar{Q}
0	0	Q	\bar{Q}
0	1	0	1
1	0	1	0
1	1	Toggle	

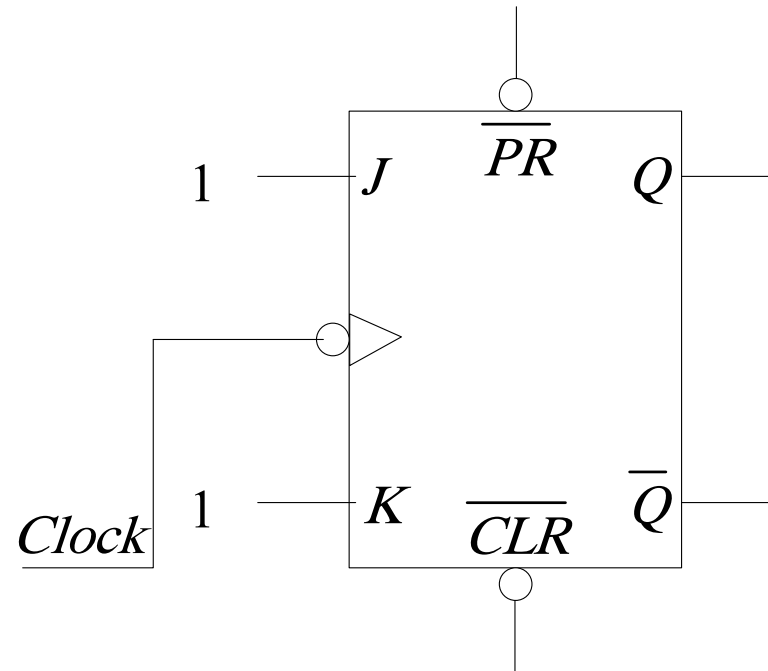

Master-Slave Flip-Flop

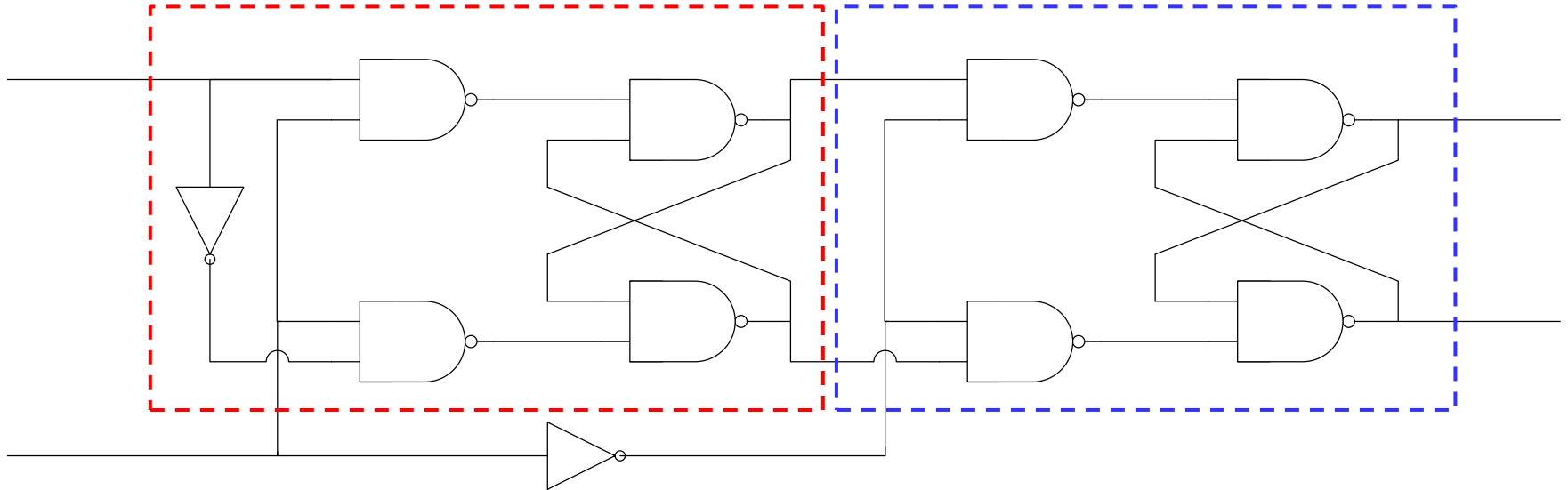Master-Slave Flip-Flop is a pair of flip-flops as illustrated.



Master-Slave Flip-Flops may be made from

- D Flip-Flops
- JK Flip-Flop

Master-Slave Flip-Flop

At the rising edge of the clock and during the clock is high:

- The first Flip-Flop works by passing the input D to its output.
- The second Flip-Flop is not activated since its clock is 0.

At the falling edge of the clock:


- The first Flip-Flop is not activated since its clock is 0.
- The second Flip-Flop works by passing the input D to its output.

➔ Negative Edge Triggered Data Transfer.

➔ Use tiny time at the negative edge for the data manipulation;


➔ Fast processing.

Master-Slave D Flip-Flop

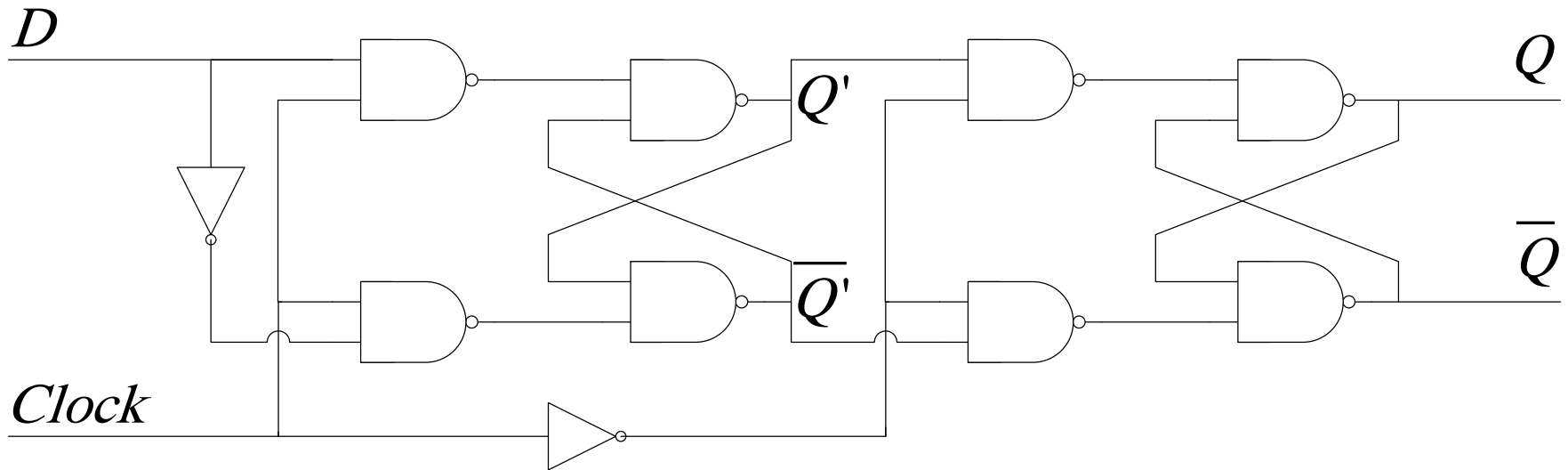

Negative Edge-Triggered Master-Slave D Flip-Flop


Master-Slave D Flip-Flop

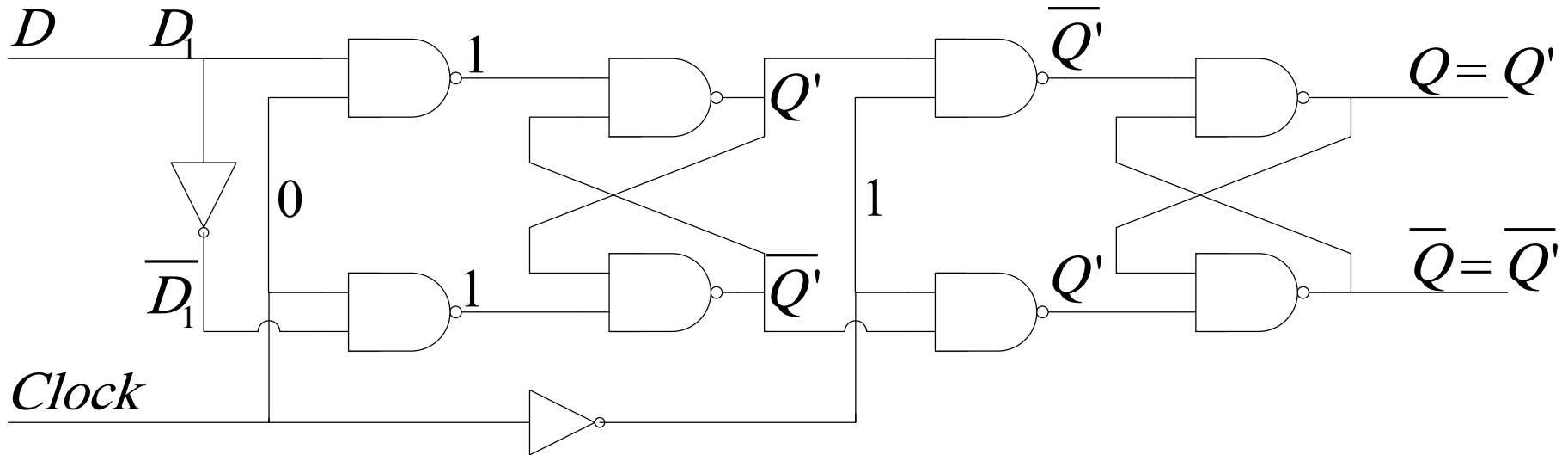

Clock


Negative Edge-Triggered Master-Slave D Flip-Flop

Master-Slave D Flip-Flop

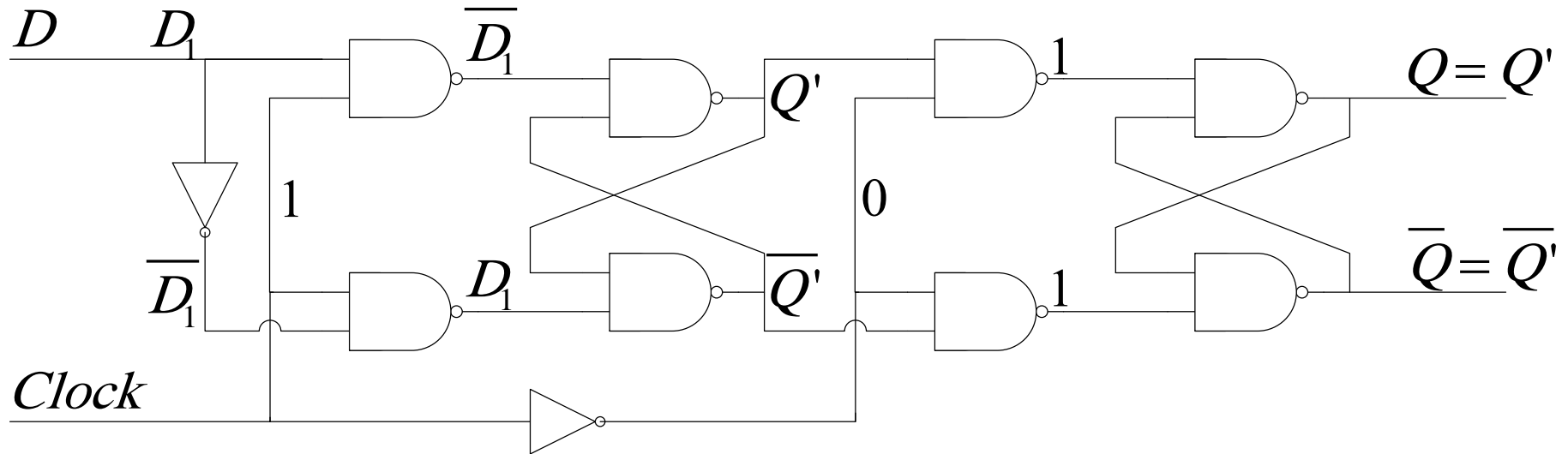


Negative Edge-Triggered Master-Slave D Flip-Flop

Master-Slave D Flip-Flop

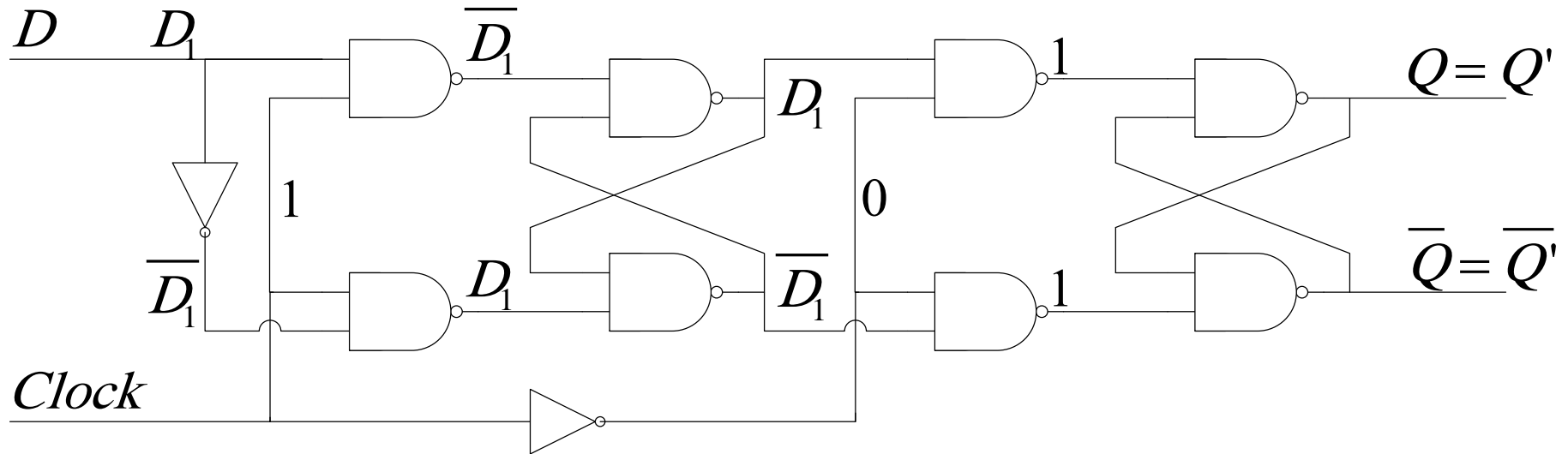

Negative Edge-Triggered Master-Slave D Flip-Flop

Master-Slave D Flip-Flop

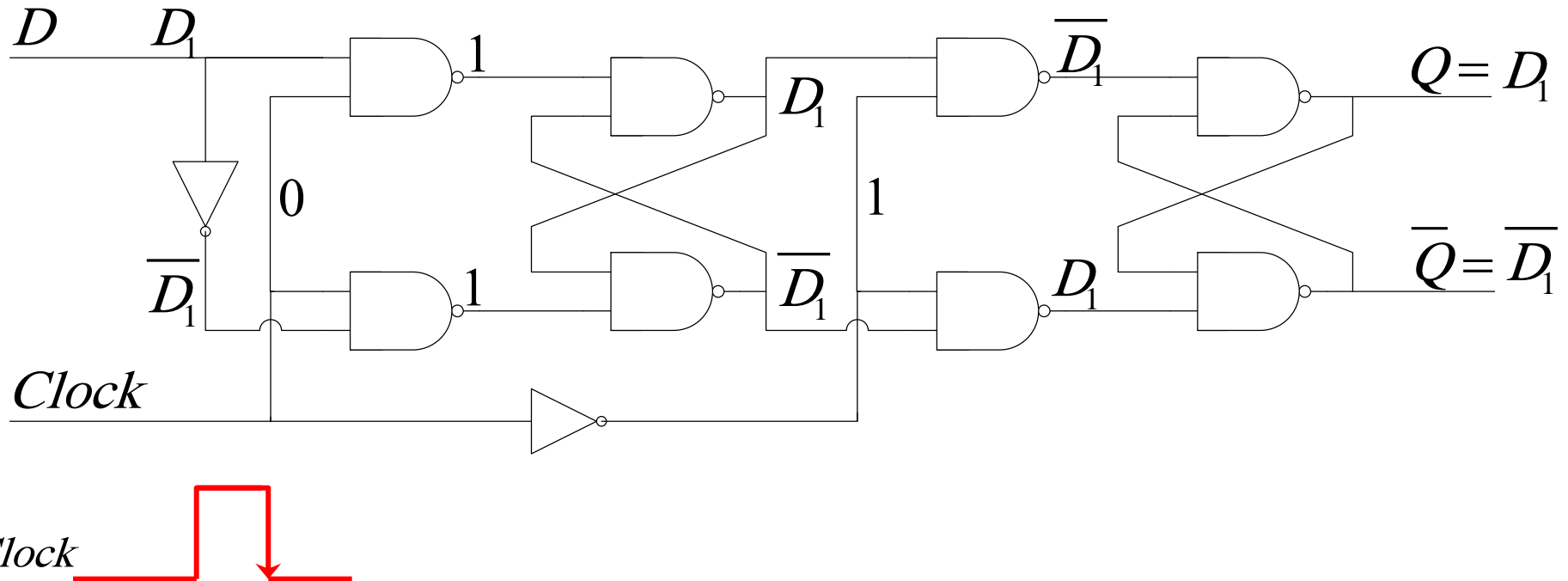


Negative Edge-Triggered Master-Slave D Flip-Flop

Flip-Flop : Implementation



Flip-Flop can be used in many applications:

- Memorize the assigned logic (D Flip-Flop);
➔ Register = A number of D Flip-Flops to memorize a byte of data.
- Changing the opposite logic (T Flip-Flop):
➔ Counter = A number of T Flip-Flops.
- Another application is the switch debouncer, as the circuit below:

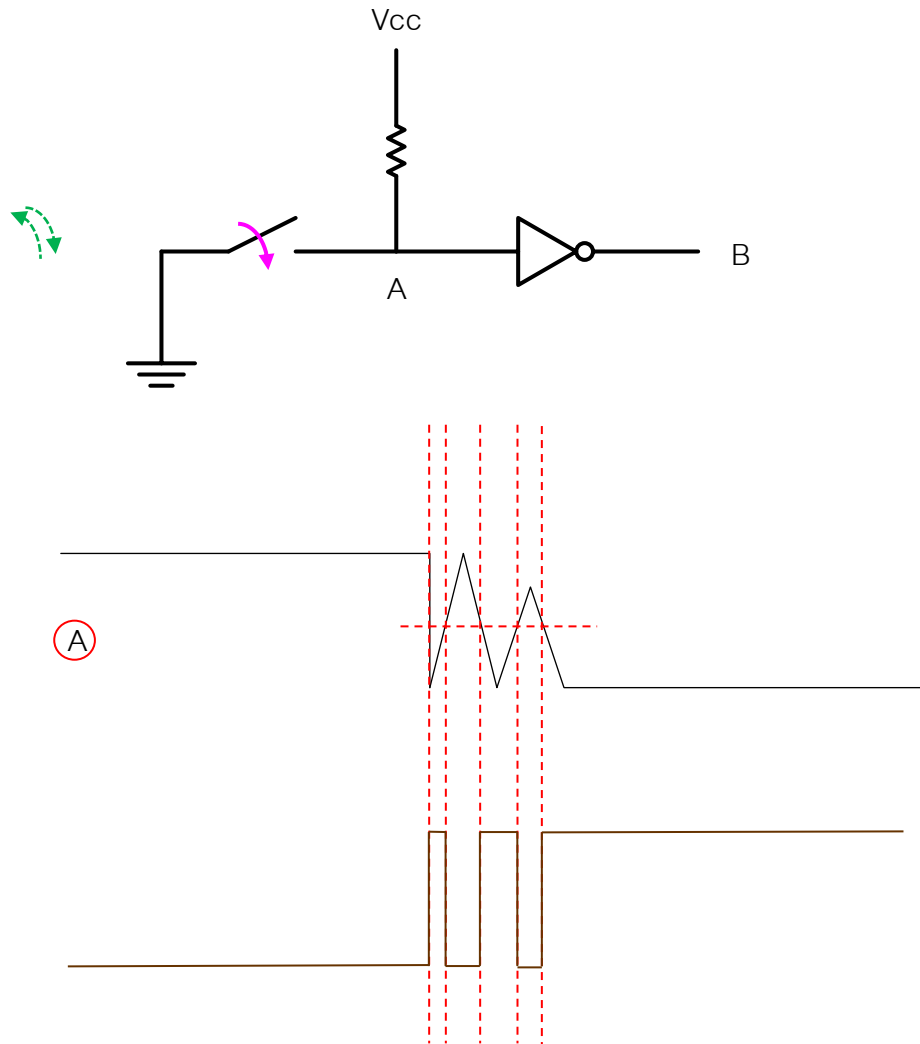Using A Set-Reset Flip-Flop as a Switch Debouncer [1]



 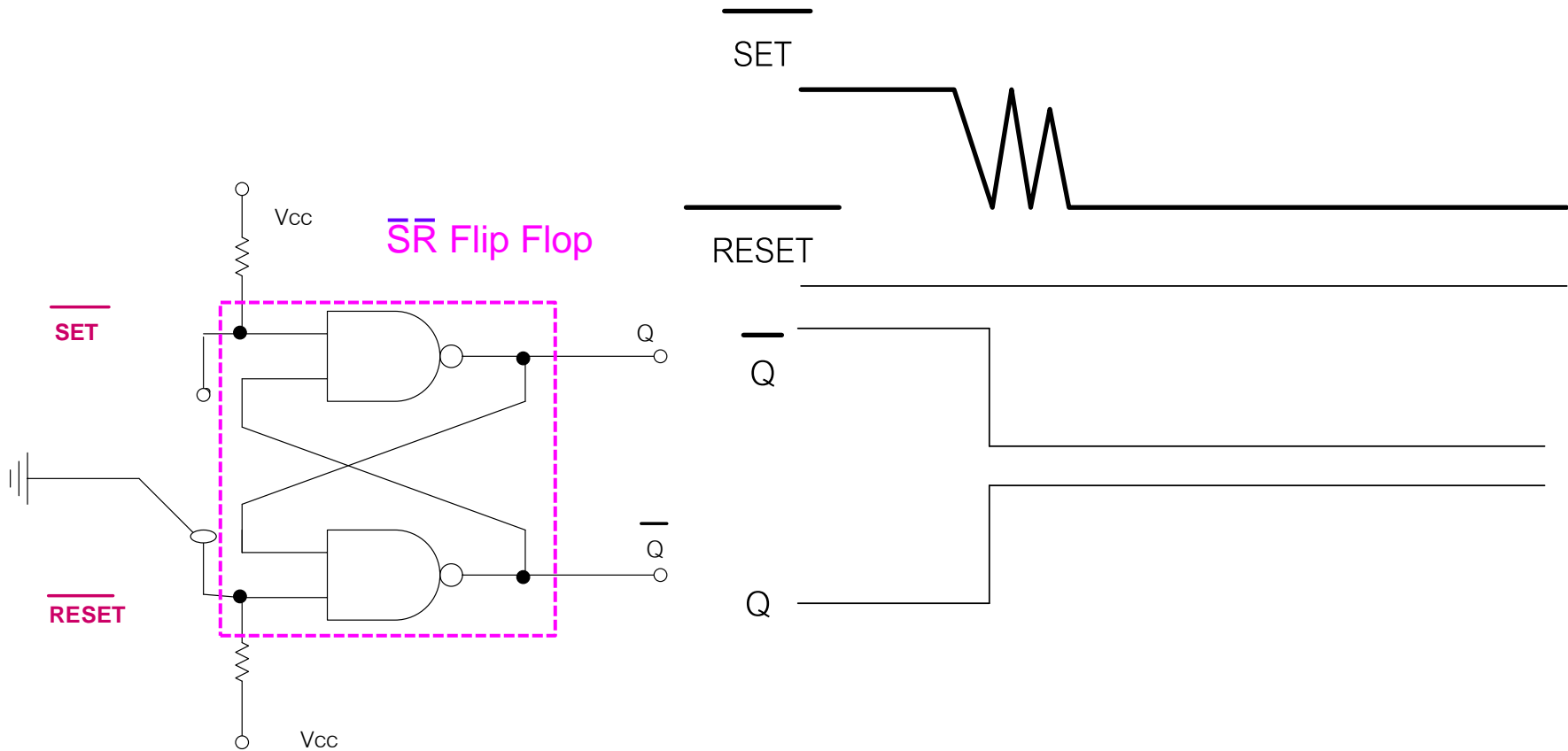Using A Set-Reset Flip-Flop as a Switch Debouncer [2]



Using A Set-Reset Flip-Flop as a Switch Debouncer [3]

