

Name: Student ID:


Name: Student ID:

Laboratory 4

Exclusive-OR gate and Exclusive-NOR gate

1. Exclusive-OR gate:

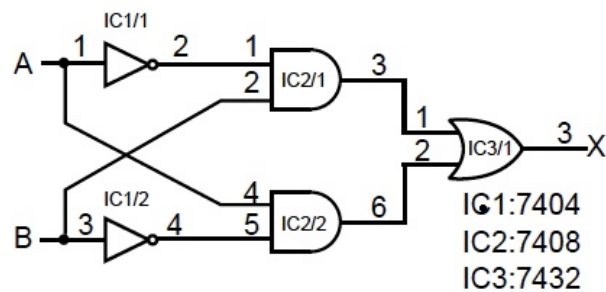1.1 Given a circuit as shown in the following figure:




1.2 Connect the circuit. Use logic switch to supply inputs as specified. The output signals should be connected to the logic monitor. Record the results in the following truth table.

A	B	X
0	0	
0	1	
1	0	
1	1	

1.3 Find the Boolean expression for the given circuit in 1.1.

Instructor's signature

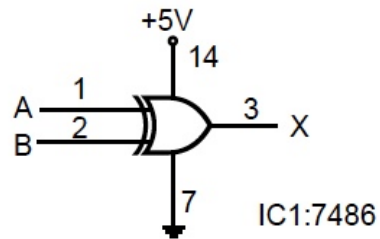1.4 Given a circuit as shown in the following figure



1.5 Connect the circuit. Use logic switch to supply inputs as specified. The output signals should be connected to the logic monitor. Record the result in the following truth table.


A	B	X
0	0	
0	1	
1	0	
1	1	

1.6 Compare the outputs of the previous two circuits and give conclusion?

Instructor's signature

2. Exclusive-NOR gate:

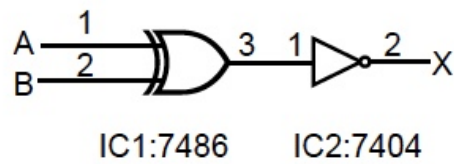2.1 Given a circuit as shown in the following figure




2.2 Connect the circuit. Use logic switch to supply inputs as specified. The output signals should be connected to the logic monitor. Record the result in the following truth table.

A	B	X
0	0	
0	1	
1	0	
1	1	

2.3 Find the Boolean expression and simplify it for the given circuit in 2.1.

Instructor's signature

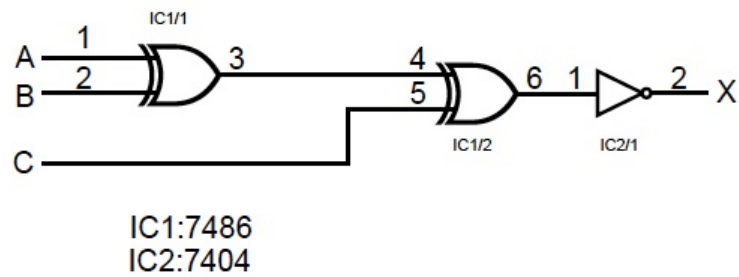2.4 Given a circuit as shown in the following figure




2.5 Connect the circuit. Use logic switch to supply inputs as specified. The output signals should be connected to the logic monitor. Record the results in the following truth table.

A	B	C	X
0	0	0	
0	0	1	
0	1	0	
0	1	1	
1	0	0	
1	0	1	
1	1	0	
1	1	1	

2.6 Find the Boolean expression and simplify for the given circuit in 2.4.

Instructor's signature

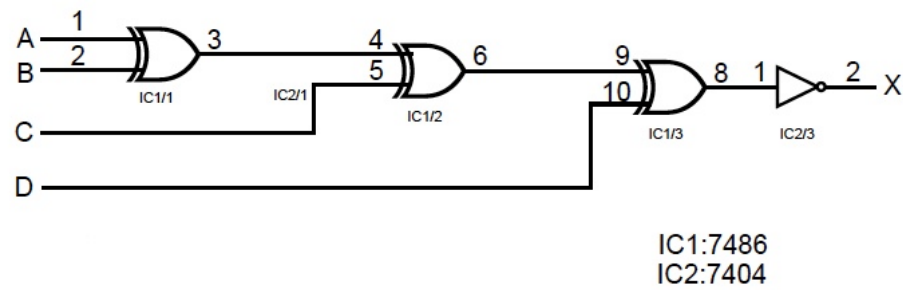2.7 Given a circuit as shown in the following figure



2.8 Connect the circuit. Use logic switch to supply inputs as specified. The output signals should be connected to the logic monitor. Record the results in the following truth table.

A	B	C	D	X
0	0	0	0	
0	0	0	1	
0	0	1	0	
0	0	1	1	
0	1	0	0	
0	1	0	1	
0	1	1	0	
0	1	1	1	
1	0	0	0	
1	0	0	1	
1	0	1	0	
1	0	1	1	
1	1	0	0	

A	B	C	D	X
1	1	0	1	
1	1	1	0	
1	1	1	1	

2.9 Find the Boolean expression for the given circuit in 2.7

2.10 Explain the characteristics of the circuit in 2.1, 2.4 and 2.7.

Instructor's signature

3 Assignments

- 3.1 There are 2 sensors required in a machine for electronics board manufacturing system. The first sensor detects the complete amount of a set of electrical components. This sensor gives LOW signals when a set of components is complete. The other sensor detects the damage of the board. It gives HIGH signal when the board is damage. The machine requires two display LEDs. The first and second LED will be ON when the board has a complete set of components but it is damage. The second LED will also be ON, when the board doesn't have a complete set of components but the board itself is not damage. Realize the logic circuit for this machine.

Instructor's signature

- 3.2 Connect a three-inputs circuit that results in the outputs specified in the following truth table.

A	B	C	X
0	0	0	1
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	1
1	0	1	0
1	1	0	1
1	1	1	0

Instructor's signature

- 3.3 The input signal is given as BCD digit (0-9). Realize a circuit including at least one exclusive-OR gate such that the outputs of the circuit will be the remainder of the inputs divided by 6.

Instructor's signature

Logic Diagram of frequently used gates