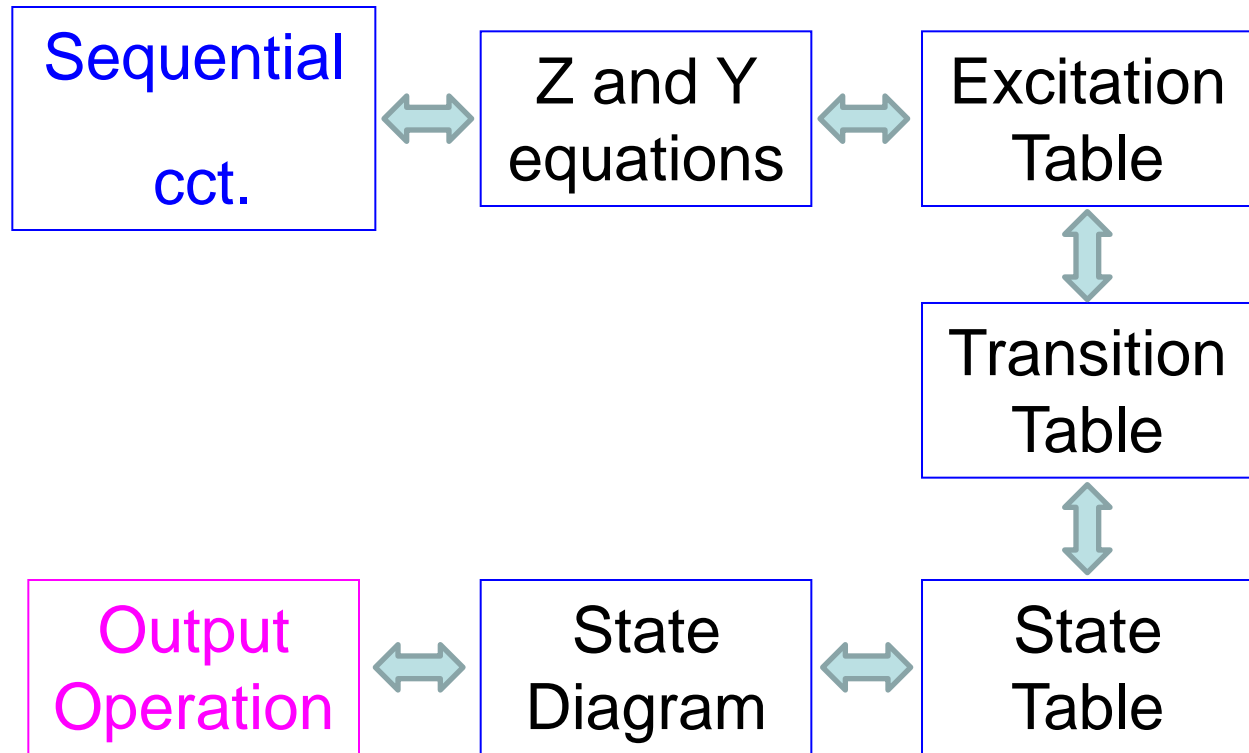


12

**Synchronous Sequential
Circuit Design**

Circuit Analysis →



Circuit Design →

Synchronous Sequential Circuit Design

Design Principles : follows these steps

- 1) Find the state diagram and state table from the given assignments;
- 2) Assign the appropriate codes for the state names,
such as $A = 00$, $B = 01$, $C = 11$ and $D = 10$.
- 3) Write the transition table and excitation map of the desired flip-flops,
- 4) Write the k-map between the inputs of logical inputs and present states (PS) for individual outputs of next states (NS) and logical outputs.
- 5) Write the logic equations from the k-map and create the corresponding circuit.

Synchronous Sequential Circuit Design: Example

Example For the given state table, design a synchronous sequential cct.

Using A) D flipflop
 B) JK flipflop

A) Using D flip-flops:

1) From the given state table,

2) Since there are 4 states, we need 2 D flip-flops.

We can assign the state variable codes y_1y_2 ,
by setting $A = 00$, $B = 01$, $C = 11$ and $D = 10$.

3) Write the transition table,

PS \ X	0	1
A	A/0	B/0
B	A/0	C/1
C	B/0	D/0
D	C/1	D/0

NS/Z

Y_1Y_2 \ X	0	1
00	00 / 0	01 / 0
01	00 / 0	11 / 1
11	01 / 0	10 / 0
10	11 / 1	10 / 0

Y_1Y_2 / Z

Synchronous Sequential Circuit Design: Example

Since using D flip-flops, whose state equation is $D = Y$;

So $D_1 = Y_1$ and $D_2 = Y_2$

Then get excitation maps of both D flip-flops.

$Y_1Y_2 \backslash X$	0	1
00	00 / 0	01 / 0
01	00 / 0	11 / 1
11	01 / 0	10 / 0
10	11 / 1	10 / 0


Y_1Y_2 / Z

$Y_1Y_2 \backslash X$	0	1
00	00 / 0	01 / 0
01	00 / 0	11 / 1
11	01 / 0	10 / 0
10	11 / 1	10 / 0

Y_1Y_2 / Z

$Y_1Y_2 \backslash X$	0	1
00	00 / 0	01 / 0
01	00 / 0	11 / 1
11	01 / 0	10 / 0
10	11 / 1	10 / 0

Y_1Y_2 / Z

 

Synchronous Sequential Circuit Design: Example

4) Write the k-map between the inputs of logical inputs and PS for individual outputs of next states (NS) and logical outputs.

$Y_1Y_2 \backslash X$	0	1
00	00 / 0	01 / 0
01	00 / 0	11 / 1
11	01 / 0	10 / 0
10	11 / 1	10 / 0

Y_1Y_2 / Z

$Y_1Y_2 \backslash X$	0	1
00	00 / 0	01 / 0
01	00 / 0	11 / 1
11	01 / 0	10 / 0
10	11 / 1	10 / 0

Y_1Y_2 / Z

$Y_1Y_2 \backslash X$	0	1
00	00 / 0	01 / 0
01	00 / 0	11 / 1
11	01 / 0	10 / 0
10	11 / 1	10 / 0

Y_1Y_2 / Z

$y_1y_2 \backslash x$	0	1
00	0	0
01	0	1
11	0	1
10	1	1

$y_1y_2 \backslash x$	0	1
00	0	1
01	0	1
11	1	0
10	1	0

$\wedge \backslash$	0	1
00	0	0
01	0	1
11	0	0
10	1	0

D_1

$$D_1 = y_1 \bar{y}_2 + x y_2$$

D_2

$$D_2 = \bar{x} y_1 + \bar{x} \bar{y}_1 = x \oplus y_1$$

Z

$$Z = x \bar{y}_1 y_2 + \bar{x} y_1 \bar{y}_2$$



Synchronous Sequential Circuit Design: Example

5) Write the logic equations
from the k-map
and draw the corresponding circuit.

$$Z = x\bar{y}_1y_2 + \bar{x}y_1\bar{y}_2$$

$$D_1 = y_1\bar{y}_2 + xy_2$$
  
$$D_2 = \bar{x}y_1 + x\bar{y}_1 = x \oplus y_1$$



Synchronous Sequential Circuit Design: Example

A) Using JK flip-flops:

1) From the given state table,

2) Since there are 4 states, we need 2 JK flip-flops.

We can assign the state variable codes y_1y_2 ,
by setting $A = 00$, $B = 01$, $C = 11$ and $D = 10$.

3) Write the transition table,

PS	X	0	1
A		A/0	B/0
B		A/0	C/1
C		B/0	D/0
D		C/1	D/0

NS/Z

Y_1Y_2	X	0	1
00		00 / 0	01 / 0
01		00 / 0	11 / 1
11		01 / 0	10 / 0
10		11 / 1	10 / 0

Y_1Y_2 / Z

Synchronous Sequential Circuit Design: Example

Then get excitation maps of both JK flip-flops.

The same as D FF

Y_1Y_2 \ X		0	1
00		00 / 0	01 / 0
01		00 / 0	11 / 1
11		01 / 0	10 / 0
10		11 / 1	10 / 0

PS → Y_1Y_2/Z

Y_1Y_2 \ X		0	1
00		00 / 0	01 / 0
01		00 / 0	11 / 1
11		01 / 0	10 / 0
10		11 / 1	10 / 0

PS → Y_1Y_2/Z

Y_1Y_2 \ X		0	1
00		00 / 0	01 / 0
01		00 / 0	11 / 1
11		01 / 0	10 / 0
10		11 / 1	10 / 0

Y_1Y_2/Z

To get NS Y_1 and Y_2 need to apply at JK inputs by $[J_1K_1] = Y_1$ and $[J_2K_2] = Y_2$.

y_1y_2 \ X		0	1
00		0d	0d
01		0d	1d
11		d1	d0
10		d0	d0

J_1K_1

y_1y_2 \ X		0	1
00		0d	1d
01		d1	d0
11		d0	d1
10		1d	0d

J_2K_2

y_1y_2 \ X		0	1
00		0	0
01		0	1
11		0	0
10		1	0

Synchronous Sequential Circuit Design: Example

4) Write the k-map between the inputs of logical inputs and PS for individual outputs of next states (NS) and logical outputs.

X \ y ₁ y ₂	00	01	11	10
0	0d	0d	d1	d0
1	0d	1d	d0	d0

$J_1 K_1$



X \ y ₁ y ₂	00	01	11	10
0	0	0	d	d
1	0	1	d	d

$$J_1 = x y_2$$

X \ y ₁ y ₂	00	01	11	10
0	d	d	1	0
1	d	d	0	0

$$K_1 = \bar{x} y_2$$

X \ y ₁ y ₂	00	01	11	10
0	0d	d1	d0	1d
1	1d	d0	d1	0d

$J_2 K_2$



X \ y ₁ y ₂	00	01	11	10
0	0	d	d	1
1	1	d	d	0

$$J_2 = x \bar{y}_1 + \bar{x} y_1$$

$$J_2 = x \oplus y_1$$

X \ y ₁ y ₂	00	01	11	10
0	d	1	0	d
1	d	0	1	d

$$K_2 = x y_1 + \bar{x} \bar{y}_1$$

$$K_2 = \overline{x \oplus y_1}$$


Synchronous Sequential Circuit Design: Example

5) Write the logic equations
from the k-map
and draw the corresponding circuit.

$$Z = x\bar{y}_1y_2 + \bar{x}y_1\bar{y}_2$$

$$J_1 = xy_2 \quad K_1 = \bar{x}y_2$$
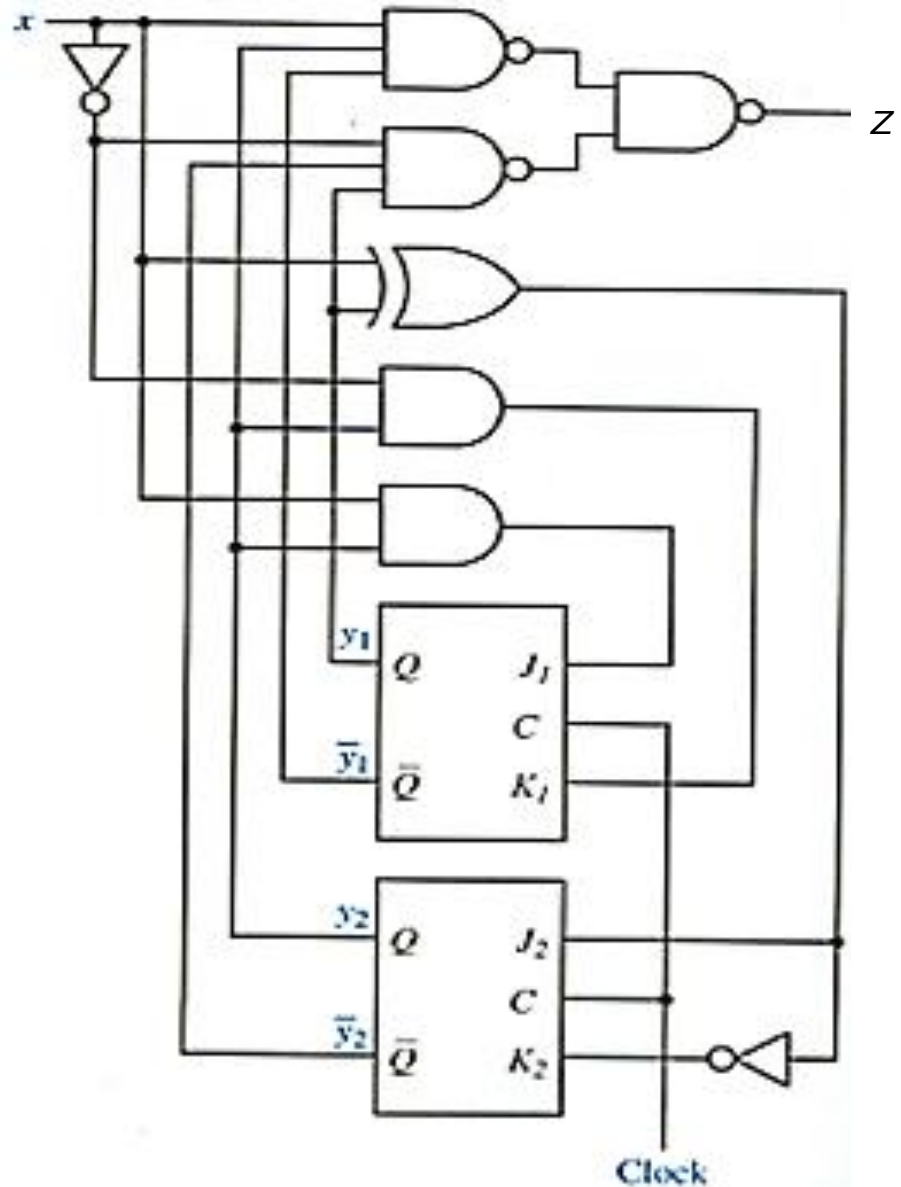
$$J_2 = x \oplus y_1 \quad K_2 = \overline{x \oplus y_1}$$




Flip-Flop Excitation Tables

Flip-flop input table

- In the previous example, we find that the excitation equations for the circuit with D FF is easier than that with JK FF.
- This is because D FF has the state equation, NS: $Y = D$
- The state equation can be derived from state diagram, excitation table and minimizing it in K-Map (transition table) as shown below:

State Transitions		Required Inputs $D(r)$
$Q(r)$	$Q(r + \epsilon)$	
0	0	0
0	1	1
1	0	0
1	1	1

$D = 1$

 


		D	
		0	1
PS Y	0	0	1
	1	0	1

NS (Y)


D Flip-flop: $Y = D$

Flip-Flop Excitation Tables

 


SR Flipflop

$$Y = S + \bar{R} y$$

 

JK Flipflop

$$Y = J \bar{y} + \bar{K} y$$

 

T Flipflop

$$Y = T \bar{y} + \bar{T} y$$

Synchronous Sequential Circuit Design: Example

Example From the State table below, design the Synchronous Sequential circuit using **a) D flip-flop** and **b) JK flip-flop**.

Step I: Assign the state codes:

- Let A = 000, B = 001, C = 010, D = 011 and E = 100
- And set the rest unused states (101, 110, 111) as Don't Care = ddd/d.

Step II: Change the state name to state codes, then get the transition table;

Input Variables: y_1, y_2, y_3 and x

$y_1 y_2 y_3$	PS	x	0	1
000	A		B / 0	E / 0
001	B		A / 1	C / 1
010	C		B / 0	C / 0
011	D		C / 0	E / 0
100	E		D / 1	A / 0

NS/Z

Output Variables: Y_1, Y_2, Y_3 and Z

$y_1 y_2 y_3$	x	0	1
A 000		001 / 0	100 / 0
B 001		000 / 1	010 / 1
C 010		001 / 0	010 / 0
D 011		010 / 0	100 / 0
E 100		011 / 1	000 / 0
d 101		ddd / d	ddd / d
d 110		ddd / d	ddd / d
d 111		ddd / d	ddd / d

$Y_1 Y_2 Y_3 / Z$

Circuit Design: Example for D Flip-Flop.

Step III: Write individual outputs in the transition table in separated K-Maps:

		X	
	$y_1 y_2 y_3$	0	1
A	000	001 / 0	100 / 0
B	001	000 / 1	010 / 1
C	010	001 / 0	010 / 0
D	011	010 / 0	100 / 0
E	100	011 / 1	000 / 0
d	101	ddd / d	ddd / d
d	110	ddd / d	ddd / d
d	111	ddd / d	ddd / d

$Y_1 Y_2 Y_3 / Z$

$y_3 x$ $y_1 y_2$	00	01	11	10
00	0	1	0	0
01	0	0	1	0
11	d	d	d	d
10	0	0	d	d

$$D_1 = x \bar{y}_1 \bar{y}_2 \bar{y}_3 + x y_2 y_3$$

D_2

$y_3 x$ $y_1 y_2$	00	01	11	10
00				
01				
11				
10				

D_3

$y_3 x$ $y_1 y_2$	00	01	11	10
00				
01				
11				
10				

Z

$y_3 x$ $y_1 y_2$	00	01	11	10
00				
01				
11				
10				

Circuit Design: Example for JK Flip-Flop.

Step III: Write individual outputs in the transition table in separated K-Maps:

	$y_1y_2y_3$	X	0	1
A	000		001 / 0	100 / 0
B	001		000 / 1	010 / 1
C	010		001 / 0	010 / 0
D	011		010 / 0	100 / 0
E	100		011 / 1	000 / 0
d	101		ddd / d	ddd / d
d	110		ddd / d	ddd / d
d	111		ddd / d	ddd / d

$Y_1Y_2Y_3 / Z$

J_1K_1

$y_1y_2 \backslash y_3X$	00	01	11	10
00	0d	1d	0d	0d
01	0d	0d	1d	0d
11	dd	dd	dd	dd
10	d1	d1	dd	dd

J_2K_2

$y_3X \backslash y_1y_2$	00	01	11	10
00				
01				
11				
10				

J_3K_3

$y_1y_2 \backslash y_3X$	00	01	11	10
00	0	0	1	1
01	0	0	0	0
11	d	d	d	d
10	1	0	d	d

$Y_1 = D_1$

$y_3X \backslash y_1y_2$	00	01	11	10
00				
01				
11				
10				

Synchronous Sequential Circuit Design: Example

J_1

$y_1y_2 \backslash y_3X$	00	01	11	10
00	0d	1d	0d	0d
01	0d	0d	1d	0d
11	d0	d0	d0	d0
10	d0	d0	d0	d0

K_1

$y_1y_2 \backslash y_3X$	00	01	11	10
00	0d	0d	0d	0d
01	0d	0d	0d	0d
11	0d	0d	0d	0d
10	01	01	0d	0d

Then we get these equations:

$$J_1 = (y_2 \odot y_3)x$$

$$J_2 = y_3x + y_1\bar{y}_3x$$

$$J_3 = \bar{x}$$

$$Z = \bar{y}_2y_3 + y_1\bar{x} + y_2\bar{y}_3x$$


$$K_1 = 1$$

$$K_2 = (y_3 \odot x)$$

$$K_3 = 1$$

Equation Reduction By Variable Entry Map (VEM)

 Example: We can reduce the equation in a system with **two** D Flip-Flops, as follows:



Equation Reduction By Variable Entry Map (VEM)

Example: We can reduce the equation by VEM in a system with **three** D Flip-Flops, as follows:

y_3x y_1y_2	00	01	11	10
00	0	1	0	0
01	0	0	1	0
11	d	d	d	d
10	0	0	d	d

Y_1 of First D FF



y_3 y_1y_2	0	1
00	x	0
01	0	x
11	d	d
10	0	d

Y_1 of First D FF

x is in the map → Mealy Model

K-Map Transform From D FF to JK FF

Converting a K-map table of D flipflop to a k-map of JK flipflop

- For a transition table, finding a K-map for D flip-flop is easier than that of JK flip-flop;
- Firstly, we prefer to design with D flip-flop to produce the excitation table;
- Then transform it to that of the JK flip-flop (the most popular);
- Finally, we get the logic equation for that circuit.

Principles from state equation of D flipflop:

$$Y = D$$

and the equation of JK flipflop:

$$Y = J\bar{y} + \bar{K}y$$

$$D = J\bar{y} + \bar{K}y$$

Then get the relationship:

So, we can separate the excitation Maps for J and K as :

Map J : $D = J\bar{y}$

For $y = 0 \rightarrow J = Y = D$

For $y = 1 \rightarrow J = d$

Map K : $D = \bar{K}y$

For $y = 0 \rightarrow K = d$

For $y = 1 \rightarrow K = \bar{Y} = \bar{D}$

K-Map Transform From D FF to JK FF

Example From the first example, transform the K-map of individual outputs D FF/JK FF to those of the JK FF.

Solution From the results of D FF

$y_1 y_2 \backslash x$	0	1
00	0	0
01	0	1
11	0	1
10	1	1

Map J : $D = J \bar{y}$
 $y = 0 \rightarrow J = Y = D$
 $y = 1 \rightarrow J = d$

Map K : $D = \bar{K} y$
 $y = 0 \rightarrow K = d$
 $y = 1 \rightarrow K = \bar{Y} = \bar{D}$


$y_1 y_2 \backslash x$	0	1
00	0	0
01	0	1
11	0	1
10	1	1

$$J_1 = y_2 x$$

$y_1 y_2 \backslash x$	0	1
00	0	0
01	0	1
11	0	1
10	1	1

d	d
d	d
1	0
0	0
$K_1 = y_2 x$	
d	d
d	d

K-Map Transform From D FF to JK FF

 

We get the same solution as done in the first example, but much easier.

Map J : $D = J \bar{y}$
 $y = 0 \rightarrow J = Y = D$
 $y = 1 \rightarrow J = d$


Map K : $D = \bar{K} y$
 $y = 0 \rightarrow K = d$
 $y = 1 \rightarrow K = \bar{Y} = \bar{D}$

K-Map Transform From D FF to JK FF

Example Redo the problem by Short-out method: Ignore the don't care cases,

- consider the case of $y = 0$ for the J Map and
- the case of $y = 1$ for the K Map.

Solution

 

Map J : $D = J \bar{y}$
 $y = 0 \rightarrow J = Y = D$
 $y = 1 \rightarrow J = d$

Map K : $D = \bar{K} y$
 $y = 0 \rightarrow K = d$
 $y = 1 \rightarrow K = \bar{Y} = \bar{D}$

Synchronous Sequential Circuit Design: Example


Example Find the state diagram and state tables of the synchronous sequential circuit that detects bit stream of 0110 in the pattern of
a) non-overlapping and b) overlapping in the stream.

Solution

 a) Non-overlapping: If $x = 0110110110$
The circuit will produce $z = 0001000001$

We can draw the state diagram to detect 0110 by assigning 4 states:

A = State to detect '0'
B = State to detect '01'
C = State to detect '011'
D = State to detect '0110'
Then go to A



Synchronous Sequential Circuit Design: Example

b) Overlapping: If
The circuit will produce

$x = 0110110110$
 $z = 000100\mathbf{1}001$

We can draw the state diagram to detect 0110 by assigning 4 states:


So, we need 4 states:

A = State to detect '0'

B = State to detect '01'

C = State to detect '011'

D = State to detect '0110'

 

Since it has detected '0' Then go to B.

Synchronous Sequential Circuit Design: Example

The state tables of both circuit can be produced from their state diagrams obtained.

PS	X	0	1
A		B/0	A/0
B		B/0	C/0
C		B/0	D/0
D		A/1	A/0

NS/Z

Non-overlapping

PS	X	0	1
A		B/0	A/0
B		B/0	C/0
C		B/0	D/0
D		B/1	A/0

NS/Z

Overlapping

- We could assign the state codes for the individual state names.
- e.g., from the assignment table above: A = 00, B = 01, C = 11 and D = 10
- Then we can also make their transition tables,
- excitation tables and the sequential circuits.

Synchronous Sequential Circuit Design: Example

Example Find the state diagram and state tables of the synchronous sequential circuit that detects bit stream of 1001 in the pattern of
a) non-overlapping and b) overlapping in the bit stream.

Answer

		X	
		0	1
PS			
A		A/0	B/0
B		C/0	B/0
C		D/0	B/0
D		A/0	A/1

Non-overlapping

		X	
		0	1
PS			
A		A/0	B/0
B		C/0	B/0
C		D/0	B/0
D		A/0	B/1

Overlapping

Solution

