

Name: Theepakorn Phayonrat Student ID: 67011352  
 Name: ..... Student ID: .....

## Laboratory 6

### Karnaugh Map

1. Write the output logic equation according to the following given truth table;

A	B	C	X
0	0	0	1
0	0	1	0
0	1	0	1
0	1	1	1
1	0	0	1
1	0	1	0
1	1	0	1
1	1	1	0

A	B	C	X
0	0	0	1
0	0	1	0
0	1	0	1
0	1	1	1
1	0	0	1
1	0	1	0
1	1	0	1
1	1	1	0

- 1.1 In m-notation of minterm expansion form:

$$F(A,B,C) = \sum m(0, 2, 3, 4, 6)$$

- 1.2 In m-notation of maxterm expansion form:

$$F(A,B,C) = \prod M(1, 5, 7)$$

- 1.3 In algebraic form:

$$\begin{aligned} X &= \bar{A}\bar{B}\bar{C} + \bar{A}B\bar{C} + \bar{A}BC + A\bar{B}\bar{C} + ABC \\ X &= (\bar{B}+B)A\bar{C} + (\bar{B}+B)\bar{A}C + \bar{A}BC \\ &= \bar{A}\bar{C} + \bar{A}C + \bar{A}BC = (\bar{A}+A)\bar{C} + \bar{A}BC = \bar{A}BC + \bar{C} = \bar{A}B + \bar{C} \end{aligned}$$

$$\bar{X} = (A+B\bar{C})(\bar{A}+B+C)(\bar{A}+\bar{B}+\bar{C})$$

Instructor's signature

*S.*

2. Draw a Karnaugh map from the truth table shown in 1. Demonstrate looping the 1's in the map in order to obtain the minimum solution.


A \ BC	00	01	11	10
0	1	0	1	1
1	1	0	0	1

$$\begin{aligned}
 X &= \bar{A}BC + \bar{C} \\
 &= \bar{A}B + \bar{C}
 \end{aligned}$$

Instructor's signature



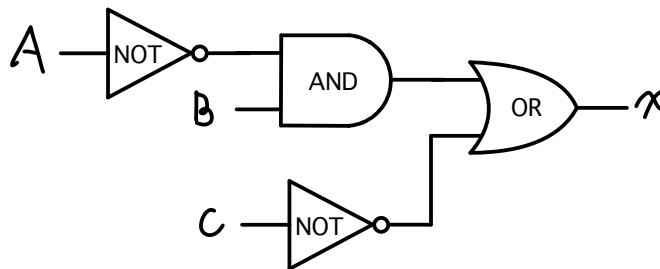3. Draw a corresponding logic circuit diagram from the logic equation obtained from 2. Connect the circuit and record the results:



A	B	C	X
0	0	0	1
0	0	1	0
0	1	0	1
0	1	1	1
1	0	0	1
1	0	1	0
1	1	0	1
1	1	1	0

Instructor's signature



4. Write the output logic equation according to the following given truth table;

A	B	C	D	Y
0	0	0	0	1
0	0	0	1	0
0	0	1	0	1
0	0	1	1	0
0	1	0	0	X
0	1	0	1	1
0	1	1	0	1
0	1	1	1	1
1	0	0	0	0
1	0	0	1	0
1	0	1	0	1
1	0	1	1	0
1	1	0	0	0
1	1	0	1	1
1	1	1	0	0
1	1	1	1	X

- 4.1 In m-notation of minterm expansion form:

$$F(A,B,C,D) = \sum m(0, 2, 5, 6, 7, 10, 13) + d(4, 15)$$

- 4.2 In m-notation of maxterm expansion form:

$$F(A,B,C,D) = \prod M(1, 3, 8, 9, 11, 12, 14) + d(4, 15)$$

- 4.3 In algebraic from:

$$\begin{aligned}
 X &= \bar{A}\bar{B}\bar{C}\bar{D} + \bar{A}\bar{B}C\bar{D} + \bar{A}B\bar{C}\bar{D} + \bar{A}B\bar{C}D + \bar{A}BC\bar{D} + \bar{A}BCD + A\bar{B}\bar{C}\bar{D} + A\bar{B}\bar{C}D \\
 \bar{X} &= (A+B+C+D)(A+B+C\bar{D})(\bar{A}+B+C+D)(\bar{A}+B+C\bar{D}) \\
 &\quad (\bar{A}+B+C\bar{D}) + (\bar{A}+\bar{B}+C+D)(\bar{A}+\bar{B}+\bar{C}+D)
 \end{aligned}$$

Instructor's signature



5. Draw a Karnaugh map from the truth table shown in 4. Demonstrate looping the 1's in the map in order to obtain the minimum solution.

AB \ CD	00	01	11	10
00	1	0	0	1
01	d	1	1	1
11	0	1	d	0
10	0	0	0	1

$$X = \bar{A}\bar{D} + BD + \bar{A}BC\bar{D}$$

$$= (\bar{A} + A\bar{B}C)\bar{D} + BD$$


$$= (\bar{A} + \bar{B}C)\bar{D} + BD$$

$$= \bar{A}\bar{D} + \bar{B}C\bar{D} + BD$$

Instructor's signature



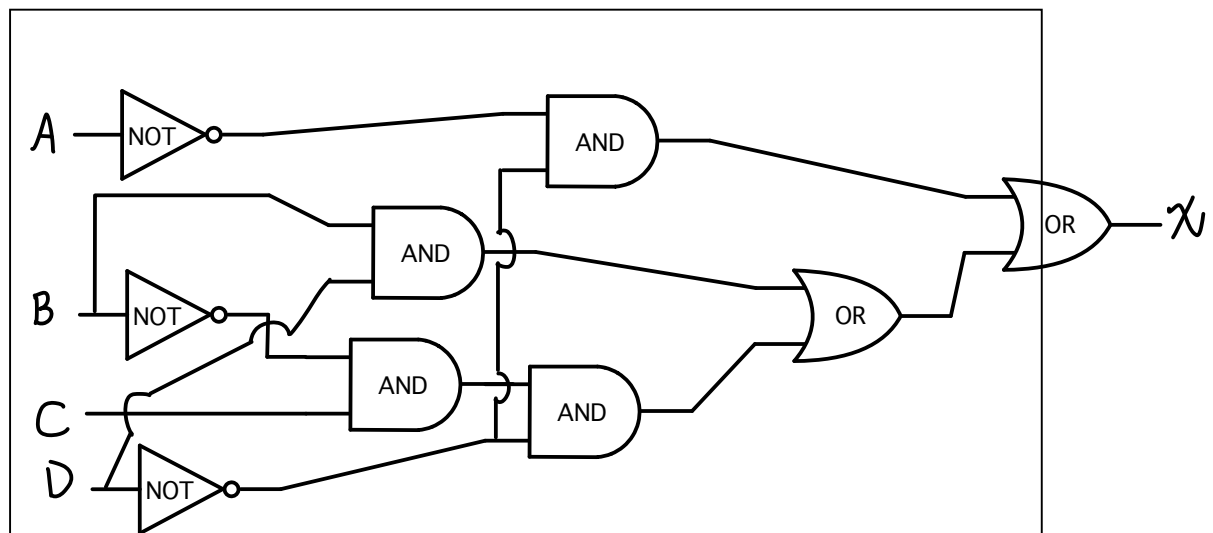6. Draw a corresponding logic circuit diagram from the logic equation obtained from 5. Connect the circuit and record the results:



A	B	C	D	Y
0	0	0	0	1
0	0	0	1	0
0	0	1	0	1
0	0	1	1	0
0	1	0	0	1
0	1	0	1	1
0	1	1	0	1
0	1	1	1	1
1	0	0	0	0
1	0	0	1	0
1	0	1	0	1
1	0	1	1	0
1	1	0	0	0
1	1	0	1	1
1	1	1	0	0
1	1	1	1	1

Instructor's signature



7. Give conclusion about the advantages of using Karnaugh map to find the minimum solution.

Solving for result by using SOP, POS, and K-map will come out with the same result.

Instructor's signature



8. Assignments:

8.1 The product package machine is built such that it loads the products into the package in the predefined number. If the desired number to be loaded is set to  $n$ , the machine is expected to load the products into the package in the range of  $[n-3, n+3]$ . From the detailed study, an engineer finds that, the machine will only load the products in the range of  $[n-8, n+7]$ . Design a logic circuit for this machine such that it outputs the alarm if the number of loaded products to the package is out of range.

- Construct a truth table
- Construct a Karnaugh map
- Give the corresponding logic equation
- Build the corresponding circuit to show the result

Instructor's signature

8.2 A simple floodgate has a sensor to measure incoming water level, which can be classified into 10 levels, (0-9). The opening height of the floodgate depends on this incoming water level. For water level of 0-3, the floodgate will be at its upper level. For water level of 4-6, the floodgate will be at its middle level, otherwise it will be at its lower level. Construct a logic circuit, which give the alarm signal when the floodgate is at its lower level.

Instructor's signature


8.3 Construct a minimum circuit which receives BCD inputs indicating the number of month in a year (for example, January is 1, February is 2, and so on). The circuit shall have the following functions:

- If the input month has 31 days, only D0 is ON
- If the month input has 30 days, only D1 is ON
- Otherwise, both D0 and D1 are ON.

(Credit: Applied from Mr. Kornkitt P. SE06)

Instructor's signature
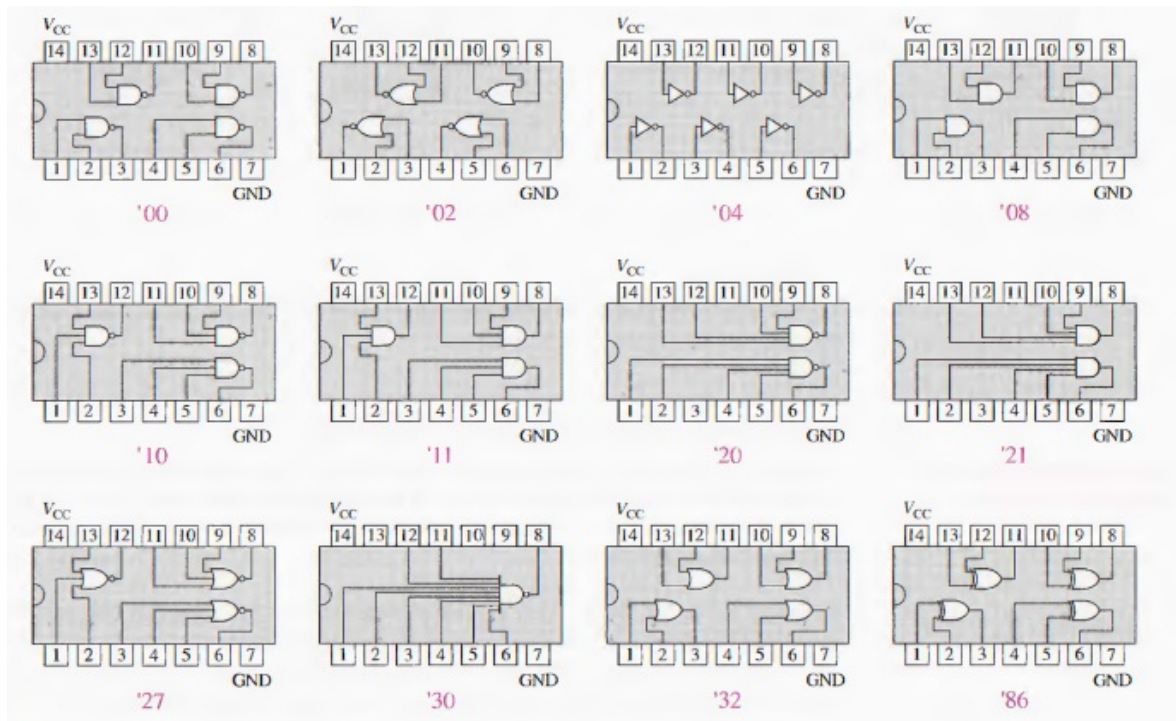
### Logic Diagram of frequently used gates





8.1 The product package machine is built such that it loads the products into the package in the predefined number. If the desired number to be loaded is set to  $n$ , the machine is expected to load the products into the package in the range of  $[n-3, n+3]$ . From the detailed study, an engineer finds that, the machine will only load the products in the range of  $[n-8, n+7]$ . Design a logic circuit for this machine such that it outputs the alarm if the number of loaded products to the package is out of range.


- Construct a truth table
- Construct a Karnaugh map
- Give the corresponding logic equation
- Build the corresponding circuit to show the result

$\rightarrow 0 = \text{No Alarm Signal}$   
 $\rightarrow 1 = \text{Give Alarm Signal}$

AB \ CD	$\bar{C}\bar{D}$	$\bar{C}D$	$CD$	$C\bar{D}$
$\bar{A}\bar{B}$	1	1	1	1
$\bar{A}B$	1	0	0	0
$A\bar{B}$	1	1	1	1
$AB$	0	0	0	0

$$x = \bar{A}\bar{B} + \bar{A}\bar{C}\bar{D} + AB$$
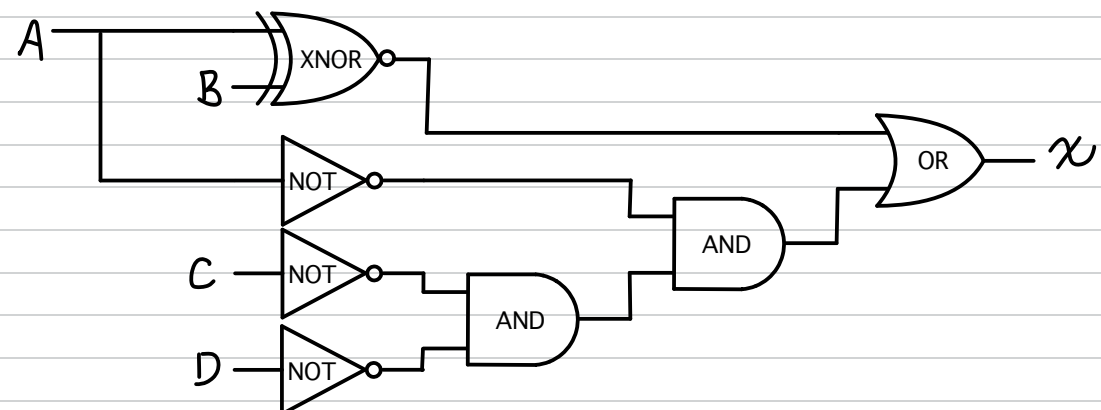
$$= (\bar{A} \oplus B) + \bar{A}\bar{C}\bar{D}$$



	A	B	C	D	x
0	0	0	0	0	1
1	0	0	0	1	1
2	0	0	1	0	1
3	0	0	1	1	1
4	0	1	0	0	1
5	0	1	0	1	0
6	0	1	1	0	0
7	0	1	1	1	0
8	1	0	0	0	0
9	1	0	0	1	0
10	1	0	1	0	0
11	1	0	1	1	0
12	1	1	0	0	1
13	1	1	0	1	1
14	1	1	1	0	1
15	1	1	1	1	1

Perfect number  
for being "n"

8.2 A simple floodgate has a sensor to measure incoming water level, which can be classified into 10 levels, (0-9). The opening height of the floodgate depends on this incoming water level. For water level of 0-3, the floodgate will be at its upper level. For water level of 4-6, the floodgate will be at its middle level, otherwise it will be at its lower level. Construct a logic circuit, which give the alarm signal when the floodgate is at its lower level.


7-9

	A	B	C	D	X
0	0	0	0	0	0
1	0	0	0	1	0
2	0	0	1	0	0
3	0	0	1	1	0
4	0	1	0	0	0
5	0	1	0	1	0
6	0	1	1	0	0
7	0	1	1	1	1
8	1	0	0	0	1
9	1	0	0	1	1
10	1	0	1	0	d
11	1	0	1	1	d
12	1	1	0	0	d
13	1	1	0	1	d
14	1	1	1	0	d
15	1	1	1	1	d

$x \begin{cases} 0 = \text{no alarm signal} \\ 1 = \text{give alarm signal} \end{cases}$

AB \ CD	$\bar{C}\bar{D}$	$\bar{C}D$	$C\bar{D}$	$CD$
$\bar{A}\bar{B}$	0	0	0	0
$\bar{A}B$	0	0	1	0
$A\bar{B}$	d	d	d	d
$AB$	1	1	d	0

$$x = A\bar{C} + BCD$$

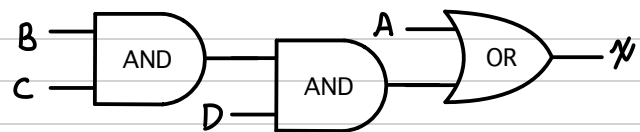

8.3 Construct a minimum circuit which receives BCD inputs indicating the number of month in a year (for example, January is 1, February is 2, and so on). The circuit shall have the following functions:

- If the input month has 31 days, only D0 is ON
- If the month input has 30 days, only D1 is ON
- Otherwise, both D0 and D1 are ON.

(Credit: Applied from Mr. Kornkitt P. SE06)

	A	B	C	D	w	x	y	z	D <sub>0</sub>	D <sub>1</sub>
0	0	0	0	0	0	0	0	0	1	1
1	0	0	0	0	0	0	0	1	1	0
2	0	0	0	0	0	0	1	0	1	1
3	0	0	0	0	0	0	1	1	1	0
4	0	0	0	0	0	1	0	0	0	1
5	0	0	0	0	0	1	0	1	1	0
6	0	0	0	0	0	1	1	0	0	1
7	0	0	0	0	0	1	1	1	1	0
8	0	0	0	0	1	0	0	0	1	0
9	0	0	0	0	1	0	0	1	0	1
	1	1	1	1	1	1	1	1	1	1
	1	1	1	1	1	1	1	1	1	1
	1	1	1	1	1	1	1	1	1	1
10	0	0	0	1	0	0	0	0	1	0
11	0	0	0	1	0	0	0	1	0	1
12	0	0	0	1	0	0	1	0	1	0
	1	1	1	1	1	1	1	1	1	1
	1	1	1	1	1	1	1	1	1	1

$$D_0 = F(\Delta, w, x, y, z) = G(\Delta, w, x, y).$$

$$D_1 = H(\Delta, w, x, y, z) = I(w, x, y, z).$$

$\Delta y$	$\bar{x}\bar{y}$	$\bar{x}y$	$x\bar{y}$	$xy$
$\bar{\Delta}\bar{w}$	$\bar{z} + \bar{z}d$	1	$z$	$z$
$\bar{\Delta}w$	$\bar{z}$	$d$	$d$	$d$
$\Delta w$	$d$	$d$	$d$	$d$
$\Delta\bar{w}$	$\bar{z}$	$\bar{z} + zd$	$d$	$d$

$y z$	$\bar{x}\bar{y}$	$\bar{x}y$	$x\bar{y}$	$xy$
$\bar{\Delta}\bar{w}$	$\bar{z} + \bar{z}d$	$\bar{z}$	$\bar{z}$	$\bar{z}$
$\bar{\Delta}w$	$z$	$d$	$d$	$d$
$\Delta w$	$d$	$d$	$d$	$d$
$\Delta\bar{w}$	$z$	$z + zd$	$d$	$d$

$$\therefore D_0 = \bar{x}z + \bar{\Delta}\bar{w}z + yz$$

$$D_1 = \bar{\Delta}\bar{w}\bar{z} + wz + \Delta z$$

$$= (\bar{\Delta}\bar{w} + x + y)z$$

$$= \bar{\Delta}\bar{w}\bar{z} + (w + \Delta)z$$

$$= \bar{\Delta}\bar{w}\bar{z} + \bar{w}\bar{\Delta}z$$

$$= (\bar{\Delta}\bar{w} \oplus \bar{z})$$

A  
B  
C

No need to connect  
because it does not  
affect the result.

