 


8 Counters


COUNTERS

- The counter is consisted of a number of n toggle flip-flops connected in cascade;
- The output of the Individual flip-flops will be toggled in sequence;
- And produces n -bit binary number, which increases/decreases by one;
- This forms a **Counter**;
- and be called the **Binary Counter**.



- For example,
- if we want to count 8 or 2^3 (3-bit binary numbers);
- We need to use 3 Toggle Flip-Flops connected in cascade;
- The circuit can generate 3-bit binary signals from 000 to 111;

Asynchronous Counter [4]

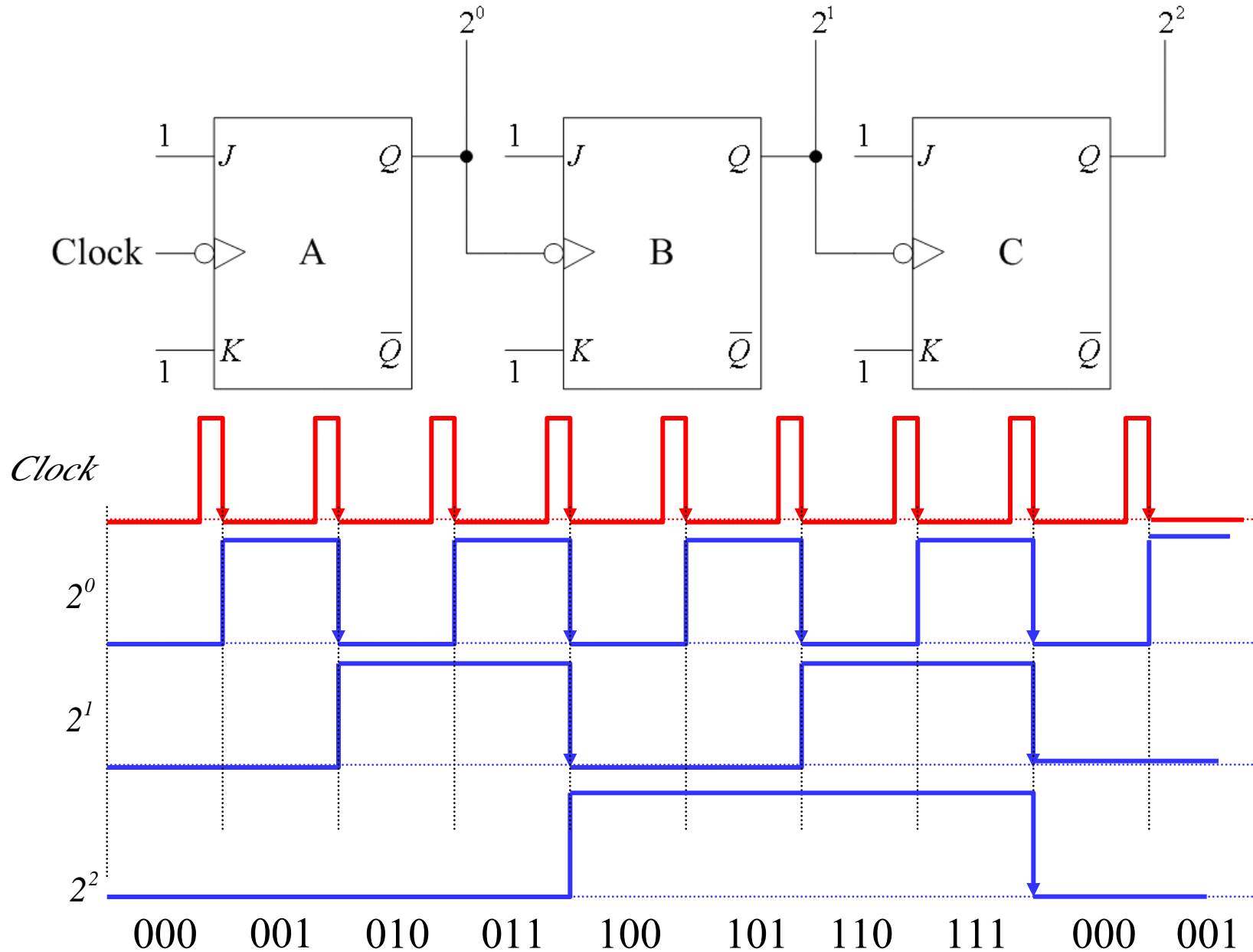

COUNTERS

- In the binary counting, the number of counting is called **Modulus (Mod)**.
- For example, a 3-bit circuit (000 to 111) has **8 countable values**, so **Modulus = 8**;
- This circuit is called the **Mod 8 counter**.
- Basically, the mod can be determined by the number of bits (or flip-flops) in counting.
 - **Mod = 2^n** where n = number of bits used in counting (number of flip-flops);
 - Start counting from 0;
 - Maximum counting value = $2^n - 1$
- e.g. 3-bit Counter would be Mod 8,
 - Start counting from 0;
 - the maximum can be counted is 7



COUNTERS: Types

- Sometimes we need to count **less** than 2^n , i.e. 4, 8, 16..
- e.g. count in a decimal digits.
- We can do it by designing a counter with Mod N , where $N \leq 2^n$;
- Where n is the number of bits (or Flip-flops) in counting;
- We can complete this counter by **the way to activate the operation by the clock:**
 - **Asynchronous Counter**
 - Clock triggering one by one,
 - Use **n clocks**.
 - **Synchronous Counter**
 - Clock triggering simultaneously,
 - Use only **ONE** clock.
- However, the types of counter can be divided by **the direction of counting counter**
 - Up Counter
 - Down Counter


Asynchronous Counter [1]

Asynchronous Counter or Ripple Counter

- Counter that has the Toggle Flip-Flops connecting in cascade;
 - Every Flip-Flop, except the last one, will send its output signal as the clock signal to the next flip-flop;
 - which means each Flip-Flop in the circuit **Asynchronous** **does not work at the same time**;
 - **[Advantages]** Easy to design. Just connecting FF in cascade.
 - **[Disadvantages]** Error in Counting is easily occurred if using a high frequency clock.
 - **[Disadvantages]** The working time of the counter is equal to the sum of the working time of all Flip-Flops.
- Counting of larger modulus has more delay time than that of less bits.


Asynchronous Counter [2]

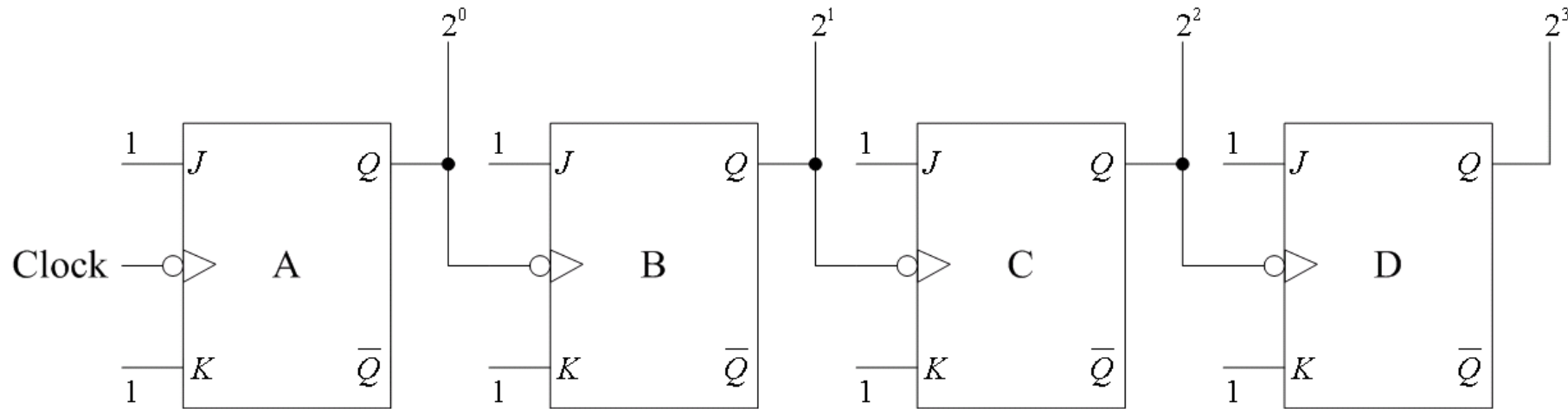This is an example of an asynchronous 4-bit counter.




- Use 4 T Flip-flops connecting in cascade;
- Every flip-flop would send its output signal as the clock signal to the next flip-flop.

Asynchronous Counter [3]

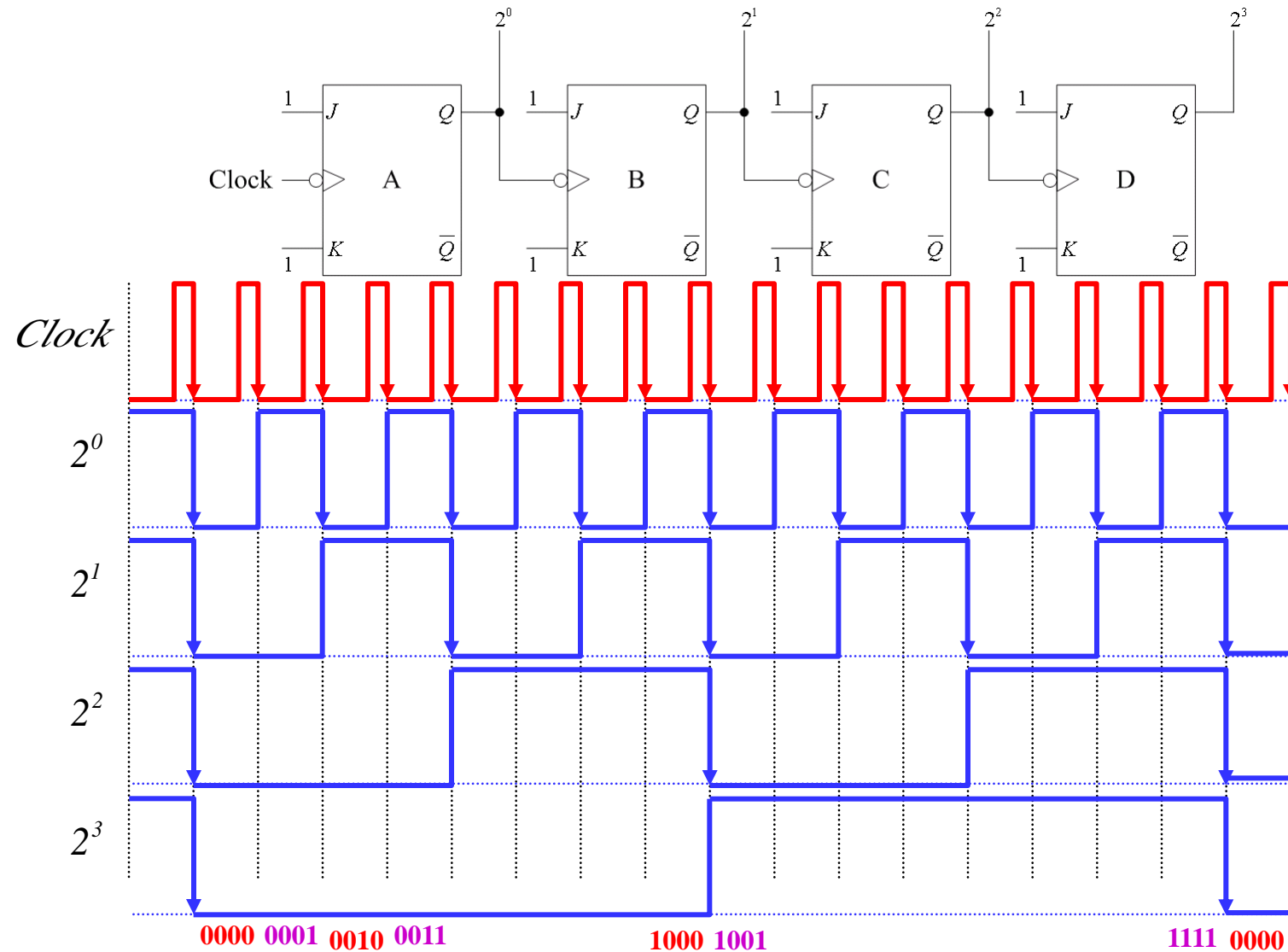


Asynchronous Counter [4]

The ideal case:
No Problem.

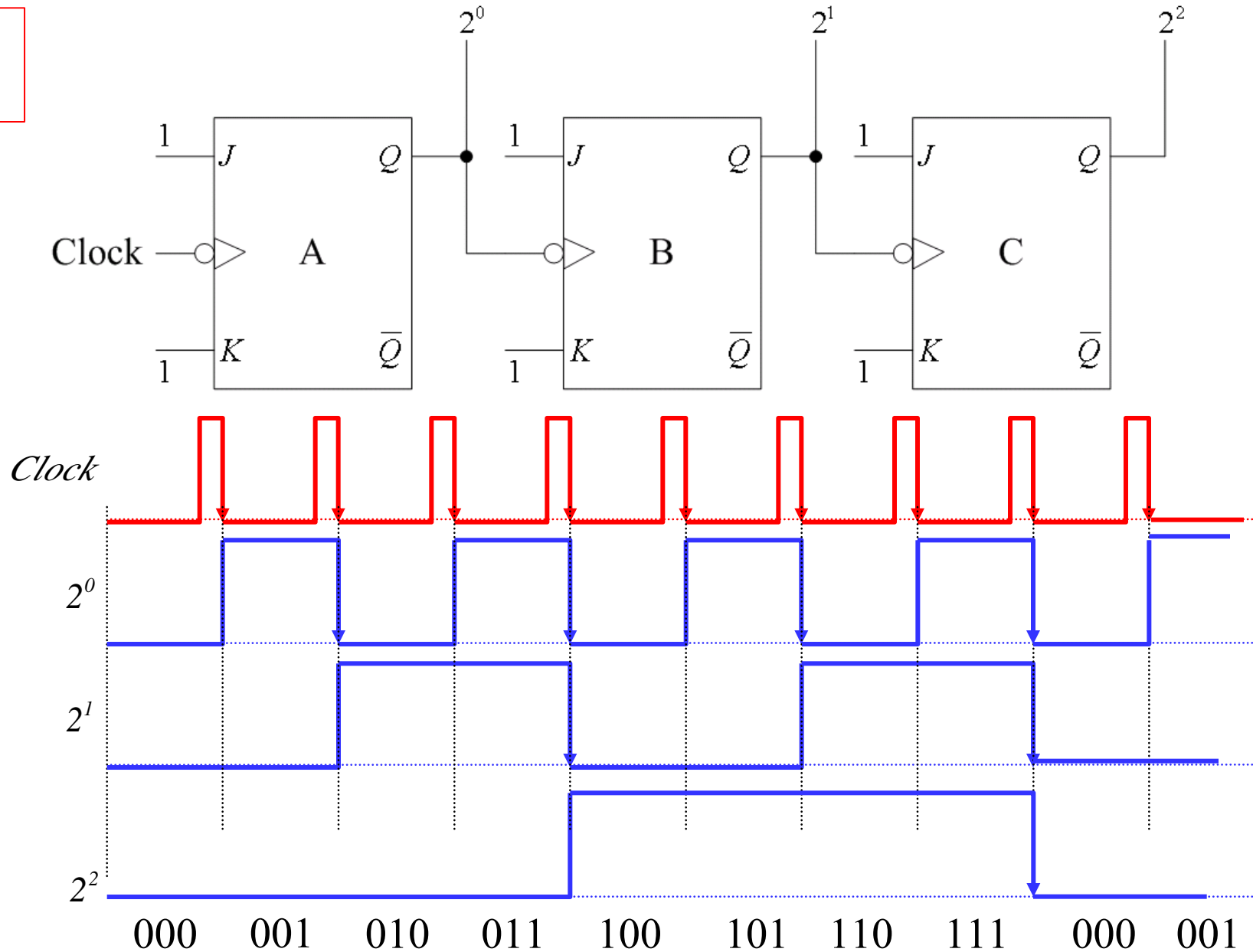

Asynchronous Counter [5]

The real case:
Problem occurs

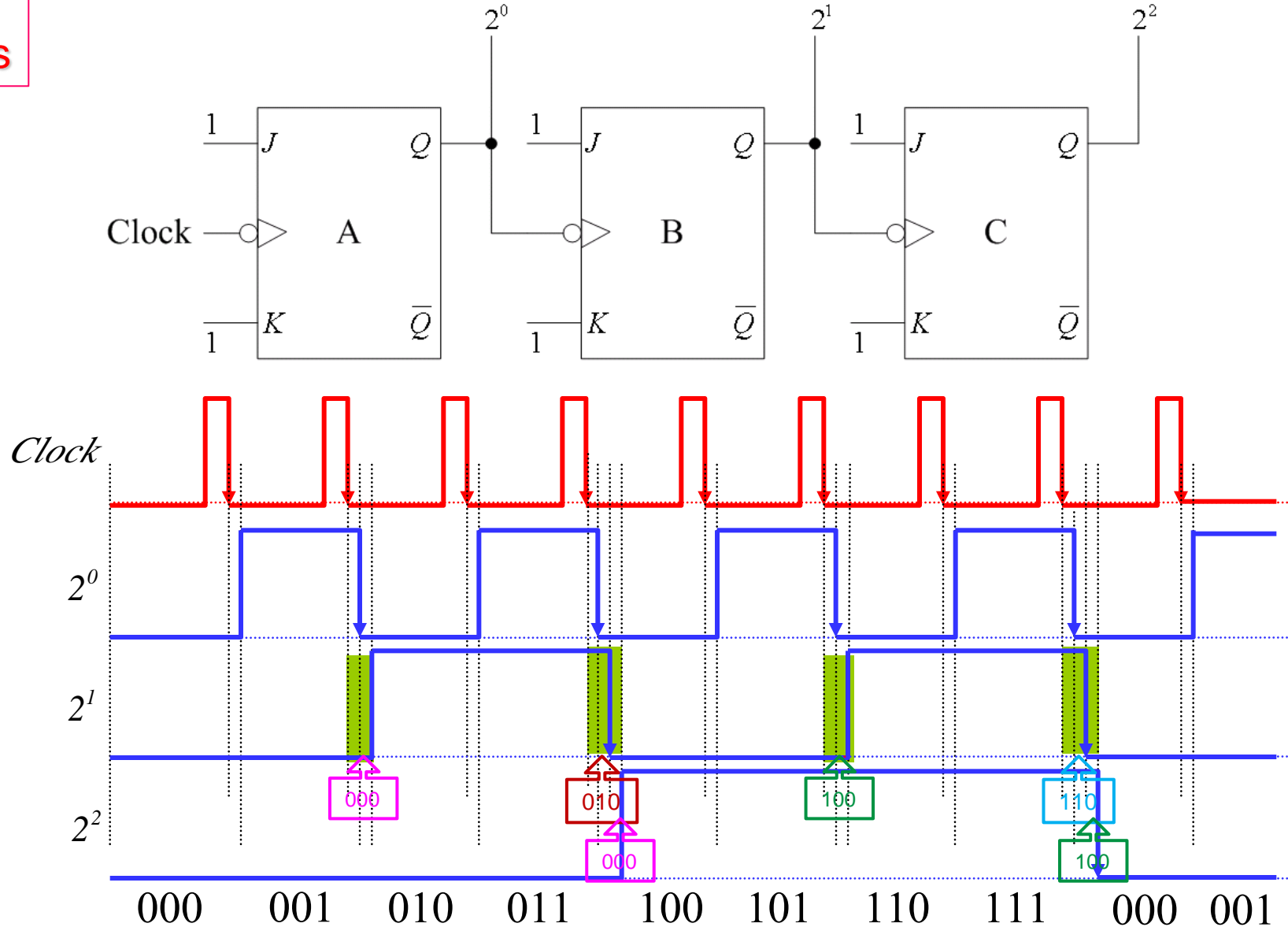


Synchronous Counter [1]

- To control ALL Flip-Flops to operation **simultaneously**;
- Using ONE clock signal (the clock signal is applied to every Flip-flop).
- In conjunction with the control signal circuit (**has to be designed**) for the desired operation;
- The counting output has the delay time that caused from only ONE Flip-flop;
- **Advantages:**
 - The operation time of the circuit is equal to the single Flip-Flop delay time.
 - Less error occurs
 - Able to operate in a higher or faster frequency.
- **Disadvantages:**
 - Require to design of the control circuits (**complicated**).

Synchronous Counter [2]

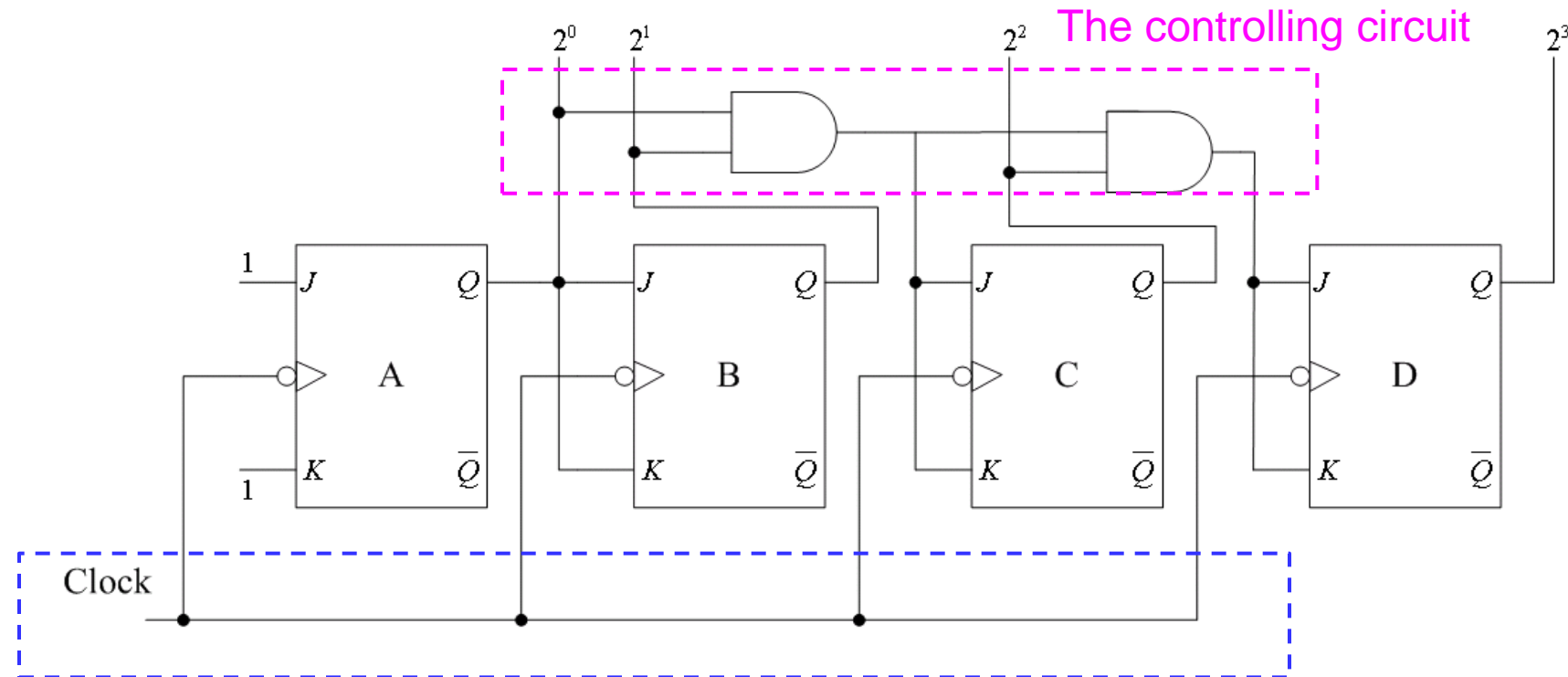Example of 4-Bit Binary Synchronous Counter Circuit



The clock signal triggers ALL flip-flops providing operation at the same time.

Synchronous Counter: Control circuit

- The operation of the circuit is to control the output to be changed as needed
- e.g. Suppose we want to change the Flip-flop output from 0 to 1:
- How to apply the inputs:
 - In In generate the case of D- Flip-flop: Enter D with 1
 - And for JK Flip-flop : Enter $J = 1$ and $K = 0$ or $K = 1$ ($K = \text{don't care}$)
 - Or for al usage of JK Flip-Flop: May activate the Preset.

Truth Table for a negative edge-triggered JK flip-flop

J	K	C	Q	\bar{Q}	State
1	0	\downarrow	1	0	Set
0	1	\downarrow	0	1	Reset
0	0	X	Q	\bar{Q}	Unchanged
1	1	\downarrow	\bar{Q} / Q		Toggle

Truth Table for a negative edge-triggered JK flip-flop

Conditions		Control		
<i>Before clock</i>	<i>After clock</i>	<i>Before clock</i>		
<i>Present Q</i>	<i>Next Q</i>	<i>State</i>	<i>J</i>	<i>K</i>
0	0	<u>N.C.</u> Reset	0	×
0	1	<u>Set</u> Toggle	1	×
1	0	<u>Reset</u> Toggle	×	1
1	1	<u>N.C.</u> Set	×	0

Synchronous Counter Design

The Steps for Designing a Synchronous Counter.

1. Assign the desired counting (output) table.
2. Make the truth table for finding the input (J and K) of every Flip-Flop from the given output, and the excitation table of Flip-Flop (if using JK Flip-Flop).
3. Use the truth table to find the input for the Flip-Flops (in the form of an equation) using Boolean Algebra / Karnaugh Map.
4. Use the equation to create the circuit.

Synchronous Counter Design: Example

1 Assign the desired counting (output) table.

The counting follows this sequence:

0 → 1

1 → 2

2 → 3

3 → 4

⋮

7 → 0

And get the table beside:

Present State			Next State		
Q_C	Q_B	Q_A	Q_C	Q_B	Q_A
0	0	0	0	0	1
0	0	1	0	1	0
0	1	0	0	1	1
0	1	1	1	0	0
1	0	0	1	0	1
1	0	1	1	1	0
1	1	0	1	1	1
1	1	1	0	0	0

Synchronous Counter Design: Example

2 Make the truth table for finding the input (J and K) of every Flip-Flop from the given output, and the excitation table of Flip-Flop (if using JK Flip-Flop).

P.S.			N.S.			C		B		A	
Q_C	Q_B	Q_A	Q_C	Q_B	Q_A	J_C	K_C	J_B	K_B	J_A	K_A
0	0	0	0	0	1	0	X	0	X	1	X
0	0	1	0	1	0	0	X	1	X	X	1
0	1	0	0	1	1	0	X	X	0	1	X
0	1	1	1	0	0	1	X	X	1	X	1
1	0	0	1	0	1	X	0	0	X	1	X
1	0	1	1	1	0	X	0	1	X	X	1
1	1	0	1	1	1	X	0	X	0	1	X
1	1	1	0	0	0	X	1	X	1	X	1

	00	01	11	10
0				
1				

	00	01	11	10
0				
1				

Synchronous Counter Design: Example

- Consider the output from Q changing from **0** → **0**

P.S.			N.S.			C		B		A	
Q_C	Q_B	Q_A	Q_C	Q_B	Q_A	J_C	K_C	J_B	K_B	J_A	K_A
0	0	0	0	0	1	0	X	0	X	1	X
0	0	1	0	1	0	0	X	1	X	X	1
0	1	0	0	1	1	0	X	X	0	1	X
0	1	1	1	0	0	1	X	X	1	X	1
1	0	0	1	0	1	X	0	0	X	1	X
1	0	1	1	1	0	X	0	1	X	X	1
1	1	0	1	1	1	X	0	X	0	1	X
1	1	1	0	0	0	X	1	X	1	X	1

Synchronous Counter Design: Example

□ Consider the output from Q changing from **1** → **0**

P.S.			N.S.			C		B		A	
Q_C	Q_B	Q_A	Q_C	Q_B	Q_A	J_C	K_C	J_B	K_B	J_A	K_A
0	0	0	0	0	1	0	X	0	X	1	X
0	0	1	0	1	0	0	X	1	X	X	1
0	1	0	0	1	1	0	X	X	0	1	X
0	1	1	1	0	0	1	X	X	1	X	1
1	0	0	1	0	1	X	0	0	X	1	X
1	0	1	1	1	0	X	0	1	X	X	1
1	1	0	1	1	1	X	0	X	0	1	X
1	1	1	0	0	0	X	1	X	1	X	1

Synchronous Counter Design: Example

3 From the truth table, write the Karnaugh Map to find the input equations for the individual Flip-Flops, e.i. J_A , K_A , J_B , K_B , J_C and K_C

		BA			
		00	01	11	10
J_C	0	0	0	1	0
	1	X	X	X	X

$$J_C = AB$$

		BA			
		00	01	11	10
K_C	0	X	X	X	X
	1	0	0	1	0

$$K_C = AB$$

Synchronous Counter Design: Example

		BA			
		00	01	11	10
J_B	0	0	1	X	X
	1	0	1	X	X

$$J_B = A$$

		BA			
		00	01	11	10
K_B	0	X	X	1	0
	1	X	X	1	0


$$K_B = A$$

Synchronous Counter Design: Example

		BA				
		00	01	11	10	
J_A	C	0	1	X	X	1
	C	1	1	X	X	1

		BA				
		00	01	11	10	
K_A	C	0	X	1	1	X
	C	1	X	1	1	X

Synchronous Counter Design: Example

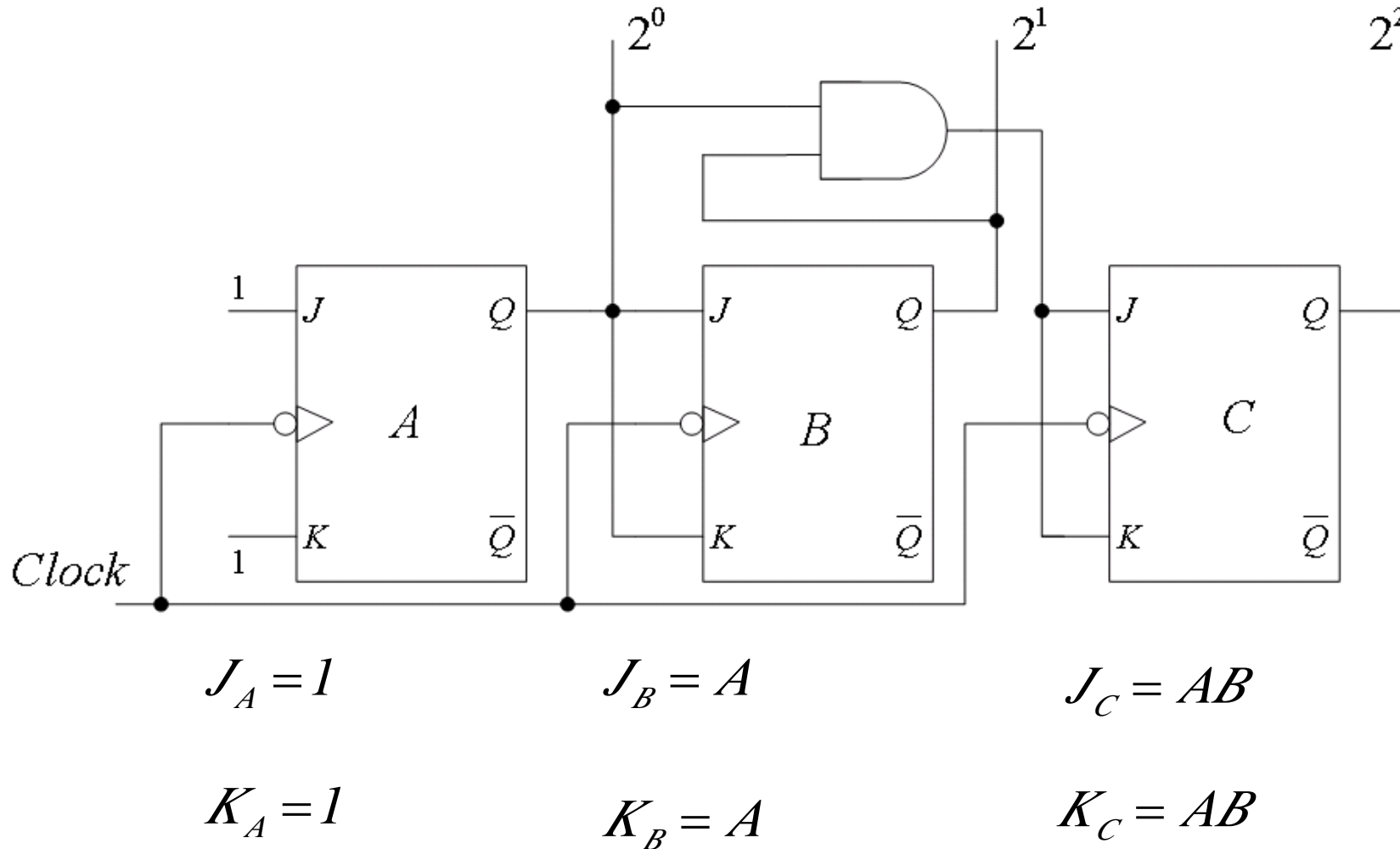

Modulus N (Mod- N) Counter

□ The Mod- N counter is the counter that counts N numbers:

- Basically, a normal n -bit BINARY counter;
- Where $N \leq 2^n$

e.g.

- The Mod-8 counter is 3-bit counter that produces the sequence of 0, 1, 2, ..., 7
- The Mod-5 counter is 3-bit counter that produces the sequence of 0, 1, 2, 3, 4
- So, Mod-5 = Mod-8 + Control circuit.

□ If we want to design Mod-10 counter:


- $10 \leq 2^4$
- Require 4-bit counter with a control circuit.

Asynchronous Mod-N Counter

- Asynchronous Mod-N Counter is the same as the typical binary counter;
- When it reaches the desire maximum, then use it to reset counting to 0;
- By activating the clear input (Sending 0 to $\overline{\text{CLR}}$ pin);



[Need to observe the desire maximum to produce a control signal for $\overline{\text{CLR}}$ pin]

Asynchronous Mod-5 Counter

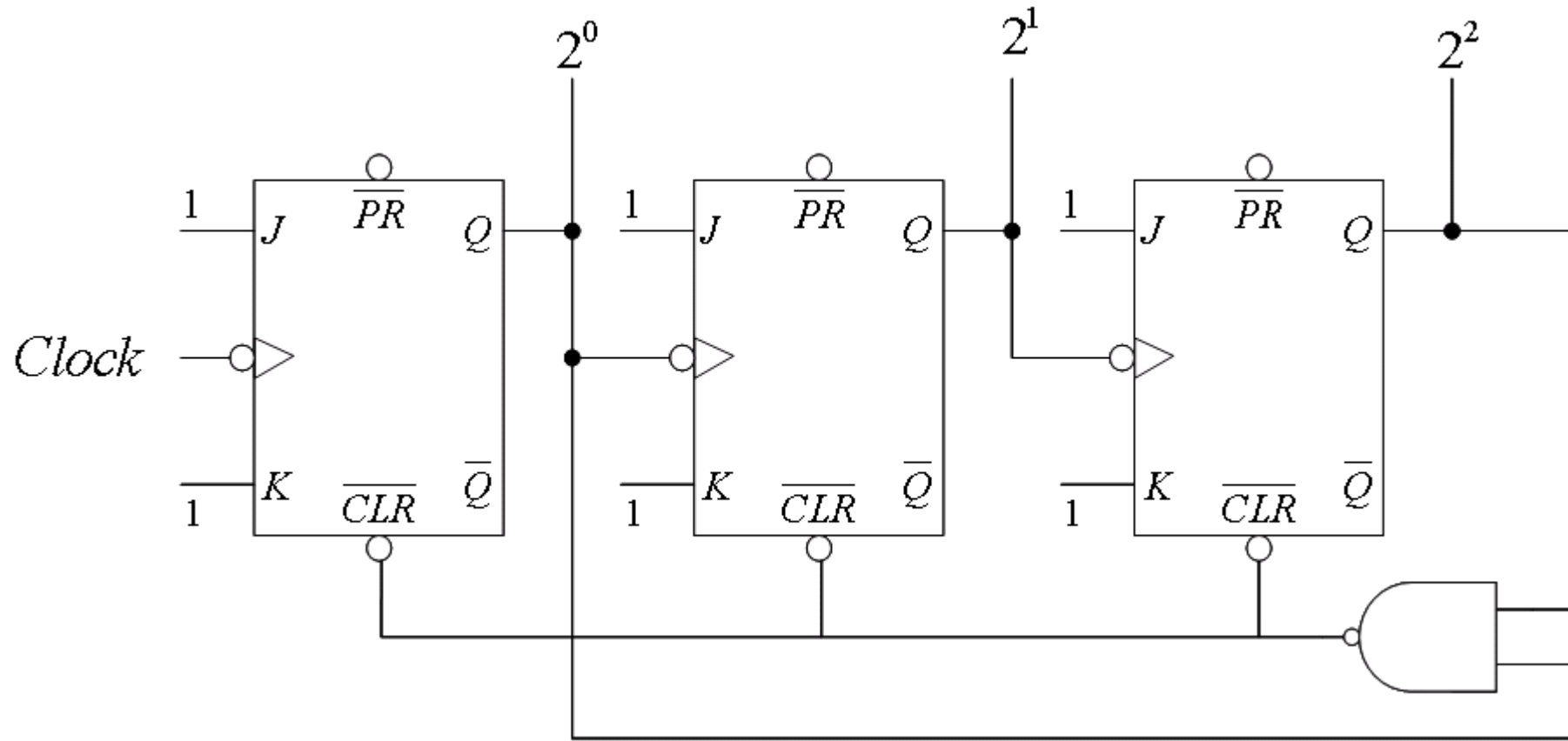


Q_C	Q_B	Q_A
0	0	0
0	0	1
0	1	0
0	1	1
1	0	0
1	0	1

Asynchronous Mod-5 Counter

  


Asynchronous Mod-6 Counter

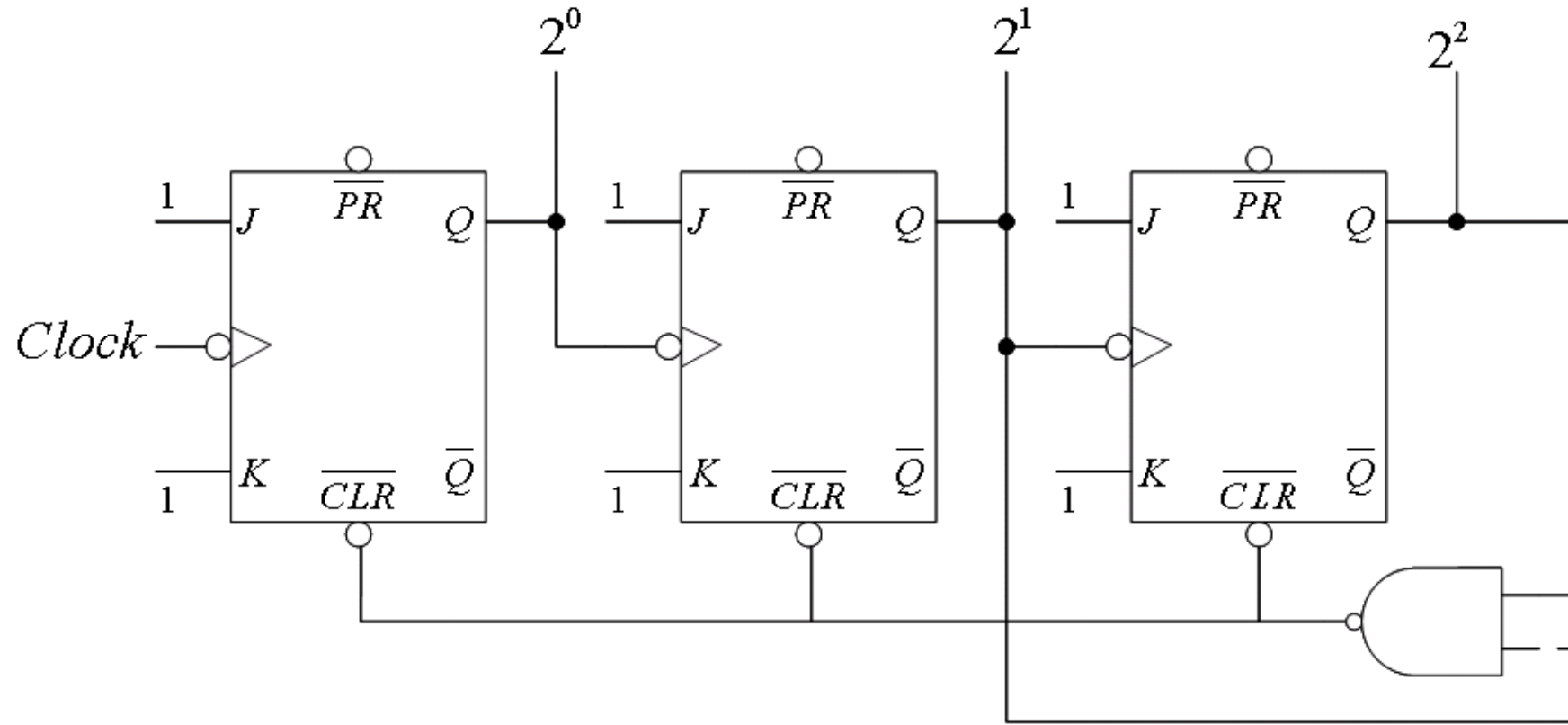

Q_C	Q_B	Q_A
0	0	0
0	0	1
0	1	0
0	1	1
1	0	0
1	0	1
1	1	0

Asynchronous Mod-6 Counter

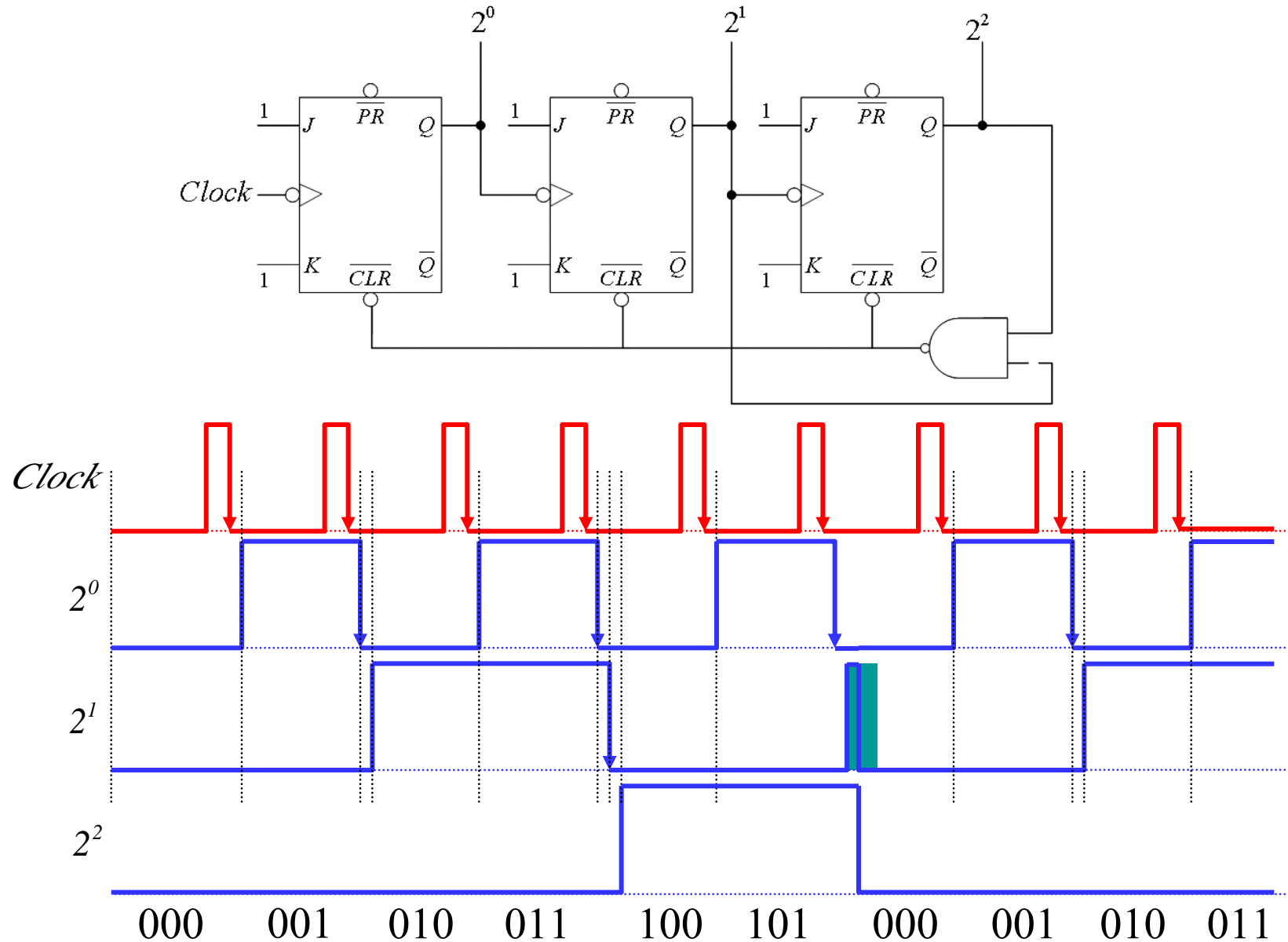

Synchronous Mod-N Counter


- The design is the same as normal synchronous counter circuit design,
- by counting the number as assigned.

Qc	Qb	Qa	Qc	Qb	Qa	Jc	Kc	Jb	Kb	Ja	Ka
0	0	0	0	0	1	0	x	0	x	1	x
0	0	1	0	1	0	0	x	1	x	x	1
0	1	0	0	1	1	0	x	x	0	1	x
0	1	1	1	0	0	1	x	x	1	x	1
1	0	0	0	0	0	x	1	0	x	0	x

	00	01	11	10
0				
1				

	00	01	11	10
0				
1				

Synchronous Mod-5 Counter

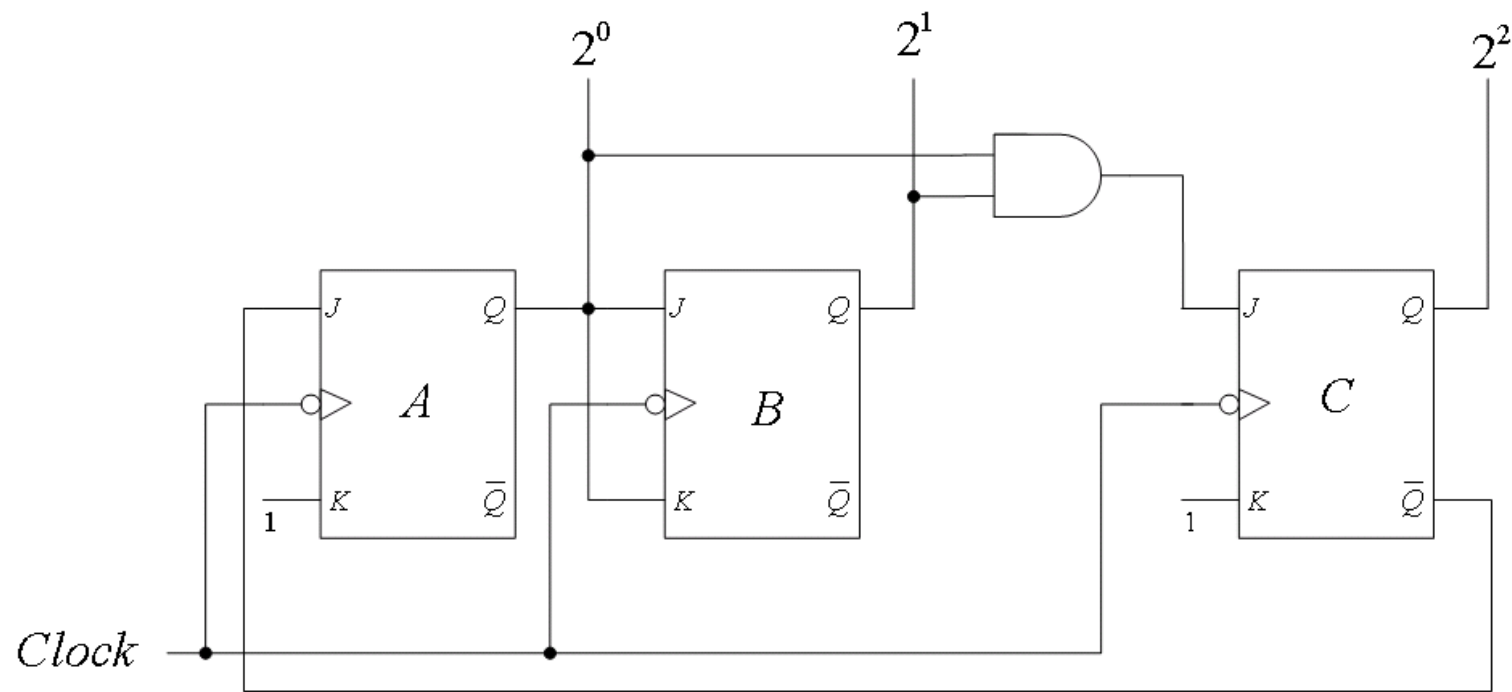

$$J_A = \bar{C}$$

$$J_B = A$$


$$J_C = AB$$

$$K_A = 1$$

$$K_B = A$$

$$K_C = 1$$

Synchronous Mod-6 Counter

 

$$J_A = 1$$

$$J_B = \bar{A}\bar{C}$$

$$J_C = AB$$

$$K_A = 1$$



$$K_B = A$$

$$K_C = A$$

DOWN Counter

- The circuit that counts downward from max to min e.g. 111, 110, 101,..., 000.
- Asynchronous Down Counter
 - Similar to the Asynchronous Counter,
 - Using \bar{Q} as a clock signal to trigger the next Flip-Flops, instead of Q .
- Synchronous Down Counter
 - The design principles are like a synchronous counter.
 - Follow the truth table assigned to design the control unit.

Asynchronous Down Counter

  


Synchronous Down Counter

Qc	Qb	Qa	Qc	Qb	Qa	Jc	Kc	Jb	Kb	Ja	Ka
0	0	0	1	1	1	1	x	1	x	1	x
1	1	1	1	1	0	x	0	x	0	x	1
1	1	0	1	0	1	x	0	x	1	1	x
1	0	1	1	0	0	x	0	0	x	x	1
1	0	0	0	1	1	x	1	1	x	1	x
0	1	1	0	1	0	0	x	x	0	x	1
0	1	0	0	0	1	0	x	x	1	1	x
0	0	1	0	0	0	0	x	0	x	x	1

	00	01	11	10
0				
1				

	00	01	11	10
0				
1				

 

How to Design ^{Synchronous} 3-bit Down Counter

①

P.S			N.S			J_C	K_C	J_B	K_B	J_A	K_A
C	B	A	C	B	A						
1	1	1	1	1	0	x	0	1	0	x	1
1	1	0	1	0	1	x	0	x	1	1	x
1	0	1	1	0	0	x	0	0	x	x	1
1	0	0	0	1	1	x	1	1	x	1	x
0	1	1	0	1	0	0	x	x	0	x	1
0	1	0	0	0	1	0	x	x	1	1	x
0	0	1	0	0	0	0	x	1	x	x	1
0	0	0	1	1	1	1	x	1	x	x	1

②

C	B	A
0	0	0
0	0	1
0	1	0
0	1	1
1	0	0
1	0	1
1	1	0
1	1	1

$$J_C = \bar{A} \bar{B}$$

$$K_C = \bar{A} \bar{B}$$

$$J_B = \bar{A}$$


$$K_B = A$$

$$J_A = 1$$

$$K_A = 1$$



 

Synchronous Down Counter




Synchronous Up-Down Counter

- Able to count UP or DOWN in the same circuit;
- By a control unit to the selection the direction to count (up or down);
- This counter could be uses counting the number of cars in the car park.


CLOCK PULSE	UP	Q_2	Q_1	Q_0	DOWN
0		0	0	0	
1		0	0	1	
2		0	1	0	
3		0	1	1	
4		1	0	0	
5		1	0	1	
6		1	1	0	
7		1	1	1	

Synchronous Up-Down Counter

**Mod-8 UP
Counter**

 

**Mod-8 DOWN
Counter**

 

Synchronous Up-Down Counter

