

1) Draw the signals of the outputs Q_1 , $\overline{Q_1}$ and Q_2 when applying the signals A , B and C to the circuit.

