

Design a logic circuit using the PAL16P8 with multiple outputs as following equations:

$$F1(A, B, C, D) = \sum m(1, 2, 10, 12, 13, 15) \qquad F2(A, B, C, D) = \sum m(3, 10, 11, 13, 14, 15)$$

$$F_3(A, B, C, D) = \sum m(0, 2, 3, 7, 8, 10, 11)$$

