

Name: Student ID:


Name: Student ID:

Laboratory 10

Flip-Flops

1. S-R Flip-Flop:

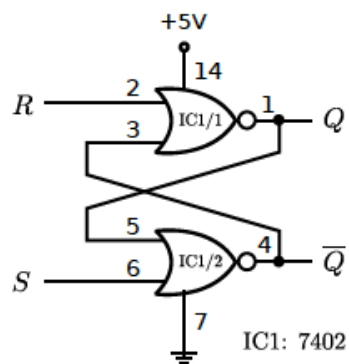- 1.1 Connect a logic circuit as shown in the following figure. The input should be connected to the logic switches and the output should be connected to logic monitor.




- 1.2 Supply the logic to the input S and R as shown in the following figure. Record the results.

S	R	Q	Q'	State
0	0			
0	1			
1	0			
1	1			

Instructor's signature

2. J-K Flip-Flop, T Flip-Flop, D Flip-Flop:

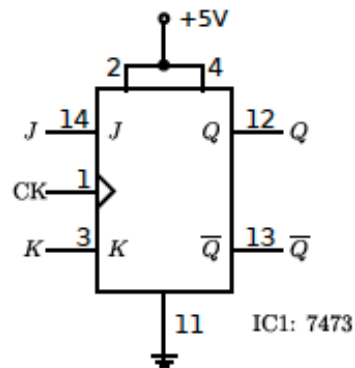2.1 Connect the circuit as shown in the following figure. The CK input should be connected to output 1 of a debounce switch.




2.2 CK=1 refers to the state where the debounce switch is not pressed and CK=0 refers to the state where the debounce switch is pressed and the pulse is supplied to pin CK.

2.3 Record the results in the following table.

Input			Output		
J	K	CK	Q	Q'	State
0	0	0			
0	0	1			
0	1	0			
0	1	1			
1	0	0			
1	0	1			
1	1	0			
1	1	1			

Instructor's signature

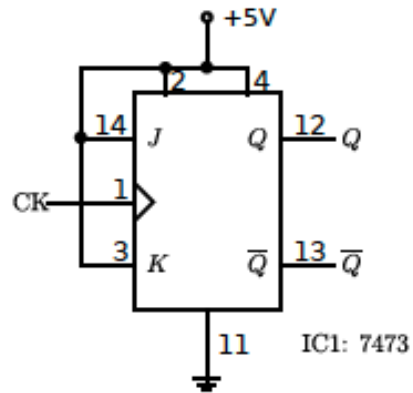2.4 Connect the circuit as shown in the following figure.



2.5 Supply a pulse using a debounce switch as shown in the following table.


2.6 Observe and record the status of Q and Q'

CK	Q	Q'
1		
0		
1		
0		

2.7 Name the type of this flip-flop

Instructor's signature

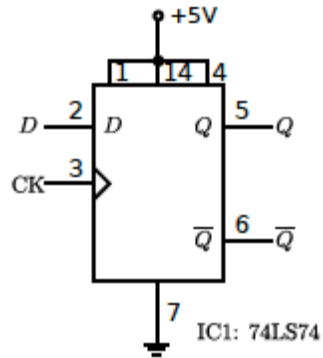2.7 Connect the circuit as shown in the following figure.



2.8 Connect pin CK to the output 1 of the debounce switch. Connect pin D to the logic switch and the output Q and Q' to the logic monitor.

2.9 CK=0 refers to the state where the debounce switch is not pressed. CK=1 refers to the state where the debounce switch is pressed **one time** to supply the pulse to CK. Record the results in the following table.

D	CK	Q	Q'
0	0		
1	0		
1	1		
0	0		
0	1		

Instructor's signature

3. Assignments:

3.1 Construct a logic circuit which can add two 2-bits binary numbers according to the following conditions:

- a) Receive the first 2-bits binary number by using SW7 and SW6 where SW7 is the MSB.
- b) To get the next input, press debounce switch to supply the rising edge for the CLK signal
- c) Get the second 2-bits number by using the SW7 and SW6 again.
- d) Show the results using logic monitors. Use D7 and D6 to display the sum and D5 to display the carry out.

Instructor's signature

3.2 Given an IC 7474, dual D-type positive-edge-triggered flip-flops with preset and clear. Show the procedure and a logic circuit to obtain a **J-K flip-flop** using this given IC and additional necessary gates.

Instructor's signature

3.3 Given an IC 7474, dual D-type positive-edge-triggered flip-flops with preset and clear. Show the procedure and a logic circuit to obtain a **S-R flip-flop** using this given IC and additional necessary gates.

Instructor's signature

Logic Diagram of frequently used gates