

Name: Theepakorn Phayomrat Student ID: 67011351

Name: \_\_\_\_\_ Student ID: \_\_\_\_\_


## Laboratory 7

### NOR Gate and NAND Gate

---


#### 1. NOR-Gate:

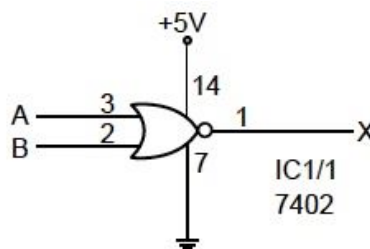- 1.1 Connect a logic circuit as shown in the figure below. Use the logic switches to supply input signals as specified. Connect the output signals to the logic monitor and record the results for each input pairs.




A	B	X
0	0	1
0	1	0
1	0	0
1	1	0

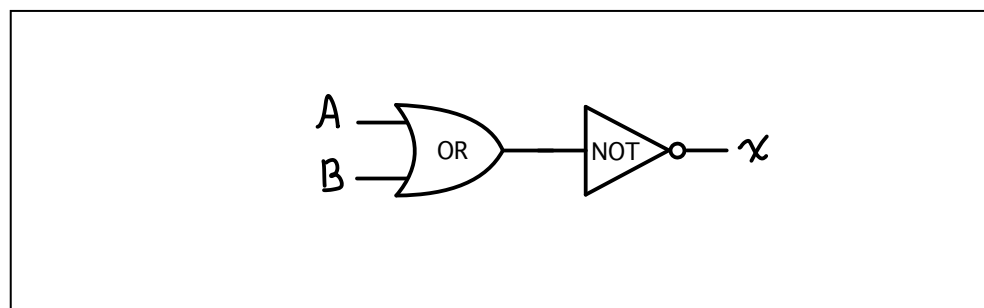- 1.2 Draw an equivalent circuit of NOR gate using basic gates (AND, OR and NOT gates)




Instructor's signature

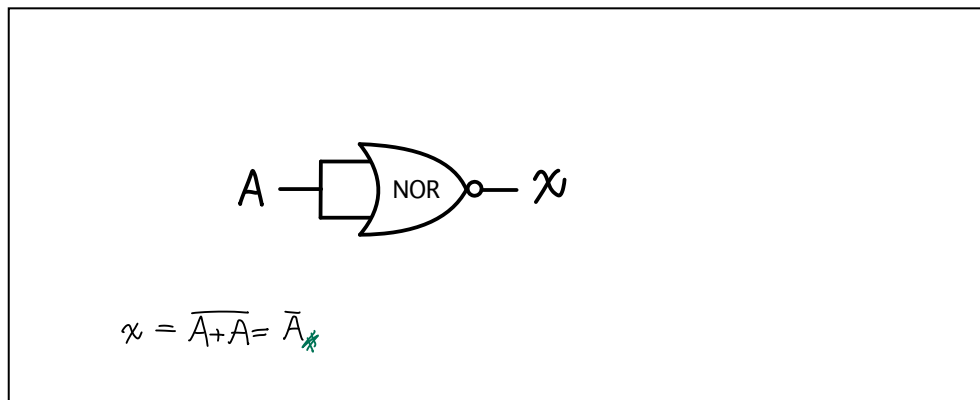1.3 Draw and construct a *NOT* gate using only *NOR* gate. Prove your answer using Boolean algebra.




Instructor's signature

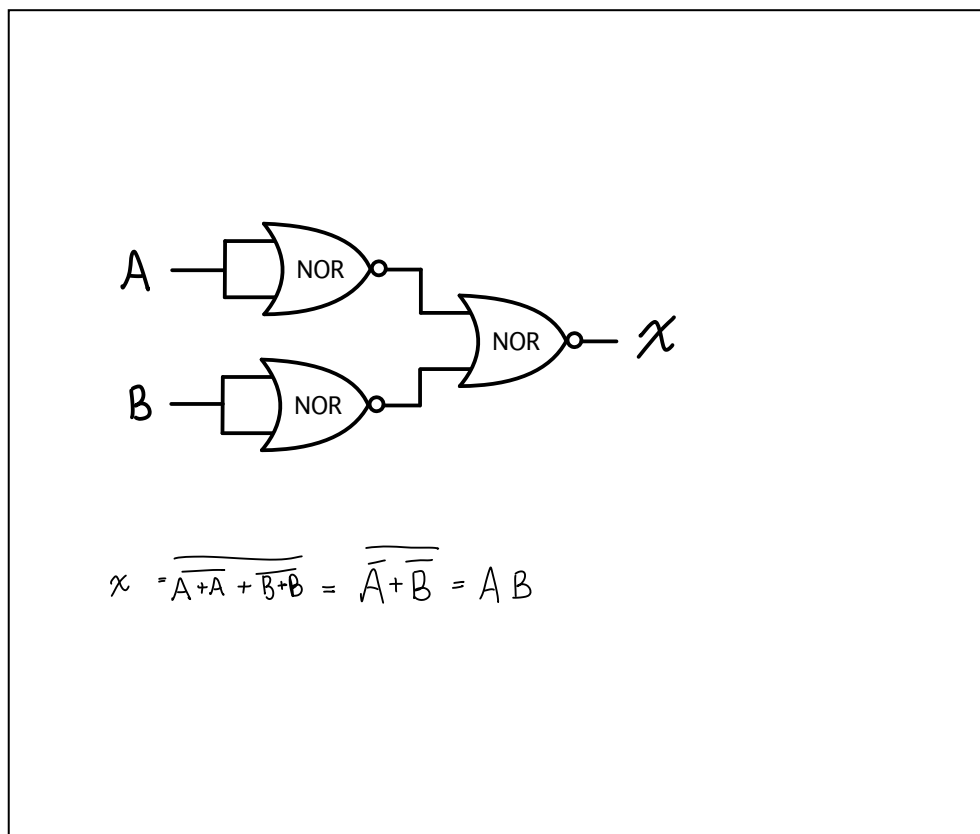1.4 Draw and construct an *AND* gate using only *NOR* gate. Prove your answer using Boolean algebra.



Instructor's signature

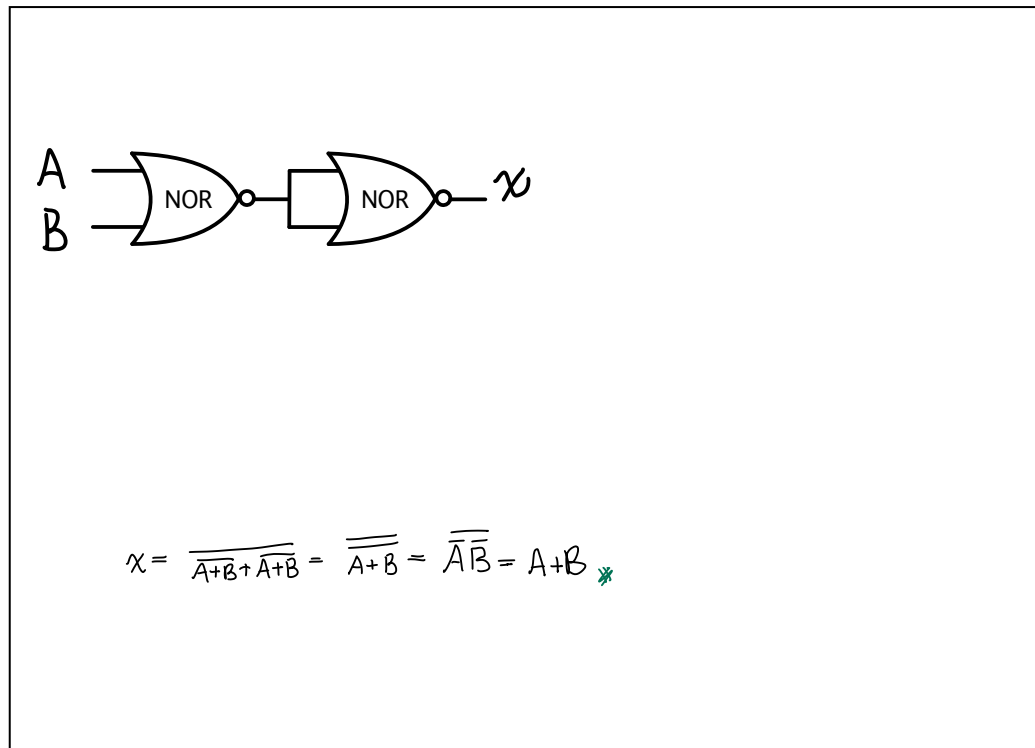1.5 Draw and construct an OR gate using only NOR gate. Prove your answer using Boolean algebra.




Instructor's signature

Sugar


2. NAND-Gate:

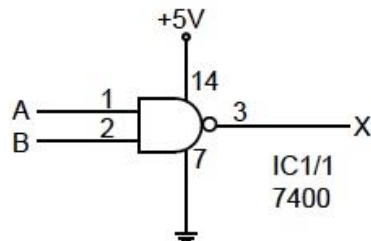2.1 Connect a logic circuit as shown in the figure below. Use the logic switches to supply input signals as specified. Connect the output signals to the logic monitor and record the results for each input pairs.



A	B	X
0	0	1
0	1	1
1	0	1
1	1	0

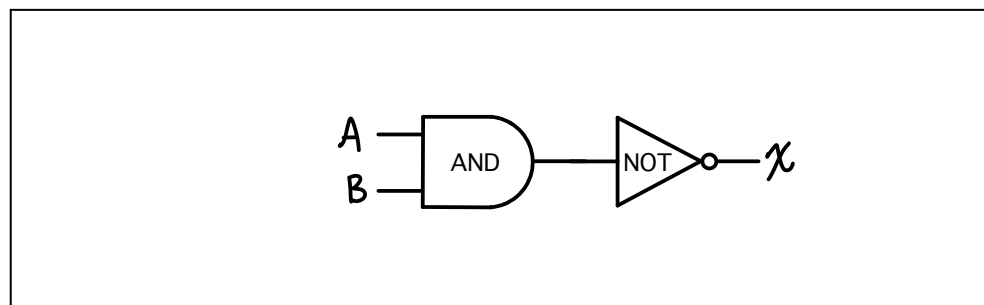2.2 Draw an equivalent circuit of *NAND* gate using basic gate (*AND*, *OR* and *NOT* gates)




Instructor's signature

Sagar



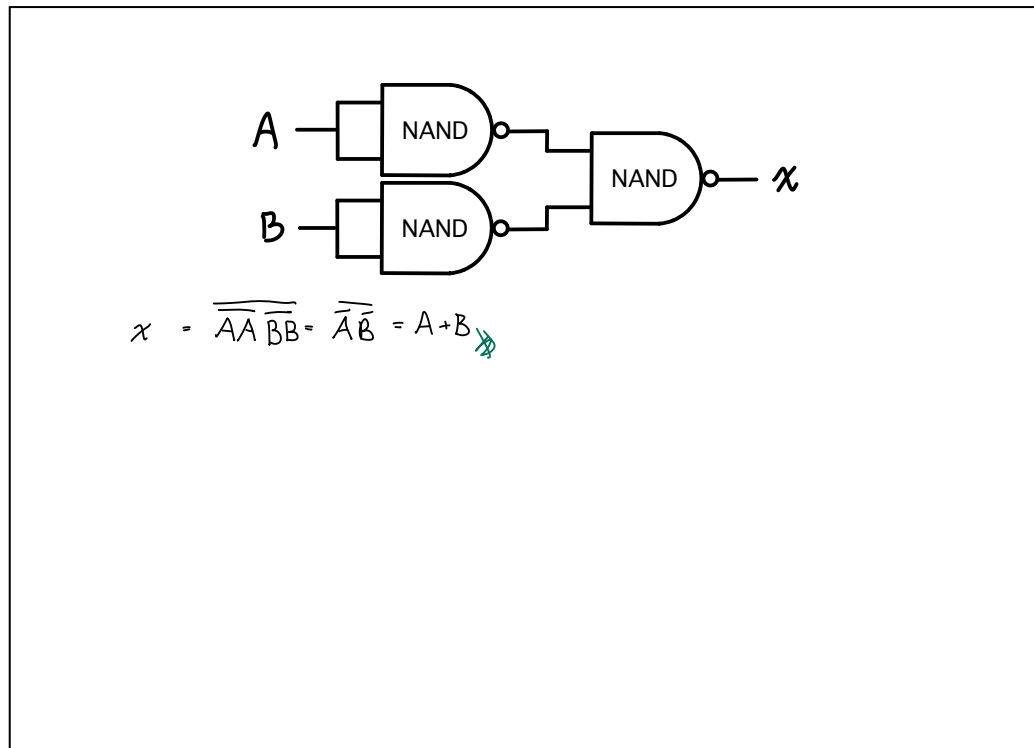2.5 Draw and construct an OR gate using only NAND gate. Prove your answer using Boolean algebra.



Instructor's signature

Sugar

### 3. Assignments

3.1 Build a NOR gate using only NAND gates.

Instructor's signature

3.2 Build a NAND gate using only NOR gates


Instructor's signature

3.3 Build XOR gate using only NAND gates

Instructor's signature


## 3.4 Build half adder circuit using NAND and NOR gates

Instructor's signature

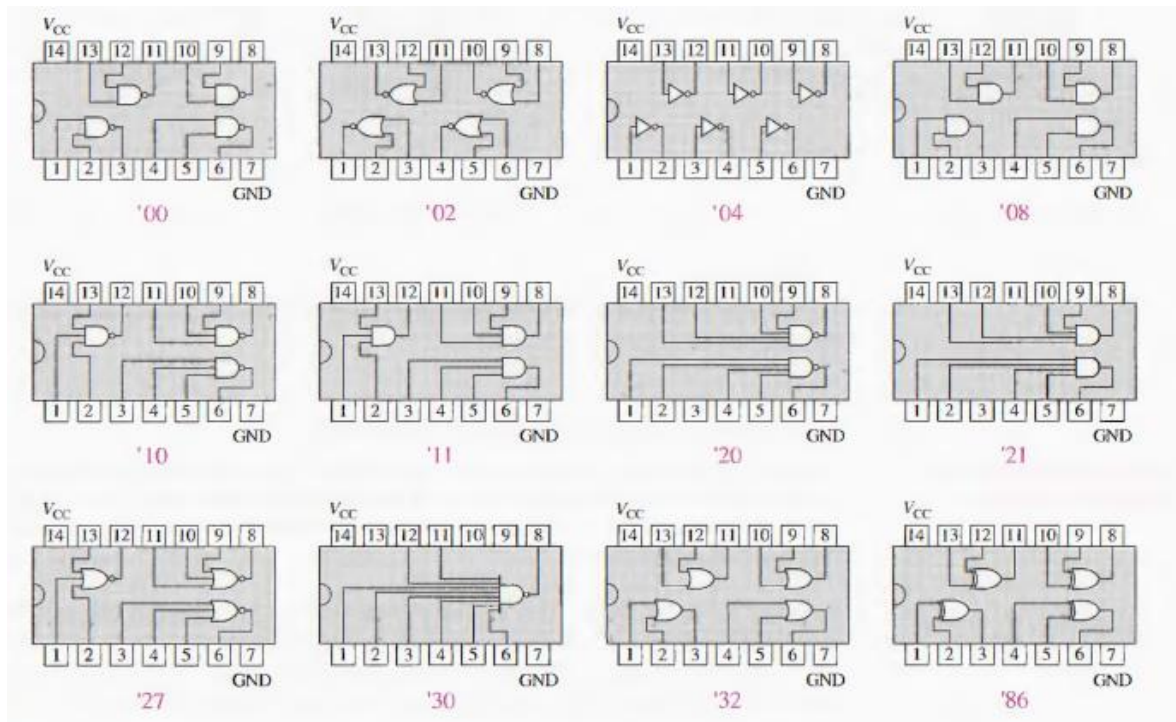Logic Diagram of frequently used gates

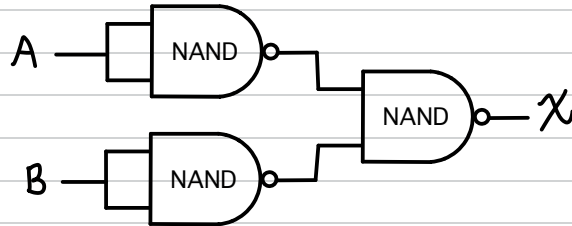
3.1 Build a *NOR* gate using only *NAND* gates.

$$\begin{aligned} X &= \overline{(\overline{A}A)(\overline{B}B)} \\ &= \overline{(\overline{A}+\overline{A})(\overline{B}+\overline{B})} \\ &= \overline{\overline{A}\overline{B}} \\ &= \overline{A+B} \end{aligned}$$



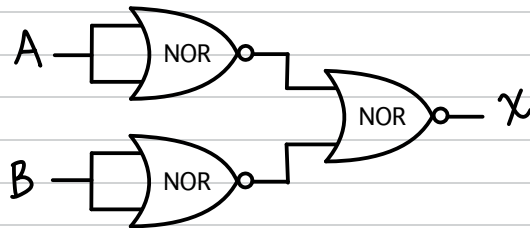
3.2 Build a *NAND* gate using only *NOR* gates

$$\begin{aligned} X &= \overline{(\overline{A+A})(\overline{B+B})} \\ &= \overline{\overline{A}\overline{B}} \\ &= \overline{A+B} \\ &= \overline{AB} \end{aligned}$$



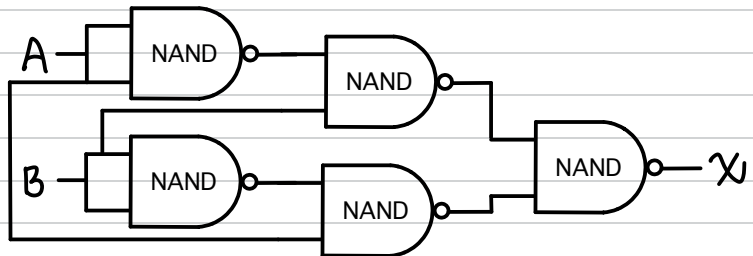3.3 Build *XOR* gate using only *NAND* gates



$$\begin{aligned} X &= \overline{(\overline{A}A(B))(\overline{A}C(B\overline{B}))} \\ &= \overline{(\overline{A}+\overline{A})B(\overline{A}(\overline{B}+\overline{B}))} \\ &= \overline{(\overline{A}B)(\overline{A}\overline{B})} \\ &= \overline{AB + A\overline{B}} \\ &= A \oplus B \end{aligned}$$





### 3.4 Build half adder circuit using NAND and NOR gates

Half Adder

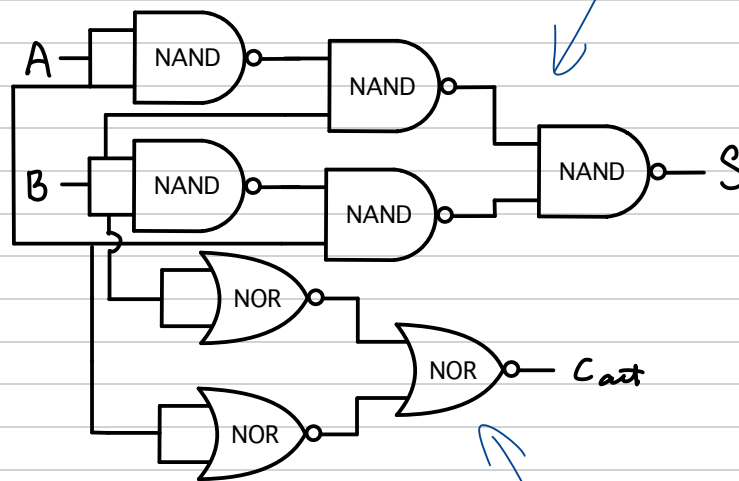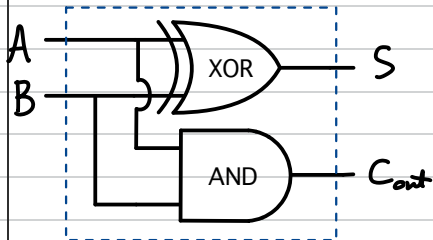

XOR Gate from NAND Gates

AND Gate from NOR Gates.